

GUJARAT TECHNOLOGICAL UNIVERSITY**Diploma Engineering - SEMESTER-IV • EXAMINATION – SUMMER • 2014****Subject Code: 3341105****Date: 03-06-2014****Subject Name: Industrial Electronics****Time: 10:30 am - 01:00 pm****Total Marks: 70****Instructions:**

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.
4. English version is considered to be Authentic.

- Q.1** (a) Explain with neat diagram the working of SCR & its characteristic with two transistor analogy. **07**
 (b) Classify Force commutation and explain with diagram any one method. **07**
- Q.2** (a) Give advantages of polyphase rectifier and state it applications. **07**
 (b) Write short note on “ Insulated Gate Bipolar Transistor(IGBT)” **07**
 OR
 (b) Explain Construction ,working and characteristic of TRIAC. **07**
- Q.3** (a) Classify the type of Chopper and explain in detail step up DC chopper. **07**
 (b) Explain with neat diagram the working of single phase parallel Inverter. **07**
 OR
- Q.3** (a) Explain 3-phase half wave rectifier with circuit diagram and waveform. **07**
 (b) What is Cyclo-converter ? Explain centre tapped transformer type single phase cycloconvertor with step down frequency output. **07**
- Q.4** (a) State advantage and application of Dielectric heating. **07**
 (b) With block diagram explain PLC and give it application. **07**
 OR
- Q.4** (a) Write short note on “ UPS” **07**
 (b) Give importance of Opto-devices. Explain with circuit diagram photo relay with LDR which operates when light falls on it. **07**
- Q.5** (a) Explain AC power control using DIAC and TRIAC. **07**
 (b) Explain construction, working and application of stepper motor. **07**
 OR
- Q.5** (a) Explain speed control of DC shunt motor using thyristors. **07**
 (b) Explain principle of Induction heating and state it advantage and application. **07**

ગુજરાતી

- પ્રશ્ન. ૧ અ SCR ની બે ટ્રાન્સીટર એનલોજી ઉપર થી કાચું પધ્ધતી અને આલેખ દોરી ૦૭
સમજાવો.
બ ફોસ કોમ્યુટેશન ના વિવિધ પ્રકાર આપી કોઈ પણ એક આકૃતી દોરી સમજાવો. ૦૭

- પ્રશ્ન. ૨ અ પોલી ફેઇઝ રેક્ટીફાયર ના ફાયદાઓ અને ઉપયોગો વણવો. ૦૭
બ ટૂક નોંધ લખો : IGBT ૦૭

અથવા

- બ TRIAC નું બંધરણ, સિમ્બોલ, કાચું પધ્ધતી અને આલેખ દોરી સમજાવો. ૦૭
- પ્રશ્ન. ૩ અ ચોપર ના વિવિધ પ્રકાર આપી ડી સી સ્ટેપ અપ ચોપર આકૃતી દોરી સમજાવો. ૦૭
બ SCR 1 ફેઝ પેરલલ ઇવન્ટર ની આકૃતી દોરી ને કાચું પધ્ધતી સમજાવો ૦૭

અથવા

- પ્રશ્ન. ૩ અ ૩-ફેઝ હાફ વેવ રેક્ટીફાયર ની આકૃતી દોરી તેની કાચું પધ્ધતી સમજાવો. ૦૭
બ સાઇકલો કન્વર્ટર શું છે ? સેન્ટર ટેપ ટ્રાંઝોરમર 1 ફેઝ સ્ટેપ ડાઉન ફીક્વન્સી ૦૭
સાઇકલો કન્વર્ટર આકૃતી દોરી તેની કાચું પધ્ધતી સમજાવો.

- પ્રશ્ન. ૪ અ ડાઇ ઇલેક્ટ્રીક હીટીંગ ના ફાયદાઓ અને વિવિધ ઉપયોગ વણવો. ૦૭
બ PLC નો બ્લોક ડયાગ્રામ દોરી સમજાવો અને તેના ઉપયોગો વણવો. ૦૭

અથવા

- પ્રશ્ન. ૪ અ ટૂક નોંધ લખો : “UPS” ૦૭
બ ઓપ્ટો ડીવાઇસ ની અગત્યતા વણવો. LDR ની મદદ થી લાઇટ ઓપરેટેડ ફોટો ૦૭
રીલે LDR ઉપર લાઇટ પડે ત્યારે કાચું કરે તેવી આકૃતી દોરી સમજાવો.

- પ્રશ્ન. ૫ અ DIAC and TRIAC ની મદદ થી AC પાવર કંટ્રોલ ની આકૃતી દોરી સમજાવો. ૦૭
બ સ્ટેપર મોટર બંધરણ, કાચું પધ્ધતી અને ઉપયોગો સમજાવો. ૦૭

અથવા

- પ્રશ્ન. ૫ અ DC સન્ટ મોટર ની સ્પીડ કંટ્રોલ ની થાઇરીસ્ટર ની પધ્ધતી સમજાવો ૦૭
બ ઇન્ડક્શન હીટીંગ નો સિધ્ધાંત આપી ફાયદાઓ અને વિવિધ ઉપયોગ સમજાવો. ૦૭
