

**GUJARAT TECHNOLOGICAL UNIVERSITY****Diploma Engineering - SEMESTER-IV • EXAMINATION – SUMMER • 2014****Subject Code: 3342401****Date: 23-05-2014****Subject Name: DC Power Electronic Converters****Time: 10:30 am - 01:00 pm****Total Marks: 70****Instructions:**

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.
4. English version is considered to be Authentic.

- Q.1** (a) Draw Half wave uncontrolled converter with RL load using freewheeling diode and also draw waveform of  $V_o$ ,  $V_{in}$ , and  $I_o$ . **07**
- (b) Draw Half wave uncontrolled converter with RC load. and also draw waveform of  $V_o$ ,  $V_{in}$ , and  $I_o$ . **07**
- Q.2** (a) Draw Full wave half controlled converters using RL load and also draw waveform of  $V_o$ ,  $V_{in}$ , and  $I_o$ . **07**
- (b) Draw circuit diagram of Single phase parallel dual converters with R load. **07**
- OR
- (b) Give classification of AC to DC converters. **07**
- Q.3** (a) Draw circuit diagram of Three phase six pulse fully controlled converter with R load. **07**
- (b) Draw circuit diagram of boost converter with relevant waveform and derive the equation for output. **07**
- OR
- Q.3** (a) Draw circuit diagram of Three phase three pulse fully controlled converter with R load. **07**
- (b) Draw circuit diagram of buck converter with relevant waveform and derive the equation for output. **07**
- Q.4** (a) Draw circuit diagram of push pull converter with relevant waveform and derive the equation for output. **07**
- (b) Give classification of DC to DC converters. **07**
- OR
- Q.4** (a) Draw circuit diagram of full bridge DC to DC converter with relevant waveform and derive the equation for output. **07**
- (b) Draw isolated CUK converter with necessary waveform. **07**
- Q.5** (a) Draw and explain working of ZVS converter with necessary sketches. **07**
- (b) Draw and Explain voltage commutation technique with necessary waveform. **07**
- OR
- Q.5** (a) Draw and explain working of ZCS converter with necessary sketches. **07**
- (b) Draw and Explain current commutation technique with necessary waveform. **07**

\*\*\*\*\*

## ગુજરાતી

- પ્રશ્ન. ૧ અ ફિ વિલીંગ ડાયોડ વાળી RL લોડ સાથે હાલ્ફ વેવ અન કંટ્રોલ્ડ કંવર્ટર દોરો. અને ૦૭  
Vo, Vin તથા Io ના વેવફોર્મ દોરો.
- બ RC લોડ સાથે હાલ્ફ વેવ અન કંટ્રોલ્ડ કંવર્ટર દોરો. અને Vo, Vin તથા Io ના ૦૭  
વેવફોર્મ દોરો.
- પ્રશ્ન. ૨ અ RL લોડ સાથે કુલ વેવ હાલ્ફ કંટ્રોલ્ડ કંવર્ટર દોરો. અને Vo, Vin તથા Io ના ૦૭  
વેવફોર્મ દોરો.
- બ R લોડ સાથે સિંગલ ફેઝ પેરેલલ ડ્યુઅલ કંવર્ટર ની સરકીટ દોરો. ૦૭
- અથવા
- બ AC ટુ DC કંવર્ટર નુ વર્ગીકરણ કરો. ૦૭
- પ્રશ્ન. ૩ અ R લોડ સાથે થ્રી ફેઝ છ પલ્સ કુલ કંટ્રોલ્ડ કંવર્ટર ની સરકીટ દોરો. ૦૭
- બ બુસ્ટ કંવર્ટર જરુરી વેવફોર્મ સાથે દોરો અને તેન આઉટપુટ નુ સમીકરણ મેળવો. ૦૭
- અથવા
- પ્રશ્ન. ૩ અ R લોડ સાથે થ્રી ફેઝ થ્રી પલ્સ કુલ કંટ્રોલ્ડ કંવર્ટર ની સરકીટ દોરો. ૦૭
- બ બક કંવર્ટર જરુરી વેવફોર્મ સાથે દોરો અને તેન આઉટપુટ નુ સમીકરણ મેળવો. ૦૭
- પ્રશ્ન. ૪ અ પુશ પુલ કંવર્ટર જરુરી વેવફોર્મ સાથે દોરો અને તેન આઉટપુટ નુ સમીકરણ ૦૭  
મેળવો.
- બ DC ટુ DC કંવર્ટર નુ વર્ગીકરણ કરો. ૦૭
- અથવા
- પ્રશ્ન. ૪ અ કુલ બ્રિજ DC ટુ DC કંવર્ટર જરુરી વેવફોર્મ સાથે દોરો અને તેન આઉટપુટ નુ ૦૭  
સમીકરણ મેળવો.
- બ આઇસોલેટેડ કક કંવર્ટર જરુરી વેવફોર્મ સાથે દોરો ૦૭
- પ્રશ્ન. ૫ અ ZVS કંવર્ટર જરુરી આકૃતી સાથે દોરી સમજાવો. ૦૭
- બ વોલ્ટેજ કોમ્યુટેશન સરકીટ જરુરી આકૃતી સાથે દોરી સમજાવો. ૦૭
- અથવા
- પ્રશ્ન. ૫ અ ZCS કંવર્ટર જરુરી આકૃતી સાથે દોરી સમજાવો. ૦૭
- બ કરંટ કોમ્યુટેશન સરકીટ જરુરી આકૃતી સાથે દોરી સમજાવો. ૦૭

\*\*\*\*\*