

GUJARAT TECHNOLOGICAL UNIVERSITY**Diploma Engineering - SEMESTER-IV • EXAMINATION – SUMMER • 2014****Subject Code: 3342405****Date: 03-06-2014****Subject Name: DC Motor Drives****Time: 10:30 am - 01:00 pm****Total Marks: 70****Instructions:**

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.
4. English version is considered to be Authentic.

- Q.1** (a) Explain DC shunt motor connection through a four point starter along with circuit diagram, characteristics and few equations. **07**
(b) Explain rheostatic braking of DC shunt motor. **07**
- Q.2** (a) Draw circuit diagram and waveforms at $\alpha=60^\circ$ for 1-phase half wave controlled DC Drive. **07**
(b) Draw circuit diagram and waveforms at $\alpha=45^\circ$ for 1-phase full wave controlled DC Drive. **07**
- OR
- (b) Draw circuit diagram and waveforms at $\alpha=45^\circ$ for 1-phase semi-controlled DC Drive. **07**
- Q.3** (a) Draw quadrant diagram of speed –torque characteristics for DC Motor drives. **07**
(b) Explain “counter current braking”. **07**
- OR
- Q.3** (a) Discuss adverse effects of heating and give its remedies. **07**
(b) Give classification of electric drives w.r.t load, mode of operation, number of machines, methods of control, etc. **07**
- Q.4** (a) Draw circuit diagram and waveform for 3- Φ half wave controlled DC Drive. **07**
(b) Draw schematic diagram of microprocessor based controller for DC motor drives. **07**
- OR
- Q.4** (a) Explain 1- Φ dual converter DC Drive. **07**
(b) Explain Chopper drives with one application. **07**
- Q.5** (a) Write short note on stepper motor. **07**
(b) Write short note on BLDC motor. **07**
- OR
- Q.5** (a) Discuss four quadrant chopper drive. **07**
(b) Draw torque-speed characteristics of DC Shunt, Series and compound motor. **07**

ગુજરાતી

- પ્રશ્ન. ૧ અ 4-પોઇન્ટ સ્ટાર્ટર સાથે જોડાણ કરેલ ડી.સી. શન્ટ મોટર માટે સર્કીટ,કેરેક્ટરીસ્ટીક ૦૭
અને કેટલાક સુત્રો સાથે વર્ણન કરો.
- બ ડી.સી. શન્ટ મોટર માટે રીઓસ્ટેટીક બ્રેકીંગ નુ વર્ણન કરો. ૦૭
- પ્રશ્ન. ૨ અ 1-ફેઝ હાફ વેવ કંટ્રોલ ડી.સી.ડ્રાઇવ માટે સર્કીટ અને વેવ ફોર્મ ($\alpha=60^\circ$) દોરો. ૦૭
બ 1-ફેઝ ફુલ વેવ કંટ્રોલ ડી.સી.ડ્રાઇવ માટે સર્કીટ અને વેવ ફોર્મ ($\alpha=45^\circ$) દોરો. ૦૭
- અથવા
- બ 1-ફેઝ સેમી કંટ્રોલ ડી.સી.ડ્રાઇવ માટે સર્કીટ અને વેવ ફોર્મ ($\alpha=45^\circ$) દોરો. ૦૭
- પ્રશ્ન. ૩ અ ડી.સી.મોટર ડ્રાઇવ માટે ટોર્ક –સ્પીડ કેરેક્ટરીસ્ટીક નો ક્વાડ્રન્ટ ડાયાગ્રામ દોરો. ૦૭
બ કાઉન્ટર કરન્ટ બ્રેકીંગ નુ વર્ણન કરો. ૦૭
- અથવા
- પ્રશ્ન. ૩ અ હીટીંગ થી થતી વીપરીત અસરો ની ચર્ચા કરો અને તેના ઉપાય જણાવો . ૦૭
બ ઇલેક્ટ્રીકલ ડ્રાઇવ માટે (Load) ભાર,મોડ ઓફ ઓપરેશન, અલગ અલગ મશીન ૦૭
ના કનેક્શન ,સ્પીડ કંટ્રોલ ની જુદી જુદી રીત ,વગેરે સાથે વર્ગીકરણ કરો.
- પ્રશ્ન. ૪ અ ૩-ફેઝ હાફ વેવ કંટ્રોલ ડી.સી.ડ્રાઇવ માટે સર્કીટ અને વેવ ફોર્મ ($\alpha=45^\circ$) દોરો. ૦૭
બ ડી.સી.ડ્રાઇવ માટે માઇક્રોપ્રોસેસર આધારીત કંટ્રોલર નો સ્કીમેટીક ડાયાગ્રામ દોરો. ૦૭
- અથવા
- પ્રશ્ન. ૪ અ ડી.સી.ડ્રાઇવ માટે 1-ફેઝ ડુઅલ કંવર્ટર નુ વર્ણન કરો. ૦૭
બ ચોપર ડ્રાઇવ ની એક એપ્લીકેશન સાથે વર્ણન કરો. ૦૭
- પ્રશ્ન. ૫ અ સ્ટેપર મોટર પર ટુંક નોંધ લખો. ૦૭
બ BLDC મોટર પર ટુંક નોંધ લખો. ૦૭
- અથવા
- પ્રશ્ન. ૫ અ ફોર ક્વાડ્રન્ટ ચોપર ડ્રાઇવ ની ચર્ચા કરો. ૦૭
બ ડી.સી.શન્ટ ,સીરીઝ અને કમ્પાઉન્ડ મોટર ની ટોર્ક –સ્પીડ કેરેક્ટરીસ્ટીક દોરો. ૦૭
