

GUJARAT TECHNOLOGICAL UNIVERSITY
Diploma Engineering - SEMESTER – V • EXAMINATION – WINTER 2012

Subject code: 351704**Date: 28/12/2012****Subject Name: Micro Processor, Interfacing and Application****Time: 10.30 am - 01.00 pm****Total Marks: 70****Instructions:**

1. Attempt any five questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.
4. English version is considered to be Authentic.

- | | | | |
|-------------|-----|---|-----------|
| Q.1 | (a) | What is interfacing? Why it needed? Explain difference between memory-mapped I/O and Peripheral I/O. | 07 |
| | (b) | Draw Interface the national ADC0801 with the 8085 MPU using memory-mapped I/O and the interrupt RST6.5. | 07 |
| Q.2 | (a) | 1) Draw control word register of IC 8255 programmable peripheral interface which shows port A and Port B as input and Port C as output. And use port A and port B as in mode 0.
2) Which port is used in BSR mode of 8255? Draw BSR register to show PC4 bit as a set. | 07 |
| | (b) | Name the IC 8259. How many ICW & OCW in 8259? Explain How ICW and OCW will be Initialized? | 07 |
| OR | | | |
| | (b) | Name the Six mode operation of programmable interrupt timer. Explain any two with wave form. | 07 |
| Q.3 | (a) | Name the IC 8279, Explain with functional block diagram. | 07 |
| | (b) | Design seven-segment LED display as an output device using 3-to-8 decoder use WR and IO/M signal from 8085 to generate IOW (use 74LS20 and 74LS02 Gate) use common-anode seven segment LED. | 07 |
| OR | | | |
| Q.3 | (a) | Name the IC 8237, Explain with functional block diagram. | 07 |
| | (b) | Interface 8 bit 1408D/A converter that is calibrated for 0 to 10 V range with 8085 μ p using 8 input NAND gate, 2 input NOR gate 74LS373 Latch. | 07 |
| Q.4 | (a) | Explain data acquisition system using microprocessor. | 07 |
| | (b) | Which Port is not used in 8255 Mode 2? Explain Mode 2 with control signals. | 07 |
| OR | | | |
| Q. 4 | (a) | Explain different interrupt mode of programmable interrupt controller. | 07 |
| | (b) | Explain concept of Analog to Digital converter and Digital to Analog converter in detail. Name which method is used for ADC and DAC conversion. | 07 |
| Q.5 | (a) | Explain level monitor system using microprocessor | 07 |
| | (b) | Explain dc motor control using microprocessor. | 07 |
| OR | | | |
| Q.5 | (a) | Name the IC 8251, Explain with functional block diagram. | 07 |
| | (b) | Explain temperature monitoring system using microprocessor. | 07 |

પ્રશ્ન-1	અ	ઇન્ટરફેસિંગ એટલે શુ? કેમ જરૂરિ કેમ છે?મેમરી મેખ I/O અને પેરિફરલ I/O વચ્ચે નો તફાવત આપો.	07
	બ	મેમરી મેખ I/O અને ઇન્ટરફેસિંગ RST6.5 નો ઉપયોગ કરીને નેશનલ ADC0801 નુ માઇક્રોપ્રોસેસર જોડે ઇન્ટરફેસિંગ દોરો.	07
પ્રશ્ન-2	અ	1) IC 8255 પ્રોગ્રામેબલ પેરિફરલ ઇન્ટરફેસિંગનુ કંટ્રોલ વર્ડ રજિસ્ટર દોરો.જેમાં પોર્ટ એ અને પોર્ટ બી ઇનપુટ તરીકે અને પોર્ટ સી આઉટપુટ તરીકે બતાવો અને.પોર્ટ એ,બી મોડ જુરો માં છે. 2) IC 8255 ના BSR મોડ માં કયો પોર્ટ ઉપયોગ થાય છે? PC 4બીટ ને સેટ કરતુ BSR રજિસ્ટર દોરો.	07
	બ	IC 8259 નું નામ આપો. અને કેટલા ICW અને OCW IC 8259 માં હોય છે?ICW અને OCW કેવી રીતે ચાલુ કારાય છે તે સમજાવો.	07
		અથવા	
	બ	પ્રોગ્રામેબલ ટાઇમરના છ જુદા જુદા મોડ ના નામ આપો.કોઇ પન બે વેવફોર્મ ધ્વારા સમજાવો.	07
પ્રશ્ન-3	અ	IC 8279 નું નામ આપો આકૃતિ ધ્વારા દરેક ફંક્સનલ બ્લોક સમજાવો.	07
	બ	સાત સેગમેન્ટ LED ને આઉટપુટ ડીવાઇસ તરીકે દર્શવતુ ઇન્ટરફેસિંગ દોરો જેમાં 3 to 8 ડીકોડર અને 8085 ની WR અને IO/M સીગ્નલ નો ઉપયોગ કરી IOW સિગ્નલ બનઓ જેમાં 74LS20 અને 74LS02 ગેટ નો ઉપયોગ કરવો.સાત સેગમેન્ટ LED નો ઉપયોગ કોમન એનોડ તરીકે કરવો.	07
		અથવા	
પ્રશ્ન-3	અ	IC 8237 નું નામ આપો આકૃતિ ધ્વારા દરેક ફંક્સનલ બ્લોક સમજાવો.	07
	બ	8 ઇનપુટ NAND ગેટ 2 ઇનપુટ NOR ગેટ અને 74LS373 લેચ નો ઉપયોગ કરી 8 બિટ 1408 D/A કન્વર્ટર જે 0 to 10 volt મા કેલિબ્રેટ કરેલુ છે તેનુ ઇન્ટરફેસિંગ 8085 માઇક્રોપ્રોસેસર સાથે દર્શાવો.	07
પ્રશ્ન-4	અ	માઇક્રોપ્રોસેસર ઉપયોગ કરીને ડેટા એક્વીજિસન સિસ્ટમ સમજાવો.	07
	બ	IC 8255 નાં મોડ 2 માં કયો પોર્ટ ઉપયોગ માં નથી આવતો?અને મોડ 2 કંટ્રોલ સિગ્નલ સાથે સમજાવો.	07
		અથવા	
પ્રશ્ન-4	અ	પ્રોગ્રામેબલ ઇન્ટરપ્રુટ કંટ્રોલર નાં જુદા જુદા ઇન્ટરપ્રુટ મોડ સમજાવો.	07
	બ	એનાલોગ ટુ ડીજીટલ અને ડીજીટલ ટુ એનાલોગ નો વિસ્તૃત ખ્યાલ આપો.ADC અને DAC કંવર્સન માટે વપરાતી મેથડ ના નામ આપો.	07
પ્રશ્ન-5	અ	માઇક્રોપ્રોસેસર ઉપયોગ કરીને લેવલ મોનિટરીંગ સીસ્ટમ સમજાવો.	07
	બ	માઇક્રોપ્રોસેસર ઉપયોગ કરીને ડીસી મોટર સિસ્ટમ સમજાવો.	07
		અથવા	
પ્રશ્ન-5	અ	IC 8251 નું નામ આપો આકૃતિ ધ્વારા દરેક ફંક્સનલ બ્લોક સમજાવો.	07
	બ	માઇક્રોપ્રોસેસર ઉપયોગ કરીને ટેમ્પરેચર મોનિટરીંગ સિસ્ટમ સમજાવો.	07
