

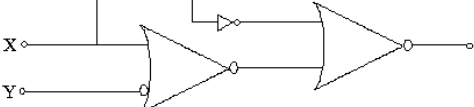
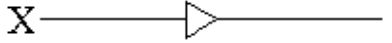

Seat No.: _____

Enrolment No. _____

GUJARAT TECHNOLOGICAL UNIVERSITY**Diploma Engineering C to D Bridge Course Examination – WINTER 2013****Subject Code: C310702****Date: 26-12-2013****Subject Name: Fundamental of Digital Electronics****Time: 02:30 pm - 04:00 pm****Total Marks: 70****Instructions:**

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Each Question is of 1 Mark.
4. English version is considered to be Authentic.
5. Use of Simple Calculator is permissible. (Scientific / Higher Version not allowed)

No.	Question Text and Option			
1.	All arithmetic calculation & logical decisions are performed by in _____ unit.			
	A.	Memory unit	B.	Control unit
	C.	ALU	D.	Output unit
2.	What is the base of binary number?			
	A.	2	B.	10
	C.	8	D.	16
3.	What is 2's complement of 00101101?			
	A.	-45	B.	11010001
	C.	11010011	D.	+45
4.	What is the 9's complement of 3465?			
	A.	6534	B.	6535
	C.	7645	D.	7646
5.	$(10101)_2 = (\quad)_{10}$			
	A.	22	B.	20
	C.	21	D.	25
6.	$(163.875)_{10} = (\quad)_2$			
	A.	10100011.111	B.	10100010.101
	C.	10100010.111	D.	10100010.001
7.	$1 + 1 = \underline{\hspace{1cm}}$			
	A.	11	B.	2
	C.	10	D.	None
8.	$(65.52)_8 = (\quad)_2$			
	A.	110101.101010	B.	101110.110010
	C.	110110.110010	D.	101110.110110
9.	$(1011011011)_2 = (\quad)_{16}$			
	A.	2FD	B.	3DB
	C.	2DB	D.	2FB
10.	$(5C7)_{16} = (\quad)_{10}$			
	A.	1479	B.	1580
	C.	1579	D.	1480
11.	The reflected code is also known as _____ code.			
	A.	ASCII	B.	Grey
	C.	XS-3 Grey	D.	XS-3
12.	The even parity of 0010 BCD code is ____.			
	A.	00	B.	0
	C.	11	D.	1
13.	$(10101111001.0111)_2 = (\quad)_8$			
	A.	3571.35	B.	2571.34
	C.	2570.34	D.	2571.35

14.	$(2598.675)_{10} = (\text{_____})_{16}$			
	A.	A27.ACCC	B.	A25.BCCC
	C.	A24.BCCC	D.	A26.ACCC
15.	$1 \text{ AND } 1 = \underline{\hspace{1cm}}$			
	A.	2	B.	1
	C.	0	D.	None
16.	$1 \text{ OR } 0 = \underline{\hspace{1cm}}$			
	A.	10	B.	0
	C.	None	D.	1
17.	The NAND gate output will be low if the two inputs are <u> </u> .			
	A.	00	B.	11
	C.	10	D.	01
18.	The simplification of the Boolean expression $(A'BC')' + (AB'C)'$ is <u> </u> .			
	A.	BC	B.	0
	C.	A	D.	1
19.	The Boolean expression $A'B + AB' + AB$ is equivalent to <u> </u> .			
	A.	$A'B$	B.	$A+B$
	C.	$(AB)'$	D.	AB
20.	The output of a logic gate is 1 when all its inputs are at logic 0. The gate is either <u> </u> .			
	A.	a NAND or an EX-OR	B.	an OR or an EX-NOR
	C.	an AND or an EX-OR	D.	a NOR or an EX-NOR
21.	De Morgan's first theorem shows the equivalence of <u> </u> .			
	A.	NOR gate & Bubbled AND gate.	B.	OR gate & Ex-OR gate.
	C.	NOR gate & NAND gate.	D.	NAND gate and NOT gate
22.	The logic circuit shown in the given fig. can be minimized to <u> </u> .			
				
	A.		B.	
23.	How many AND gates are required to realize $Y = CD + EF + G$?			
	A.	2	B.	3
	C.	4	D.	5
24.	The NOR gate output will be low if the two inputs are <u> </u> .			
	A.	All	B.	01
	C.	10	D.	11
25.	How many two-input AND & OR gates are required to realize $Y = CD + EF + G$?			
	A.	2,2	B.	2,3
	C.	3,3	D.	None
26.	When an input signal $A = 11001$ is applied to a NOT gate serially, its output signal is <u> </u> .			
	A.	00110	B.	01100
	C.	00111	D.	10101
27.	A universal logic gate is one, which can be used to generate any logic function. Which of the following is a universal logic gate?			
	A.	NAND	B.	OR
	C.	XOR	D.	AND
28.	How many two input AND gates and two input OR gates are required to realize $Y = BD + CE + AB$?			
	A.	1,1	B.	4,2
	C.	3,2	D.	2,3

29.	K - Map is used for the purpose of ____.		
	A.	To minimize the terms in a Boolean expression.	B. Reducing the electronic circuits used.
	C.	To maximize the terms of a given a Boolean expression.	D. To map the given Boolean logic function.
30.	____ is a sum term or a logical product (AND) of several sum terms.		
	A.	POS	B. SOP
	C.	Minterm	D. Either A or B.
31.	Canonical form is a unique way of representing ____.		
	A.	SOP	B. Boolean Expressions
	C.	Minterm	D. None
32.	A K-map is an abstract form of ____ diagram, organized as a matrix of squares.		
	A.	Block Diagram	B. Venn Diagram
	C.	Cycle Diagram	D. Triangular Diagram
33.	There are __ Minterms for 3 variables (a, b, c).		
	A.	2	B. 8
	C.	0	D. None
34.	There are __ cells in a 4-variable K-map.		
	A.	12	B. 16
	C.	18	D. None
35.	Each product term of a group, w'xy' and wy, represents the ____ in that group.		
	A.	POS	B. Sum of Minterms
	C.	Input	D. Both A & B
36.	Each group of adjacent Minterms (group size in powers of twos) corresponds to a possible product term of the given ____.		
	A.	Value	B. Function
	C.	Set	D. None
37.	Don't care conditions can be used for simplifying Boolean expressions in ____.		
	A.	Terms	B. K – Maps
	C.	Examples	D. None
38.	Don't care terms should be used along with the terms that are present in ____.		
	A.	Maxterm	B. Minterms
	C.	K-Map	D. None
39.	A ____ is a table, which consists of every possible combination of inputs and its corresponding outputs.		
	A.	False Table	B. Truth Table
	C.	K – Map	D. None
40.	There are __ cells in a 3-variable K-map.		
	A.	6	B. 8
	C.	9	D. None
41.	The don't care terms are denoted by ____.		
	A.	Ø	B. d
	C.	All	D. X
42.	A group of 2 cells is called a ____.		
	A.	Quad	B. Octet
	C.	Pair	D. None
43.	____ is a simple combinational digital circuit built from logic gates.		
	A.	None	B. Null Adder
	C.	Half Adder	D. Full Adder
44.	____ is used to subtract two inputs having more than one bit.		
	A.	Half Subtractor	B. Counter
	C.	Full Subtractor Circuit	D. Multiplexer
45.	____ is a circuit, which subtracts two inputs each of one bit.		
	A.	All	B. Full Subtractor
	C.	Half Subtractor	D. Full Adder






46.	A ____ circuit converts the code of one form to another form.			
	A.	All	B.	Decoder
	C.	Code Converter	D.	Encoder
47.	A full adder logic circuit will have ____.			
	A.	2 inputs and 2 outputs.	B.	3 inputs and 3 outputs.
	C.	3 inputs and 2 outputs.	D.	2 inputs and 1 output.
48.	A ____ Converter deals with converting binary code to gray code.			
	A.	Gray to Binary Code	B.	Binary Code
	C.	Binary to Gray Code	D.	Grey Code
49.	The full adder is the combination of ____.			
	A.	2 Half Subtractor	B.	2 BCD Adder
	C.	2 Half Adder	D.	None
50.	A Full Subtractor is the combination of ____.			
	A.	2 Half Adder	B.	2 BCD Subtractor
	C.	2 Half Subtractor	D.	None
51.	In half adder, the carry is 1 when $AB =$ ____.			
	A.	01	B.	10
	C.	00	D.	11
52.	In Half Subtractor, borrow is 1 when $XY =$ ____.			
	A.	00	B.	10
	C.	11	D.	01
53.	In half adder, Sum $S =$ ____.			
	A.	$A'B + AB'$	B.	$A \text{ XOR } B$
	C.	None	D.	Both A & B
54.	In Half Subtractor, Difference $D =$ ____.			
	A.	$A'B + AB'$	B.	$A \text{ XOR } B$
	C.	None	D.	Both A & B
55.	In Half Subtractor, borrow $B_{out} =$ ____.			
	A.	XY'	B.	XY
	C.	$X'Y'$	D.	$X'Y$
56.	In half adder, Carry $C =$ ____.			
	A.	$A'B'$	B.	$A'B$
	C.	AB'	D.	AB
57.	The number of control lines for an 8 – to – 1 multiplexer is ____.			
	A.	2	B.	4
	C.	5	D.	3
58.	The device which changes from serial data to parallel data is ____.			
	A.	MULTIPLEXER	B.	COUNTER
	C.	FLIP-FLOP	D.	DEMULTIPLEXER
59.	A device which converts BCD to Seven Segment is called ____.			
	A.	Encoder	B.	Demultiplexer
	C.	Multiplexer	D.	Decoder
60.	The number of control lines for 16 to 1 multiplexer is ____.			
	A.	2	B.	3
	C.	5	D.	4
61.	The number of control lines for 32 to 1 multiplexer is ____.			
	A.	5	B.	4
	C.	6	D.	6
62.	A 1 to 16 Demultiplexer requires __ select lines.			
	A.	2	B.	4
	C.	5	D.	8
63.	A multiplexer is also called ____.			
	A.	Many into One	B.	Data Selector
	C.	Both A & B	D.	None

64.	The word “Demultiplex” means ____.			
	A.	Many	B.	None
	C.	One	D.	One into Many
65.	A 3 to 8 Decoder is also called ____.			
	A.	Binary to Octal decoder	B.	Grey Code Converter
	C.	Binary Code Converter	D.	None
66.	Decoders are used in ____.			
	A.	Counter systems.	B.	All
	C.	A/D converters.	D.	To drive a display system.
67.	A combinational circuit is one in which the output depends on the ____.			
	A.	Input combination & the previous output.	B.	Present output & the previous output.
	C.	Input combination at that time.	D.	None
68.	A ____ generates a particular binary word or number.			
	A.	Decoder	B.	Demultiplexer
	C.	Encoder	D.	Multiplexer
69.	A ____ is used to change a BCD number into an equivalent decimal number.			
	A.	Decoder	B.	Demultiplexer
	C.	Encoder	D.	Multiplexer
70.	A 1 to 8 Demultiplexer requires ____ select lines.			
	A.	1	B.	3
	C.	2	D.	4

ગુજરાતી

નં.	પ્રશ્ન તેમજ વિકલ્પ			
૧.	બધી એરીથમેટીક ગણતરી અને લોજીકલ ડીસીજન ____ યુનીટ દ્વારા પરફોર્મ થાય છે.			
	A.	મેમરી યુનીટ	B.	કંટ્રોલ યુનીટ
	C.	ALU	D.	આઉટપુટ યુનીટ
૨.	બાઈનરી નંબરનો બેઝ શું છે?			
	A.	૨	B.	૧૦
	C.	૮	D.	૧૬
૩.	૦૦૧૦૧૧૦૧નું ૨નું કોમ્પલીમેન્ટ શું છે?			
	A.	-૪૫	B.	૧૧૦૧૦૦૦૧
	C.	૧૧૦૧૦૦૧૧	D.	+૪૫
૪.	૩૪૬૫નું ૮નું કોમ્પલીમેન્ટ શું છે?			
	A.	૬૫૩૪	B.	૬૫૩૫
	C.	૭૬૪૫	D.	૭૬૪૬
૫.	$(૧૦૧૦૧)_2 = (_)_{10}$			
	A.	૨૨	B.	૨૦
	C.	૨૧	D.	૨૫
૬.	$(૧૬૩.૮૭૫)_{10} = (_)_2$			
	A.	૧૦૧૦૦૦૧૧.૧૧૧	B.	૧૦૧૦૦૦૧૦.૧૦૧
	C.	૧૦૧૦૦૦૧૦.૧૧૧	D.	૧૦૧૦૦૦૧૦.૦૦૧

૭.	$1 + 1 = \underline{\hspace{1cm}}$			
	A.	૧૧	B.	૨
	C.	૧૦	D.	એક પણ નહીં
૮.	$(54.42)_6 = (\underline{\hspace{1cm}})_2$			
	A.	૧૧૦૧૦૧.૧૦૧૦૧૦	B.	૧૦૧૧૧૦.૧૧૦૦૧૦
	C.	૧૧૦૧૧૦.૧૧૦૦૧૦	D.	૧૦૧૧૧૦.૧૧૦૧૧૦
૯.	$(1011011011)_2 = (\underline{\hspace{1cm}})_{15}$			
	A.	૨FD	B.	૩DB
	C.	૨DB	D.	૨FB
૧૦.	$(4C9)_{15} = (\underline{\hspace{1cm}})_{10}$			
	A.	૧૪૭૯	B.	૧૫૮૦
	C.	૧૫૭૯	D.	૧૪૮૦
૧૧.	રીફ્લેક્સ કોડ _____ કોડથી પણ ઓળખાય છે.			
	A.	ASCII	B.	ગ્રેય
	C.	XS-3 ગ્રેય	D.	XS-3
૧૨.	૦૦૧૦ BCD કોડની ઇવન પેરીટી _____ છે.			
	A.	૦૦	B.	૦
	C.	૧૧	D.	૧
૧૩.	$(10101111001.0111)_2 = (\underline{\hspace{1cm}})_6$			
	A.	૩૫૭૧.૩૫	B.	૨૫૭૧.૩૪
	C.	૨૫૭૦.૩૪	D.	૨૫૭૧.૩૫
૧૪.	$(2467.594)_{10} = (\underline{\hspace{1cm}})_{15}$			
	A.	A૨૭.ACCC	B.	A૨૫.BCCC
	C.	A૨૪.BCCC	D.	A૨૬.ACCC
૧૫.	$1 \text{ AND } 1 = \underline{\hspace{1cm}}$.			
	A.	૨	B.	૧
	C.	૦	D.	એક પણ નહીં
૧૬.	$1 \text{ OR } 0 = \underline{\hspace{1cm}}$.			
	A.	૧૦	B.	૦
	C.	એક પણ નહીં	D.	૧
૧૭.	જો બન્ને ઇનપુટ _____ છે તો NAND ગેટનું આઉટપુટ લો હશે.			
	A.	૦૦	B.	૧૧
	C.	૧૦	D.	૦૧
૧૮.	$(A'BC')' + (AB'C)'$ બુલીયન એક્સપ્રેશનનું સીમ્પ્લીફિકેશન _____ છે.			
	A.	BC	B.	0
	C.	A	D.	૧

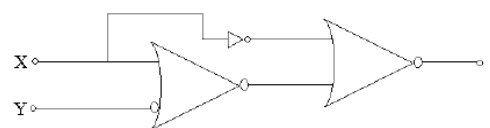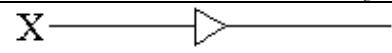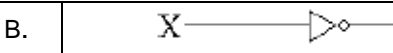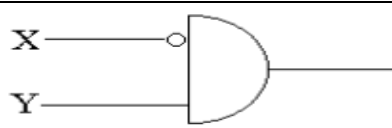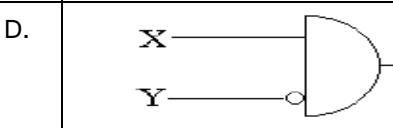૧૮.	A'B + AB' + AB બુલીયન એક્ષપ્રેશનનું ઇક્વીવેલન્ટ ____ છે.			
	A.	A'B	B.	A+B
	C.	(AB)'	D.	AB
૨૦.	જ્યારે લોજિક ગેટનાં બધા ઇનપુટ ૦ લોજિક છે ત્યારે તેનું આઉટપુટ ૧ છે. ગેટ ____ છે			
	A.	NAND કે EX-OR	B.	OR કે EX-NOR
	C.	AND કે EX-OR	D.	NOR કે EX-NOR
૨૧.	De Morganનો પહેલો નિયમ ____ની સરખામણી બતાવે છે.			
	A.	NOR ગેટ અને Bubbled ANDગેટ	B.	OR ગેટ અને EX-OR ગેટ
	C.	NOR ગેટ અને NAND ગેટ	D.	NAND ગેટ અને NOT ગેટ
૨૨.	નીચે દર્શાવેલ લોજિક સર્કીટ ____ માં મીનીમાઇઝ થઈ શકે.			
				
	A.		B.	
	C.		D.	
૨૩.	Y = CD+EF+G દર્શાવવા માટે કેટલા AND ગેટની જરૂર પડે?			
	A.	૨	B.	૩
	C.	૪	D.	૫
૨૪.	જો બે ઇનપુટ __ હોય તો NOR ગેટનું આઉટપુટ લો હશે.			
	A.		B.	૦૧
	C.	૧૦	D.	૧૧
૨૫.	Y = CD+EF+G દર્શાવવા માટે કેટલા AND અને OR ગેટની જરૂર પડે?			
	A.	૨, ૨	B.	૨, ૩
	C.	૩, ૩	D.	એક પણ નહીં
૨૬.	જ્યારે ઇનપુટ સીઝલ A = ૧૧૦૦૧ NOT ગેટમાં સીરીયલી આપવામાં આવે ત્યારે તેનું આઉટપુટ ____ છે.			
	A.	૦૦૧૧૦	B.	૦૧૧૦૦
	C.	૦૦૧૧૧	D.	૧૦૧૦૧
૨૭.	એક એવો યુનિવર્સલ ગેટ છે કે જેનો ઉપયોગ કોઈ પણ લોજિક ફંક્શન જનરેટ કરવા માટે થઈ શકે. નીચેમાંથી કયો યુનિવર્સલ ગેટ છે?			
	A.	NAND	B.	OR
	C.	XOR	D.	AND

૨૮.	Y = BD+CE+AB દર્શાવવા માટે કેટલા બે ઈનપુટ AND ગેટ અને બે ઈનપુટ OR ગેટની જરૂર પડે?			
	A.	૧,૧	B.	૪,૨
	C.	૩,૨	D.	૨,૩
૨૯.	K – Mapનો ઉપયોગ _____ નાં પરપઝ માટે થાય છે.			
	A.	બુલીયન એક્સપ્રેશનમાં ટર્મ્સ મીનીમાઇઝ કરવા	B.	ઇલેક્ટ્રોનીક્સ સર્કીટમો વપરાશ ઘટાડવા
	C.	આપેલાં બુલીયન એક્સપ્રેશનની ટર્મ્સ મીનીમાઇઝ કરવા	D.	આપેલાં બુલીયન લોજીક ફંક્શન મેપ કરવા
૩૦.	થોડા Sum ટર્મ્સની sum ટર્મ અથવા લોજીકલ પ્રોડક્ટ (AND) _____ છે.			
	A.	POS	B.	SOP
	C.	મીનટર્મ	D.	A અથવા B
૩૧.	_____ દર્શાવવાનો યુનિક વે કેનોનિકલ ફોર્મ છે.			
	A.	SOP	B.	બુલીયન એક્સપ્રેશન
	C.	મીનટર્મ	D.	એક પણ નહીં
૩૨.	સ્કેઅરનો મેટ્રીક્ષ દર્શાવતો K – Map _____ ડાયાગ્રામનું એબસ્ટ્રેક્ટ ફોર્મ છે.			
	A.	બ્લોક ડાયાગ્રામ	B.	વેન ડાયાગ્રામ
	C.	સાયકલ ડાયાગ્રામ	D.	ટ્રાયંગ્યુલર ડાયાગ્રામ
૩૩.	૩ વેરીએબલ (a,b,c) માટે _____ મીનટર્મ્સ છે.			
	A.	૨	B.	૮
	C.	૦	D.	
૩૪.	૪ વેરીએબલ K – Mapમાં _____ શેલ્સ છે.			
	A.	૧૨	B.	૧૬
	C.	૧૮	D.	
૩૫.	ગ્રુપનાં પ્રત્યેક પ્રોડક્ટ ટર્મ w'xy' અને wy તે ગ્રુપમાં _____ દર્શાવે છે.			
	A.	POS	B.	મીનટર્મ્સનો સરવાળો
	C.	ઈનપુટ	D.	A અને B બન્ને
૩૬.	એડજેસ્ટ મીનટર્મ્સનું પ્રત્યેક ગ્રુપ (બેનાં પાવરમાં ગ્રુપ સાઈઝ) આપેલા _____નાં સંભવિત પ્રોડક્ટ ટર્મ દર્શાવે છે.			
	A.	વેલ્યુ	B.	ફંક્શન
	C.	સેટ	D.	એક પણ નહીં
૩૭.	ડોટ ક્રેડ કંડીશનનો ઉપયોગ _____ માં બુલીયન એક્સપ્રેશન સીમ્પ્લીફાઇ કરવા માટે થઈ શકે.			
	A.	ટર્મ્સ	B.	K – Maps
	C.	એક્ઝામ્પ્લસ	D.	એક પણ નહીં

૩૮.	ડોટ કેર કંડીશનનો ઉપયોગ ટર્મ્સ સાથે કે જે _____ માં ઉપસ્થીત હોય ત્યારે કરવો જોઈએ.			
	A.	મેક્સટર્મ	B.	મીનટર્મ
	C.	K - Map	D.	એક પણ નહી
૩૯.	_____ એક ટેબલ છે કે જે ઇનપુટ અને તેને અનુરૂપ આઉટપુટની પ્રત્યેક શક્ય કોમ્બીનેશન ધરાવે છે.			
	A.	ફ્લ્સ ટેબલ	B.	ટ્રુથ ટેબલ
	C.	K - Map	D.	એક પણ નહી
૪૦.	૩ વેરીએબલ K - Mapમાં _____ શેલ્સ છે.			
	A.	૬	B.	૮
	C.	૯	D.	એક પણ નહી
૪૧.	ડોટ કેર ટર્મ્સને _____ વડે દર્શાવવામાં આવે છે.			
	A.	Ø	B.	d
	C.	બધા	D.	X
૪૨.	૨ સેલ્સનાં ગ્રુપને _____ કહેવાય છે.			
	A.	કલ્ડ	B.	ઓક્ટેટ
	C.	જોડી	D.	એક પણ નહી
૪૩.	લોજીક ગેઈટ્સમાંથી બનાવેલ સીમ્પલ કોમ્બીનેશનલ ડીજીટલ સર્કીટ _____ છે.			
	A.	એક પણ નહી	B.	નલ એડર
	C.	હાફ એડર	D.	ફૂલ એડર
૪૪.	એકથી વધારે બીટ ધરાવતાં બે ઇનપુટને બાદ કરવા _____ છે.			
	A.	હાફ એડર	B.	કાઉન્ટર
	C.	ફૂલ સબટ્રેક્ટર સર્કીટ	D.	મલ્ટીપ્લેક્સર
૪૫.	_____ સર્કીટ છે કે જે એક બીટવાળા બે ઇનપુટને બાદ કરે છે.			
	A.	બધા	B.	ફૂલ સબટ્રેક્ટર
	C.	હાફ સબટ્રેક્ટર	D.	ફૂલ એડર
૪૬.	_____ સર્કીટ કોડને એક ફોર્મમાંથી બીજાં ફોર્મમાં બદલે છે.			
	A.	બધા	B.	ડીકોડર
	C.	કોડ કન્વર્ટર	D.	એનકોડર
૪૭.	ફૂલ એડર સર્કીટ _____ હશે.			
	A.	૨ ઇનપુટ અને ૨ આઉટપુટ	B.	૩ ઇનપુટ અને ૩ આઉટપુટ
	C.	૩ ઇનપુટ અને ૨ આઉટપુટ	D.	૨ ઇનપુટ અને ૧ આઉટપુટ
૪૮.	_____ કન્વર્ટર બાઈનરી કોડમાંથી ગ્રેય કોડમાં રૂપાંતર કરે છે.			
	A.	ગ્રેય ટુ બાઈનરી કોડ	B.	બાઈનરી કોડ
	C.	બાઈનરી ટુ ગ્રેય કોડ	D.	ગ્રેય કોડ

	ફૂલ એડર _____ નું કોમ્પીનેશન છે.			
૪૯.	A.	૨ હાફ સબટ્રેક્ટર	B.	૨ BCD એડર
	C.	૨ હાફ એડર	D.	એક પણ નહી
	ફૂલ સબટ્રેક્ટર _____ નું કોમ્પીનેશન છે.			
૫૦.	A.	૨ હાફ એડર	B.	૨ BCD સબટ્રેક્ટર
	C.	૨ હાફ સબટ્રેક્ટર	D.	એક પણ નહી
	હાફ એડરમાં, કેરી ૧ છે જ્યારે $AB = \underline{\hspace{1cm}}$.			
૫૧.	A.	૦૧	B.	૧૦
	C.	૦૦	D.	૧૧
	હાફ સબટ્રેક્ટરમાં, બોરોવ ૧ છે જ્યારે $XY = \underline{\hspace{1cm}}$.			
૫૨.	A.	૦૦	B.	૧૦
	C.	૧૧	D.	૦૧
	હાફ એડરમાં, $\text{Sum } S = \underline{\hspace{1cm}}$.			
૫૩.	A.	$A'B + AB'$	B.	$A \text{ XOR } B$
	C.	એક પણ નહી	D.	બન્ને A અને B
	હાફ સબટ્રેક્ટરમાં, $\text{Difference } D = \underline{\hspace{1cm}}$.			
૫૪.	A.	$A'B + AB'$	B.	$A \text{ XOR } B$
	C.	એક પણ નહી	D.	બન્ને A અને B
	હાફ સબટ્રેક્ટરમાં, બોરોવ $B_{\text{out}} = \underline{\hspace{1cm}}$.			
૫૫.	A.	XY'	B.	XY
	C.	$X'Y'$	D.	$X'Y$
	હાફ એડરમાં, કેરી $C = \underline{\hspace{1cm}}$.			
૫૬.	A.	$A'B'$	B.	$A'B$
	C.	AB'	D.	AB
	૮ ટુ ૧ મલ્ટીપ્લેક્ષર માટે કંટ્રોલ લાઈનની સંખ્યા _____ હોય છે.			
૫૭.	A.	૨	B.	૪
	C.	૫	D.	૩
	એક સાધન કે જે સીરીયલ ડેટાને પેરેલલ ડેટામાં બદલે છે તે _____ છે.			
૫૮.	A.	મલ્ટીપ્લેક્ષર	B.	કાઉન્ટર
	C.	ફ્લોપ ફ્લોપ	D.	ડીમલ્ટીપ્લેક્ષર
	એક સાધન કે જે BCDને સેવન સેગમેન્ટમાં બદલે છે તે _____ છે.			
૫૯.	A.	એનકોડર	B.	ડીમલ્ટીપ્લેક્ષર
	C.	મલ્ટીપ્લેક્ષર	D.	કાઉન્ટર
	૧૬ ટુ ૧ મલ્ટીપ્લેક્ષર માટે કંટ્રોલ લાઈનની સંખ્યા _____ હોય છે.			
૬૦.	A.	૨	B.	૪
	C.	૫	D.	૩

૬૧.	૩૨ ટુ ૧ મલ્ટીપ્લેક્ષર માટે કંટ્રોલ લાઈનની સંખ્યા __ હોય છે.			
	A.	૫	B.	૩
	C.	૬	D.	૪
૬૨.	૧ ટુ ૧૬ ડીમલ્ટીપ્લેક્ષર __ સીલેક્ટ લાઈન્સ જોઈએ છે.			
	A.	૨	B.	૪
	C.	૫	D.	૮
૬૩.	મલ્ટીપ્લેક્ષરને _____ પણ કહે છે.			
	A.	મેની ઈન્ટ્રુ વન	B.	ડેટા સીલેક્ટર
	C.	બન્ને A અને B	D.	એક પણ નહી
૬૪.	ડીમલ્ટીપ્લેક્ષ શબ્દનો અર્થ _____ છે.			
	A.	મેની	B.	એક પણ નહી
	C.	વન	D.	વન ઈન્ટ્રુ મેની
૬૫.	૩ ટુ ૮ ડીકોડરને _____ પણ કહે છે.			
	A.	બાઈનરી ટુ ઓક્ટલ ડીકોડર	B.	ગ્રેય કોડ કન્વર્ટર
	C.	બાઈનરી કોડ કન્વર્ટર	D.	એક પણ નહી
૬૬.	ડીકોડરનો ઉપયોગ _____ માં થાય છે.			
	A.	કાઉન્ટર સીસ્ટમ	B.	બધા
	C.	A/D કન્વર્ટર	D.	ડીસપ્લેય સીસ્ટમ ડ્રાઈવ કરવા માટે
૬૭.	કોમ્પીનેશનલ સર્કીટ એક છે કે જેમાં આઉટપુટ _____ ઉપર આધાર ધરાવે છે.			
	A.	ઈનપુટ કોમ્પીનેશન અને પાછલા આઉટપુટ	B.	હાજર આઉટપુટ અને પાછલા આઉટપુટ
	C.	તે સમયનાં ઈનપુટ કોમ્પીનેશન	D.	એક પણ નહી
૬૮.	_____ પર્ટીક્યુલર બાઈનરી શબ્દ અથવા સંખ્યા જનરેટ કરે છે.			
	A.	ડીકોડર	B.	ડીમલ્ટીપ્લેક્ષર
	C.	એનકોડર	D.	મલ્ટીપ્લેક્ષર
૬૯.	BCD સંખ્યાને ઈક્વીવેલન્ટ ડેસીમલ સંખ્યામાં બદલવા માટે _____ નો ઉપયોગ થાય છે.			
	A.	ડીકોડર	B.	ડીમલ્ટીપ્લેક્ષર
	C.	એનકોડર	D.	મલ્ટીપ્લેક્ષર
૭૦.	૧ ટુ ૮ ડીમલ્ટીપ્લેક્ષર __ સીલેક્ટ લાઈન્સ જોઈએ છે.			
	A.	૧	B.	૩
	C.	૨	D.	૪
