Seat No	·.:	Enrolment No	
	Dip	GUJARAT TECHNOLOGICAL UNIVERSITY loma Engineering – SEMESTER – II • EXAMINATION – WINTER • 2014	
Subjec	et Co	de: 320009 Date: 20-12-2014	
	10:30	me: Electrical Circuit) am - 01:00 pm Total Marks: 70	
2	 Ma Fig 	empt all questions. Aske suitable assumptions wherever necessary. A ures to the right indicate full marks. B glish version is considered to be Authentic.	
Q.1	(a)	Derive the equation for delta to star transformation. Three resistances of 40Ω , 50Ω and 60Ω are connected in star connection. Find the equivalent delta connected resistance.	07
	(b)	Explain factors affecting to the Resistance. Also give difference between emf and potential difference.	07
Q.2	(a)	Define the term:- 1. Flux density 2. MMF 3. Magnetic field strength 4. Reluctance 5. Permeability 6. Permeance 7. Reluctivity	07
	(b)	Compare Magnetic circuit with Electric circuit. OR	07
	(b)	An iron ring of 1m average diameter is made from iron of 15cm ² cross sectional area. 300 turns are wound over it. Calculate the value of current necessary to produce flux of 1.5mWb. Assume permeability of iron as 600.	07

State and Explain Dynamically induced emf and Statically induced emf.

Calculate equivalent capacitance when three capacitors of $30\mu F,\!60\mu F$ and

Expression for equation of AC current is given by $i=100\sin(2\pi 50t)$ ampere

Obtain the equation, $K = \frac{M}{\sqrt{L_1 L_2}}$ for co-Efficient of coupling.

90μF are connected in series and parallel.

Derive the formula for Energy stored in capacitor.

07

07

07

07

07

07

Q.3

Q.3

Q.4

(a)

(b)

(a)

(b)

(a)

(b)

find:

Define the terms:-

Cycle
 Frequency

Instantaneous value
 Average value
 Form Factor
 Peak Factor
 RMS Value

Maximum value

		 Frequency Angular frequency Time period 					
0.4	(-)	OR OR					
Q. 4	(a) (b)	Drive the expression of power consumption for AC through pure resistance. Explain the RC series with circuit diagram And waveform.	07 07				
Q.5	(a) (b)	Derive the expression of power consumption for AC through pure inductance. Compare series resonance with parallel resonance. OR	07 07				
Q.5	(a)	State advantage of 3phase system over 1phase system. Explain generation of 3phase voltage with waveform.	07				
	(b)	A resistance of 20Ω and an inductance of 0.2H are connected in series across 230V, 50HZ supply. Calculate:-	07				
		 Inductive reactance Impedance Current Power factor True power Reactive power Apparent power 					

ગુજરાતી

પ્રશ્ન. ૧	અ	કેલ્ટા માથી સ્ટાર ટ્રાન્સ્ફ્રૉમેશન માટેનુ સૂત્ર તરવો. 40Ω, 50Ω, અને 60Ω ના	೦೨
		ત્રણ રજીસ્ટર સ્ટારમાં કનેક્ટ કરેલા છે, તો તેના સમતુલ્ય ડેલ્ટા શોધો.	
	બ	પ્રતીરોધને અસરકર્તા પરીબળો સમજાવો. EMF અને પોટેન્શીયલ ડીફરન્સ	೦೨
		વચ્ચેના તફાવત સમજાવો.	
પ્રશ્ન. ર	અ	નીચેના પદો સમજાવો.	0.9
		ા. ફલ્ક્સ કેન્સીટી	
		2. એમ.એમ.એફ	
		3. મેગ્નેટીક ફિલ્ડ સ્ટ્રેન્થ	
		4. રીલક્ટન્સ	
		5. પરમીયાબીલીટી	
		6. પરમીથન્સ	
		7. રીલક્ટીવીટી	
	બ	ઈલેકટ્રીક સરકીટને મેગ્નેટીક સરકીટ સાથે સરખાવો.	೦೨
		અથવા	
	બ	1m એવરેજ ડાયામીટર ની આર્ચન રીંગ 15cm² ક્રોસ સેકશનલ એરીયા ધરાવે છે.	೦೨
		તેની ઉપર 300 આટા વીટડાવામાં આવે છે. 1.5mWb ફલ્ક્સ ઉત્તપન્ન કરવા માટે	
		જોયતા કરંટ ની ગણતરી કરો. આર્ચન ની પરમીયાબીલીટી 600 ધારો.	
પ્રશ્ન. ૩	અ	ડાચિનેમીક્લી ઈન્ક્યુસ્ડ EMF અન ે સ્ટેટીક્લી ઈન્ક્યુસ્ડ EMF સમજા વો.	೦೨
		કો- એફીસીયન્ટ ઓફ કપલીંગ માટેનુ $K = \frac{M}{\sqrt{L_1 L_2}}$ સૂત્ર તરવો.	0.9
		અથવા	
પ્રશ્ન. ૩	અ	30μF, 60μF અને 90μF ના ત્રણ કેપેસીટર નો સમતુલ્થ કેપેસીટન્સ સીરીઝ	೦೨
		ક્નેકશન અને પેરેલલ ક્નેકશન માટે શોધો.	
	બ	કેપેસીટર માટે એનજી સ્ટોરેજ નું સૂત્ર તારવો.	೦೨
1181 V	311	નીચેના પદો સમજાવો.	
પ્રશ્ન. ૪	અ		೦೨
		1. સાથકલ 2. ફિંક્વન્સી	,
		2. લક્કવન્સ 3. તત્જ્ઞણીક કિંમત	
		4. એવરેજ વેલ્યુ કુ કોર્ય કેલ્સ્ટ્ર	
		5. ફોર્મ ફેક્ટર . પ્રાક્ત કેલ્ટર	
		6. પીક ફેક્ટર	
		7. આર.એમ.એસ વેલ્યુ	

બ AC કરંટ માટેનુ સૂત્ર i =100sin(2π50t) એમ્પીયર છે. તો આ સૂત્ર ઉપરથી ૦૭ નીચેની કિંમત શોધો. 1. મેકસીમમ વેલ્યુ 2. ફ્રીક્વંસી 3. એન્ગ્યુલર ફ્રીક્વંસી

અથવા

પ્રશ્ન. ૪ અ શુદ્ધ પ્રતીરોધમાંથી A.C પસાર કરવાથી વપરાતા પાવરનુ સ્ત્ર તારવો. ૦૭ બ સરકિટ ડાયાગ્રામ અને વેવફોમ સાથે RC સીરીઝ સરકીટ સમજાવો. ૦૭
 પ્રશ્ન. ૫ અ શુદ્ધ ઈન્ડક્ટરમાંથી A.C પસાર કરવાથી વપરાતા પાવરનુ સ્ત્ર તારવો. ૦૭ બ સીરીઝ રેઝોનન્સ સાથે પેરેલલ રેઝોનન્સ ની સરખામણી કરો. ૦૭

અથવા

- પ્રશ્ન.૫ અ થ્રીફેઇઝ સીસ્ટમના, સિંગલ ફેઇઝ સીસ્ટમ ઉપરના ફાયદા સમજાવો. થ્રીફેઇઝ ૦૭ વોલ્ટેઝ જનરેશન વેવકોમ સાથે સમજાવો.
 - બ 20Ω નૉ પ્રતીરોધ, 0.2H નો ઈન્ડક્ટર સીરીઝમાં જોડેલ છે અને આ સીરીઝ 0.9 સરકીટને 230V, 50HZ નો સપ્લાય આપવામાં આવે તો નીચેની કિંમત શોધો.
 - ા. ઈન્ડક્ટીવ રીએક્ટન્સ

4. ટાઈમ પીરીયડ

- 2. ઈમ્પીડન્સ
- ડ. કરંટ
- 4. પાવર ફેક્ટર
- 5. ટ્રુ પાવર
- 6. રીએક્ટીવ પાવર
- 7. એપરન્ટ પાવર
