

Seat No.: _____

Enrolment No._____

GUJARAT TECHNOLOGICAL UNIVERSITY**Diploma Engineering - SEMESTER-I (CtoD) • EXAMINATION – WINTER • 2014****Subject Code: C310702****Date: 24-12-2014****Subject Name: Fundamental of Digital Electronics****Time: 10:30 am - 12:00 pm****Total Marks: 70****Instructions:**

1. Attempt all questions.
2. Make suitable assumption wherever necessary.
3. Each question is of 1 mark.
4. Use of SIMPLE CALCULATOR is permissible. (Scientific/Higher Version not allowed)
5. English version is authentic.

No.	Question Text and Option			
1.	What Radix of binary number system?			
A.	0	B.	1	
C.	2	D.	A & B	
2.	Any number with an exponent of zero is equal to:			
A.	1	B.	0	
C.	10	D.	2	
3.	What are the symbols used to represent digits in the binary number system?			
A.	0,1	B.	0 to 7	
C.	1,2	D.	0,1,2,3	
4.	A full adder circuit requires _____.			
A.	2 input and 2 output	B.	2 input and 3 output	
C.	3 input and 3 output	D.	3 input and 2 output	
5.	In positive logic, _____.			
A.	HIGH=1,LOW=0	B.	HIGH=0,LOW=1	
C.	Only High Present	D.	Only Low Present	
6.	Give the decimal value of binary 10010.			
A.	6	B.	9	
C.	18	D.	20	
7.	Convert the fractional binary number 0000.1010 to decimal.			
A.	0.625	B.	0.50	
C.	0.55	D.	0.10	
8.	How many unique symbols are used in the decimal number system?			
A.	1	B.	8	
C.	9	D.	10	
9.	Convert hexadecimal value $(16)_{16}$ to decimal.			
A.	22	B.	10	
C.	16	D.	20	
10.	One hex digit is sometimes referred to as			
A.	Byte	B.	Nibble	
C.	Grouping	D.	Instruction	
11.	Which is typically the longest: bit, byte, nibble, word?			
A.	Bit	B.	Byte	
C.	Nibble	D.	Word	
12.	Convert decimal to binary: $(32)_{10}$			
A.	100010	B.	100000	
C.	100011	D.	100001	
13.	Convert hexadecimal to binary: $(C)_{16}$			
A.	1100	B.	1000	
C.	1010	D.	1101	
14.	Convert octal number to decimal: $(17)_8$			

	A.	51	B.	82
	C.	57	D.	15
15.	How many binary digits are required to count to $(100)_{10}$?			
	A.	7	B.	2
	C.	3	D.	100
16.	What is the BCD number for decimal $(347)_{10}$?			
	A.	1100 1011 1000	B.	0011 0100 0111
	C.	0011 0100 0001	D.	1100 1011 0110
17.	What is the binary number of $(46)_8$ octal number?			
	A.	100010	B.	100110
	C.	110101	D.	100100
18.	Identify the type of gate below from the equation $Y=AB$.			
	A.	AND Gate	B.	OR Gate
	C.	NOR Gate	D.	NAND Gate
19.	Identify the type of gate below from the equation $Y=A+B$.			
	A.	AND Gate	B.	OR Gate
	C.	NOR Gate	D.	NAND Gate
20.	Which type of gate can be used to add two bits?			
	A.	Ex-OR	B.	Ex-NOR
	C.	OR	D.	NOR
21.	The Ex-NOR is sometimes called the _____.			
	A.	parity gate	B.	equality gate
	C.	inverted OR	D.	A & B
22.	A logic circuit that provides a HIGH output for both inputs HIGH or both inputs LOW is			
	A.	OR	B.	NOT
	C.	Ex-NOR	D.	NAND
23.	The output of an AND gate with three inputs, A, B, and C, is HIGH when _____.			
	A.	$A = 1, B = 1, C = 0$	B.	$A = 1, B = 0, C = 1$
	C.	$A = 0, B = 0, C = 0$	D.	$A = 1, B = 1, C = 1$
24.	The output of an OR gate with three inputs, A, B, and C, is LOW when _____.			
	A.	$A = 1, B = 1, C = 1$	B.	$A = 0, B = 1, C = 1$
	C.	$A = 0, B = 1, C = 0$	D.	$A = 0, B = 0, C = 0$
25.	Output will be a LOW for any case when one or more inputs are zero for			
	A.	NOR	B.	OR
	C.	NOT	D.	AND
26.	What is operating voltage of TTL?			
	A.	2V	B.	5V
	C.	9V	D.	12V
27.	When output of NOR gate is High?			
	A.	all inputs are LOW	B.	any input is LOW
	C.	all inputs are HIGH	D.	any input is HIGH
28.	How many input combinations would a truth table have for a 3-input AND gate?			
	A.	3	B.	8
	C.	12	D.	16
29.	What is Boolean expression of NOR gate?			
	A.	$A+B$	B.	A^*B
	C.	$(A+B)'$	D.	$(A^*B)'$
30.	What is the output of three input OR gate when $A=0, B=1, C=1$?			
	A.	0	B.	01
	C.	1	D.	10
31.	How many entries would a truth table for a four-input NAND gates have?			
	A.	4	B.	8
	C.	12	D.	16
32.	What is output of NAND gate if $A=0$ and $B=0$?			

	A.	0	B.	1
	C.	01	D.	10
33.	If a 2-input NOR gate has four input possibilities, how many of those possibilities will result in a HIGH output?			
	A.	0	B.	1
	C.	2	D.	3
34.	What is the output of Ex-NOR when A=0 and B=0?			
	A.	11	B.	0
	C.	1	D.	10
35.	A 2-input NOR gate is equivalent to a _____.			
	A.	negative-OR gate	B.	negative-NAND gate
	C.	negative-AND gate	D.	none of the above
36.	The basic logic gate whose output is the complement of the input is the:			
	A.	OR	B.	NOT
	C.	AND	D.	EX-NOR
37.	What is the sum of $11101 + 10111$?			
	A.	110011	B.	100001
	C.	110100	D.	100100
38.	What is the sum of the two BCD numbers, $0011 + 0011$?			
	A.	0110	B.	0111
	C.	0011	D.	1100
39.	Convert into hexadecimal 1100101000110101 ?			
	A.	121035	B.	CA35
	C.	53CA1	D.	3510CA
40.	Which is the $(35)_{10}$ decimal number to binary?			
	A.	10010	B.	10011
	C.	100011	D.	100010
41.	What is the BCD of decimal $(11)_{10}$?			
	A.	00000001	B.	00010000
	C.	00000011	D.	00010001
42.	A small circle on the output of a logic gate is used to represent the:			
	A.	AND operation	B.	NOT operation
	C.	Comparator operation	D.	OR operation
43.	Which of the examples below expresses the distributive law?			
	A.	$(A + B) + C = A + (B + C)$	B.	$A + (B + C) = AB + AC$
	C.	$A(B + C) = AB + AC$	D.	$A(BC) = (AB) + C$
44.	Which of the examples below expresses the associative law of addition:			
	A.	$A + (B + C) = (A + B) + C$	B.	$A + (B + C) = A + (BC)$
	C.	$A+(BC) = (AB) + C$	D.	$ABC = A + B + C$
45.	Which most commonly system used for representing signed binary numbers?			
	A.	1' compliment	B.	2' compliment
	C.	9' compliment	D.	10' compliment
46.	Major difference between Half Adder and Full Adder is:			
	A.	Full Adder is made up of 2 Half Adder	B.	Full adders can handle double-digit numbers
	C.	Half adders can handle only single-digit numbers	D.	Full adders have a carry input capability
47.	$1111 - 1100$ perform binary operation			
	A.	1	B.	11
	C.	10	D.	100
48.	Find 1'compliment of 1011001 ?			
	A.	1011000	B.	0100110
	C.	1000111	D.	0100111
49.	Give binary subtraction of 0-1 is			

	A.	Difference=1, Borrow=1	B.	Difference=0, Borrow=0
	C.	Difference=0, Borrow=1	D.	Difference=1, Borrow=0
50.	Give binary addition of $1+1+1$ is			
	A.	Sum=0, Carry=0	B.	Sum=0, Carry=1
	C.	Sum=1, Carry=0	D.	Sum=1, Carry=1
51.	The number of control line in 8 to 1 multiplexer is			
	A.	1	B.	2
	C.	3	D.	4
52.	Give the 2' compliment of the 1001.			
	A.	1000	B.	0110
	C.	1111	D.	0111
53.	The device which changes from serial data to parallel data is			
	A.	Multiplexer	B.	Demultiplexer
	C.	Counter	D.	Flip-flop
54.	A device which converts BCD to Seven Segment is called			
	A.	Encoder	B.	Multiplexer
	C.	Decoder	D.	Demultiplexer
55.	Which of following are known as universal gates			
	A.	AND & OR	B.	NAND & NOR
	C.	Ex-OR & Ex-NOR	D.	NOT & AND
56.	The number of control line in 1 to 16 demultiplexer is			
	A.	1	B.	2
	C.	3	D.	4
57.	A binary equivalent of hexadecimal number $(FF)_{16}$ is			
	A.	11111111	B.	11110000
	C.	11110001	D.	11001100
58.	Which term is Sum of Product?			
	A.	$AB+BC$	B.	$(B+C)(C+A)$
	C.	$(A+B)AB$	D.	None of these
59.	The decimal number of BCD code 10011001			
	A.	15	B.	20
	C.	99	D.	90
60.	The number of bits in nibble			
	A.	1	B.	2
	C.	3	D.	4
61.	Which term is Product of Sum?			
	A.	$XY+YZ$	B.	$(X+Y)(Y+Z)$
	C.	$X(YZ)$	D.	$X(Y+Z)+X$
62.	Convert the BCD 0001 0000 in binary.			
	A.	1010	B.	1000
	C.	1110	D.	1100
63.	The number of digit in hexadecimal number system is			
	A.	2	B.	8
	C.	16	D.	32
64.	Convert $(85)_{10}$ in to Binary Coded Decimal			
	A.	10000001	B.	10000101
	C.	01011000	D.	00011000
65.	De-Morgan's first theorem shows the equivalence of			
	A.	NOR gate and Bubbled AND gate	B.	OR gate and Exclusive OR gate.
	C.	NOR gate and NAND gate.	D.	NAND gate and NOT gate
66.	Add Hexadecimal number $(14)_{16}+(18)_{16}$			
	A.	$(25)_{16}$	B.	$(CC)_{16}$
	C.	$(2A)_{16}$	D.	$(2C)_{16}$
67.	Multiply two binary number $(1010)_2 * (11)_2$			

	A.	11110	B.	11011
	C.	10001	D.	10101
68.	When 11110 is divided by 101, what is the decimal remainder?			
	A.	1	B.	2
	C.	3	D.	0
69.	Subtract the hexadecimal number $(FA)_{16} - (2F)_{16}$			
	A.	$(CB)_{16}$	B.	$(CC)_{16}$
	C.	$(BB)_{16}$	D.	$(CD)_{16}$
70.	Which is following invalid BCD code?			
	A.	1000	B.	1001
	C.	1011	D.	0001

ગુજરાતી

નં.	પ્રશ્ન તેમજ વિકલ્પ			
1.	બાયનરી નો રેડિક્સ શું છે?			
	A.	0	B.	1
	C.	2	D.	A & B
2.	કોઇપણ નંબર નો ધાત 0 હોય તો:			
	A.	1	B.	0
	C.	10	D.	2
3.	બાયનરી નંબર સીસ્ટમ મા ડિજિટ દરશાવા માટે ક્યા સિમ્બોલ નો ઉપયોગ થાય છે?			
	A.	0,1	A.	0 થી 7
	C.	1,2	C.	0,1,2,3
4.	કુલ એડર સરકિટ મા : _____			
	A.	2 ઇનપુટ અને 2 આઉટપુટ	A.	2 ઇનપુટ અને 3 આઉટપુટ
	C.	3 ઇનપુટ અને 3 આઉટપુટ	C.	3 ઇનપુટ અને 2 આઉટપુટ
5.	પોલિટ્રિવ લોજીક મા: _____			
	A.	હાઇ = 1 ,લો = 0	B.	હાઇ = 0 ,લો = 1
	C.	બધા જા હાઇ	D.	બધા જા લો
6.	બાયનરી નંબર નો ડેસિમલ નંબર આપો: 10010			
	A.	6	B.	9
	C.	18	D.	20
7.	કનવટ્ટ ફક્સન બાયનરી નંબર નો ડેસિમલ નંબર કરો : 0000.1010			
	A.	0.625	B.	0.50
	C.	0.55	D.	0.10
8.	ડેસિમલ નંબર સીસ્ટમ મા ડિજિટ દરશાવા માટે કેટલા અલગ સિમ્બોલ નો ઉપયોગ થાય છે?			
	A.	1	B.	8
	C.	9	D.	10
9.	હેક્સાડેસિમલ નંબર માથી ડેસિમલ નંબર કરો: $(16)_{16}$			

	A.	22	B.	10
	C.	16	D.	20
10.	ઇક હેક્સ ડિજિટ કોઈકવાર આ નામે ઉપયોગ થાય છે?			
10.	A.	બાઇટ	B.	નિબ્બલ
	C.	ગૃપિગા	D.	ઇનસ્ટ્રુક્શન
11.	આમા થી શુ લાભુ હોય છે: બીટ, બાઇટ, નિબ્બલ , વડુ			
11.	A.	બીટ	B.	બાઇટ
	C.	નિબ્બલ	D.	વડુ
12.	ડેસિમલ નંબર માથી બાયનરી નંબર મા બદલો: $(32)_{10}$			
12.	A.	100010	B.	100000
	C.	100011	D.	100001
13.	હેક્સાડેસિમલ નંબર માથી બાયનરી નંબર મા બદલો: $(C.)_{16}$			
13.	A.	1100	B.	1100
	C.	1010	D.	1010
14.	ઓક્ટલ નંબર માથી ડેસિમલ નંબર મા બદલો: $(17)_8$			
14.	A.	51	B.	82
	C.	57	D.	15
15.	$(100)_{10}$ લખાવા માટે કેટલા બાયનરી ડિજિટ ની જરૂર પડે છે?			
15.	A.	7	B.	2
	C.	3	D.	100
16.	ડેસિમલ નંબર $(347)_{10}$ નો BCD નંબર ક્યો છે?			
16.	A.	1100 1011 1000	B.	0011 0100 0111
	C.	0011 0100 0001	D.	1100 1011 0110
17.	$(46)_8$ ઓક્ટલ નંબર નો બાયનરી નંબર ક્યો છે?			
17.	A.	100010	B.	100110
	C.	110101	D.	100100
18.	આ ઇક્વેશન ક્યા ગેટ નું છે તે કહો: $Y=AB$			
18.	A.	એન્ડ ગેટ	B.	ઓર ગેટ
	C.	નોર ગેટ	D.	નંડ ગેટ
19.	આ ઇક્વેશન ક્યા ગેટ નું છે તે કહો: $Y=A+B$			
19.	A.	એન્ડ ગેટ	B.	ઓર ગેટ
	C.	નોર ગેટ	D.	નંડ ગેટ
20.	ક્યો ગેટ 2 બાયનરી નંબર ને સરવાળો કરવા માટે ઉપયોગ થાય છે?			
20.	A.	એક્સ - ઓર	B.	એક્સ- નોર

	C.	ઓર	D.	નોર
21.	એક્સ - ઓર ગેઇટ કોઇવાર આ નામે ઓળખાય છે.			
	A.	પરિટી ગેઇટ	B.	ઇકવાલિટી ગેઇટ
	C.	ઇનવેટ ઓર	D.	A & B
22.	ક્યો ગેઇટ આઉટપુટ હાઇ આવે, જ્યારે બજે ઇનપુટ હાઇ અથવા લો હોય...			
	A.	ઓર	B.	નોર
	C.	એક્સ - ઓર	D.	નંદ
23.	3 ઇનપુટ વાળા એન્ડ ગેઇટ નો આઉટપુટ હાઇ ક્યારે આવે: A,B,C,			
	A.	A = 1, B = 1, C = 0	B.	A = 1, B = 0, C = 1
	C.	A = 0, B = 0, C = 0	D.	A = 1, B = 1, C = 1
24.	3 ઇનપુટ વાળા ઓર ગેઇટ નો આઉટપુટ લો ક્યારે આવે: A,B,C,			
	A.	A = 0, B = 1, C = 1	B.	A = 0, B = 1, C = 1
	C.	A = 0, B = 1, C = 0	D.	A = 0, B = 0, C = 0
25.	એક અથવા વધારે ઇનપુટ 0 હોય તો ક્યા ગેઇટ મા આઉટપુટ લો આવે			
	A.	નોર	B.	ઓર
	C.	નોટ	D.	એન્ડ
26.	TTL ના ઓપરેટિંગ વોલ્ટેજ કેટલા છે?			
	A.	2V	B.	5V
	C.	9V	D.	12V
27.	ક્યારે નોર ગેઇટ નો આઉટપુટ હાય આવે?			
	A.	બધા ઇનપુટ લો	B.	કોઇ ઇનપુટ લો
	C.	બધા ઇનપુટ હાય	D.	કોઇ ઇનપુટ હાય
28.	3 ઇનપુટ વાળા એન્ડ ગેઇટ ના દ્વથ ટેબલ મા કેટલી ઇનપુટ કોમ્બિનેશન હોય છે?			
	A.	3	B.	8
	C.	12	D.	16
29.	નોર ગેઇટ નું બુલિયન શુ હોય છે?			
	A.	A+B	B.	A*B
	C.	(A+B)'	D.	(A*B)'
30.	3 ઇનપુટ વાળા ઓર ગેઇટ મા A=0,B=1,C=1 ઇનપુટ હોય તો આઉટપુટ શુ હોય?			
	A.	0	B.	01
	C.	1	D.	10
31.	4 ઇનપુટ વાળા નંદ ગેઇટ ના દ્વથ ટેબલ મા કેટલી એન્ડ હોય છે?			
	A.	4	B.	8
	C.	12	D.	16

	નંદ ગેઇટ નો આઉટપુટ જ્યારે ,A=0 અને B=0 શું હોય?			
32.	A.	0	B.	1
	C.	01	D.	10
33.	2 ઇનપુટ વાળા નોર ગેઇટ મા 4 પોસીબલ ઇનપુટ હોય તો, આઉટપુટ મા હાય કેટલી વખત આવે?			
	A.	0	B.	1
	C.	2	D.	3
34.	એક્સ- નોર ગેઇટ નો આઉટપુટ જ્યારે ,A=0 અને B=0 શું હોય?			
	A.	11	B.	0
	C.	1	D.	10
35.	2 ઇનપુટ વાળા નોર ગેઇટ કોણા બરાબર છે?			
	A.	નેગે ટિવ ઓર ગેઇટ	B.	નેગે ટિવ નંદ ગેઇટ
	C.	નેગે ટિવ એંડ ગેઇટ	D.	એક્પન નહિ
36.	ક્યા બેઝિક લોજીક ગેઇટ નો આઉટપુટ કોમ્પિમેન્ટ હોય છે?			
	A.	ઓર	B.	નોટ
	C.	એંડ	D.	એક્સ-નોર
37.	11101 + 10111 નો સરવાળો શું હોય?			
	A.	110011	B.	100001
	C.	110100	D.	100100
38.	BCD નંબર નો સરવાળો કરો: 0011 + 0011			
	A.	0110	B.	0111
	C.	0011	D.	1100
39.	હેક્સાડેસિમલ નંબર મા બદલો: 1100101000110101			
	A.	121035	B.	CA35
	C.	53CA1	D.	3510CA
40.	$(35)_{10}$ ડેસિમલ નંબર નો બાયનરી નંબર ક્યો છે?			
	A.	10010	B.	10011
	C.	100011	D.	100010
41.	ડેસિમલ નંબર $(11)_{10}$ નો BCD શું હોય?			
	A.	00000001	B.	00010000
	C.	00000011	D.	00010001
42.	લોજીક ગેઇટ ની આગામ નાનુ વતૃળ શું સુચવે છે:			
	A.	એંડ ઓપરેશન	B.	નોટ ઓપરેશન
	C.	ક્રેપેરિટર ઓપરેશન	D.	ઓર ઓપરેશન

	નીચે ના માથી ક્યો ઉદાહરણ ડિસ્ટિબિવ લો બતાવે છે?			
43.	A.	$(A + B) + C = A + (B + C)$	B.	$A + (B + C) = AB + AC$
	C.	$A(B + C) = AB + AC$	D.	$A(BC) = (AB) + C$
	નીચે ના માથી ક્યો ઉદાહરણ એસોસિએટ લો બતાવે છે?			
44.	A.	$A + (B + C) = (A + B) + C$	B.	$A + (B + C) = A + (BC)$
	C.	$A+(BC) = (AB) + C$	D.	$ABC = A + B + C$
	સાઇન નંબર ને દરશાવા માટે કઈ સિસ્ટમ વધુ ઉપયોગ મા લેવાય છે?			
45.	A.	1' કોમ્પ્યુમેન્ટ	B.	2' કોમ્પ્યુમેન્ટ
	C.	9' કોમ્પ્યુમેન્ટ	D.	10' કોમ્પ્યુમેન્ટ
	હાફ એડર અને કુલ એડર વચ્ચે નો મોટો તફાવત શું છે?			
46.	A.	2 હાફ એડર નો ઉપયોગ થી કુલ એડર.	B.	કુલ એડર 2 ડિજિટ હેન્ડલ કરે છે.
	C.	હાફ એડર 1 ડિજિટ હેન્ડલ કરે છે.	D.	કુલ એડર કેરી ઇનપુટ કેપેસિટી છે.
	બાયનરી ઓપરેશન કરો: 1111 – 1100			
47.	A.	1	B.	11
	C.	10	D.	100
	1' કોમ્પ્યુમેન્ટ શોધો: 1011001			
48.	A.	1011000	B.	0100110
	C.	1000111	D.	0100111
	બાયનરી બાદબક્રિ કરો: 0 - 1			
49.	A.	ડિફરન્સ= 1, બોરો= 1	B.	ડિફરન્સ= 0, બોરો= 0
	C.	ડિફરન્સ= 0, બોરો= 1	D.	ડિફરન્સ= 1, બોરો= 0
	બાયનરી સરવાળો કરો: 1 + 1 + 1			
50.	A.	સમ = 0, કેરી= 0	B.	સમ = 0, કેરી= 1
	C.	સમ = 1, કેરી= 0	D.	સમ = 1, કેરી= 1
	8 થી 1 મલ્ટિપ્લેક્સર મા કેટલી કંટોલ લાઇન હોય છે?			
51.	A.	1	B.	2
	C.	3	D.	4
	2' કોમ્પ્યુમેન્ટ આપો: 1001			
52.	A.	1000	B.	0110
	C.	1111	D.	0111
	ક્યુ સાધન સિરીયલ ડેટા માથી પેરેલલ ડેટામા ફેરવે છે?			
53.	A.	મલ્ટિપ્લેક્સર	B.	ડિમલ્ટિપ્લેક્સર

	C.	કાન્ટર	D.	ડિલ્યુ- ફ્લોપ
54.	ક્યુ સાધન BCD માથી સેવન સેગમેન્ટ ફેરવે છે?			
	A.	એનકોડર	B.	માલ્ટિપ્લેક્સર
	C.	ડિકોડર	D.	ડિમાલ્ટિપ્લેક્સર
55.	યુનિવરસલ ગેઇટ તરિકે ઓળખાય છે.			
	A.	એન્ડ અને ઓર	B.	નંદ અને નોર
	C.	એક્સ-ઓર અને એક્સ- નોર	D.	નોટ અને એન્ડ
56.	1 થી 16 ડિમાલ્ટિપ્લેક્સર મા કેટલી કંટૈલ લાઇન હોય છે?			
	A.	1	B.	2
	C.	3	D.	4
57.	બાયનરી નંબર આપો: $(FF)_{16}$			
	A.	11111111	B.	11110000
	C.	11110001	D.	11001100
58.	કઈ ટુમ સમ ઓફ પ્રોડક્ટ છે?			
	A.	$AB+BC$	B.	$(B+C)(C+A)$
	C.	$(A+B)AB$	D.	એક પન નહિ
59.	BCD 10011001 ને ડેસિમલ મા બતાવો.			
	A.	15	B.	20
	C.	99	D.	90
60.	નિયબલ મા કેટલા બિટ હોય છે.			
	A.	1	B.	2
	C.	3	D.	4
61.	કઈ ટુમ પ્રોડક્ટ ઓફ સમ છે?			
	A.	$XY+YZ$	B.	$(X+Y)(Y+Z)$
	C.	$X(YZ)$	D.	$X(Y+Z)+X$
62.	BCD 0001 0000 ને બાયનરી મા બદલો:			
	A.	1010	B.	1000
	C.	1110	D.	1100
63.	હેક્સાડેસિમલ નંબર સિસ્ટમ મા કેટલા ડિજિટ હોય છે?			
	A.	2	B.	8
	C.	16	D.	32
64.	$(85)_{10}$ ને BCD બદલો:			
	A.	10000001	B.	10000101
	C.	01011000	D.	00011000

	ડિ મોરગન નો પહેલો શીયરમ સમાનતા બતાવે છે.			
65.	A.	નોર ગેઇટ અને બબલ એંડ ગેઇટ	B.	ઓર ગેઇટ અને એક્સ - ઓર ગેઇટ
	C.	નોર ગેઇટ અને નંદ ગેઇટ	D.	નંદ ગેઇટ અને નોર ગેઇટ
66.	સરવાળો કરો: $(14)_{16} + (18)_{16}$			
67.	A.	$(25)_{16}$	B.	$(CC)_{16}$
	C.	$(2A)_{16}$	D.	$(2C)_{16}$
68.	બાયનરી ગુનાકાર કરો : $(1010)_2 * (11)_2$			
69.	A.	11110	B.	11011
	C.	10001	D.	10101
70.	11110 ને 101 વડે ભાગવાથી કેટલા વધે છે?			
70.	A.	1	B.	2
	C.	3	D.	0
69.	હેએક્સાડેસિમલ બાદબાકી કરો : $(FA)_{16} - (2F)_{16}$			
70.	A.	$(CB)_{16}$	B.	$(CC)_{16}$
	C.	$(BB)_{16}$	D.	$(CD)_{16}$
70.	નીચે માથી કયો કોડ BCD નથી?			
70.	A.	1000	B.	1001
	C.	1011	D.	0001
