

Seat No.: _____


Enrolment No. _____

GUJARAT TECHNOLOGICAL UNIVERSITY**Diploma Engineering - SEMESTER-I (CtoD) • EXAMINATION – WINTER • 2014****Subject Code: C321102****Date: 29-12-2014****Subject Name: Electronic Network****Time: 10:30 am – 12:00 pm****Total Marks: 70****Instructions:**

1. Attempt all questions.
2. Make suitable assumption wherever necessary.
3. Each question is of 1 mark.
4. Use of SIMPLE CALCULATOR is permissible. (Scientific/Higher Version not allowed)
5. English version is authentic.


| No. | Question Text and Option | | | |
|-----|---|--|----|---|
| 1. | A branch is said to be active when it contains | | | |
| | A. | An energy source | B. | Resistor |
| | C. | Inductor | D. | Capacitor |
| 2. | A circuit is said to be linear when the current voltage relationship can be expressed by linear | | | |
| | A. | Algebraic equations | B. | Differential equations |
| | C. | Integral equations | D. | All of these |
| 3. | Which of the following is not a characteristic of an independent voltage source? | | | |
| | A. | Voltage independent of magnitude of current drawn | B. | Voltage dependent on magnitude of current drawn |
| | C. | Independent of direction of current flow | D. | Can supply or receive uninterrupted energy at constant voltage |
| 4. | A practical voltage source can be represented by | | | |
| | A. | An ideal voltage source with its internal resistance connected in series | B. | An ideal voltage source with its internal resistance connected across its terminals |
| | C. | By neglecting the internal resistance | D. | None of these |
| 5. | The two resistances of 5Ω and 20Ω are connected in parallel. The parallel combination is connected in series with 1Ω resistance and this series parallel combination connected across DC source of 50 V. The current in 20Ω resistor is | | | |
| | A. | 10 A | B. | 8A |
| | C. | 2 A | D. | None of these |
| 6. | Star to Delta and vice-versa transformations are employed to simplify circuit elements connected in | | | |
| | A. | Series-parallel | B. | Series |
| | C. | Parallel | D. | None of these |
| 7. | Which of the following is not a bilateral element? | | | |
| | A. | Transistor | B. | Resistor |
| | C. | Inductor | D. | Capacitor |
| 8. | In order to analyses of two-port network which of the following is the essential combination? | | | |
| | A. | Four independent variable and four parameters | B. | Four independent variable and two parameters |
| | C. | Two independent variable and four parameters | D. | None of these |
| 9. | Why do we say the "voltage across" or "the voltage with respect to?" Why can't we just say voltage? | | | |

| | | | | |
|-----|---|--|----|--|
| | A. | Voltage is a measure of Electric Potential difference between two electrical points. | B. | It's an Electrical 'Cliche'. |
| | C. | The other point could be Negative or positive. | D. | None of the above. |
| 10. | In a two port network, the ratio of change of input voltage to the change of input currents with output shorted, is called | | | |
| | A. | forward current gain | B. | input impedance |
| | C. | output admittance | D. | short circuit gain |
| 11. | A 5k Ω resistor is connected across 50V supply. The power consumed by the resistor is | | | |
| | A. | 1000mW | B. | 500mW |
| | C. | 250mW | D. | 10mW |
| 12. | A 16 W resistor has maximum current rating of 400 mA. What is the maximum current rating if the power rating of the resistor is limited to 1 W? | | | |
| | A. | 400 mA | B. | 300 mA |
| | C. | 200 mA | D. | 100mA |
| 13. | Characteristic impedance of the π network is | | | |
| | A. | = characteristic impedance of T network | B. | \neq characteristic impedance of T network |
| | C. | = $Z_1 * Z_2 /$ characteristic impedance of T network | D. | None of these |
| 14. | The two laws which form basis of circuit analysis were stated by | | | |
| | A. | Bohr | B. | Ohm |
| | C. | Kirchhoff's | C. | Faraday |
| 15. | How many branches can be connected to the node? | | | |
| | A. | 1 | B. | 2 |
| | C. | 3 | C. | Any number |
| 16. | The development of nodal equations is based on | | | |
| | A. | KVL | B. | KCL |
| | C. | Ohm's law | C. | All these |
| 17. | The nodal analysis technique will be applicable when a circuit containing | | | |
| | A. | Current source | B. | Current and voltage source |
| | C. | Dependent source | D. | All of these |
| 18. | In the mesh analysis technique the independent variable is | | | |
| | A. | Node currents | B. | Mesh currents |
| | C. | Branch currents | D. | Node voltages |
| 19. | When branch is removed from the mesh | | | |
| | A. | Flow of current is unaffected | B. | Open circuits occurs |
| | C. | Short circuit occurs | C. | None of these |
| 20. | While Thevenising a circuit between two terminals, Thevenin voltage equals | | | |
| | A. | short circuit terminal voltage | B. | open circuit terminal voltage |
| | C. | e.m.f. of batter nearest to the terminals | D. | net voltage available in the circuit |
| 21. | Thevenin's theorem can be applied to | | | |
| | A. | d.c. circuits only | B. | a.c. circuits only |
| | C. | both d.c. and a.c. circuits | C. | none of these |
| 22. | Short - circuit current flows through a load of | | | |
| | A. | infinite impedance | B. | zero impedance |
| | C. | capacitive impedance | D. | inductive impedance |
| 23. | Open circuit voltage is the p.d between two points, having | | | |
| | A. | zero impedance | B. | finite impedance |
| | C. | infinite impedance | C. | reactive impedance |
| 24. | Thevenin's equivalent of a circuit consists of | | | |
| | A. | a single current source and a single voltage source | B. | voltage source with a series resistance |
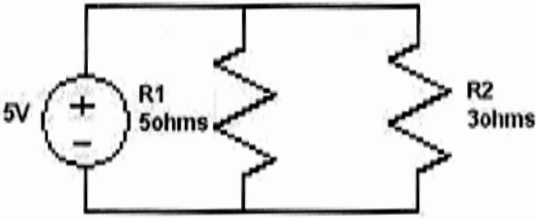
| | | | | |
|-----|---|---|----|---|
| | C. | current source with a parallel resistance | D. | voltage source with a parallel resistance |
| 25. | Norton's equivalent of a circuit consists of | | | |
| | A. | ideal voltage source and a parallel resistor | B. | ideal current source and a parallel resistor |
| | C. | ideal voltage source and a series resistor | D. | ideal current source and a series resistor |
| 26. | Superposition theorem is not applicable to networks having | | | |
| | A. | linear elements | B. | non linear elements |
| | C. | dependent current source | D. | transformer |
| 27. | A network is linear if | | | |
| | A. | response proportional to excitation function | B. | principle of superposition applies |
| | C. | principle of homogeneity applies | D. | both b and c |
| 28. | Which of the following statements is False? | | | |
| | A. | Nodal & Mesh Analysis are only used for Linear circuits | B. |) Kramers rule is used in solving Nodal Analysis Problems |
| | C. | Gaussian Method can be used to solve Nodal analysis problems | D. | Nodal Analysis can be used to verify any Mesh analysis problem |
| 29. | What is the significance of a negative (-) sign from a calculation when solving circuit problems? | | | |
| | A. | None | B. | It means you did something wrong on your calculation |
| | C. | Real resulting current or Voltage is in the opposite direction to one assumed | D. | You probably used a smaller scaling factor |
| 30. | The dynamic impedance of a parallel RLC circuit at resonance is | | | |
| | A. | C/LR | B. | LC/R |
| | C. | L/CR | D. | R/LC |
| 31. | The voltage across two resistors in series is 10 volts. One resistor is twice as large as the other. What is the voltage across the larger resistor | | | |
| | A. | $V(\text{small resistor})=5V$ and $V(\text{big resistor})=5V$. | B. | $V(\text{small resistor})=6.67V$ and $V(\text{big resistor})=3.33V$. |
| | C. | $V(\text{small resistor})=3.33V$ and $V(\text{big resistor})=6.67$. | C. | None of the above. |
| 32. | A 1 ohm, 2 ohm, and 3 ohm resistor are connected in parallel. What is the total resistance? | | | |
| | A. | $6/3 \Omega$ | B. | $3/6 \Omega$ |
| | C. | $11/6 \Omega$ | D. | $6/11 \Omega$ |
| 33. |  | | | |
| | What is the current through R1 and R2 in the diagram? | | | |
| | A. | $I_1=1A$ and $I_2=25A$ | B. | $I_1=0.1A$ and $I_2=0.1667A$ |
| | C. | $I_1=1A$ and $I_2=1.667A$ | D. | $I_1=10A$ and $I_2=16.67A$ |
| 34. | Two resistors are in parallel with a voltage source. How do their voltages compare? | | | |
| | A. | The voltage across both resistors | B. | The voltage across both resistors is half |

| | | | | |
|-----|----|---|----|--|
| | | is the same as the source | | the voltage of the source. |
| | C. | One has full voltage, the other has none. | D. | None of the above. |
| 35. | | Maximum power transfer takes place when load impedance is | | |
| | A. | Equal to the complex conjugate of source impedance | B. | Equal to the source impedance |
| | C. | Both A and B are true | D. | None of these |
| 36. | | What is the total reactance of series RLC circuit at resonance? | | |
| | A. | Equal to X_L | B. | Equal to X_C |
| | C. | Equal to R | D. | Zero |
| 37. | | What is the phase angle of series RLC circuit at resonance? | | |
| | A. | Zero | B. | 90° |
| | C. | 45° | D. | 30° |
| 38. | | In series RLC circuit of $L=15\text{mH}$, $C=0.015\mu\text{F}$ and $R=80\Omega$. What is the impedance at resonance frequency? | | |
| | A. | $15\text{mH} \cdot \omega$ | B. | $0.015\text{F} \cdot \omega$ |
| | C. | 80Ω | D. | $1/(\omega \cdot 0.015)$ |
| 39. | | In series RLC circuit operating below the resonance frequency, the current | | |
| | A. | I leads V_s | B. | I lags behind V_s |
| | C. | I is in phase with V_s | D. | None of these |
| 40. | | In series RLC circuit if C increases what happens to the resonance frequency? | | |
| | A. | It increase | B. | It decreases |
| | C. | It remains the same | D. | It is zero |
| 41. | | In a certain series resonance circuit $V_C=150\text{V}$, $V_L=150\text{V}$ and $V_R=50\text{V}$. What is the value of source voltage? | | |
| | A. | Zero | B. | 50V |
| | C. | 150V | D. | 200V |
| 42. | | A series RLC circuit has a bandwidth of 1000Hz . If the existing coil is replaced by a coil with lower Q , what happen to the bandwidth? | | |
| | A. | It increase | B. | It decrease |
| | C. | It is zero | D. | It remains the same. |
| 43. | | In the parallel resonance circuit why the current does lags behind the source voltage at the frequency below resonance? | | |
| | A. | Because the circuit is predominantly resistive | B. | Because the circuit is predominantly inductive |
| | C. | Because the circuit is predominantly capacitive | D. | None of the above |
| 44. | | All the flux produced by one coil link with other coil when coefficient of coupling | | |
| | A. | $K=0$ | B. | $K=1$ |
| | C. | $0 < K < 1$ | D. | All of these |
| 45. | | What is the impedance of an ideal parallel resonance circuit without resistance in the either branch? | | |
| | A. | Zero | B. | Inductive |
| | C. | Capacitive | D. | infinite |
| 46. | | If the lower cut-off frequency is 2400Hz and higher cut-off frequency is 2800Hz . What is the bandwidth? | | |
| | A. | 400Hz | B. | 2800Hz |
| | C. | 2400Hz | D. | 5200Hz |
| 47. | | Resonance frequency of series RLC circuit and parallel RLC circuit will be same when | | |
| | A. | $Q \gg 10$ | B. | $Q \ll 10$ |
| | C. | $Q=1$ | D. | None of these |
| 48. | | A transformer has | | |
| | A. | primary and secondary windings, both of which are considered inputs | B. | primary and secondary windings, both of which are considered outputs |

| | | | | |
|-----|---|--|----|--|
| | C. | a primary winding used as an output and a secondary winding used as an input | D. | a primary winding used as an input and a secondary winding used as an output |
| 49. | If α is attenuation in nepers then | | | |
| | A. | attenuation in dB = $\alpha / 0.8686$. | B. | attenuation in dB = 8.686α |
| | C. | attenuation in dB = 0.1α . | D. | attenuation in dB = 0.01α . |
| 50. | An attenuator is a | | | |
| | A. | R's network. | B. | RL network. |
| | C. | RC network. | D. | LC network. |
| 51. | The purpose of an Attenuator is to: | | | |
| | A. | Increase signal strength. | B. | Provide impedance matching. |
| | C. | Decrease reflections. | D. | Decrease value of signal strength. |
| 52. | In a symmetrical T attenuator with attenuation N and characteristic impedance R_0 , the resistance of each shunt arm is equal to | | | |
| | A. | R_0 | B. | $\frac{2N}{N^2 - 1} R_0$ |
| | C. | $(N-1)R_0$ | D. | $\frac{N}{N^2 - 1} R_0$ |
| 53. | In a symmetrical π attenuator with attenuation N and characteristic impedance R_0 , the resistance of each shunt arm is equal to | | | |
| | A. | R_0 | B. | $(N-1)R_0$ |
| | C. | $\frac{N-1}{N+1} R_0$ | D. | $\frac{N+1}{N-1} R_0$ |
| 54. | One neper is equal to | | | |
| | A. | 0.8686 dB | B. | 8.686 dB |
| | C. | 0.1152 dB | D. | 86.86 dB |
| 55. | Symmetrical attenuators have ' N ' = $V_1/V_2 = I_1/I_2$ given by | | | |
| | A. | Antilog(dB/20) | B. | 20log(dB/20) |
| | C. | Antilog(20/dB) | D. | None of these |
| 56. | If f_1 and f_2 are half power frequencies and f_0 is the resonance frequency, the selectivity of RLC circuit is given by | | | |
| | A. | $f_2 - f_1 / f_0$ | B. | $f_2 - f_1 / 2f_0$ |
| | C. | $f_2 - f_1 / f_1 - f_0$ | C. | $f_2 - f_0 / f_1 - f_0$ |
| 57. | The unit of admittance of network is | | | |
| | A. | ohm | B. | henry |
| | C. | ampere | D. | mho |
| 58. | Active filter circuit contains | | | |
| | A. | Resistors, inductors and capacitors only | B. | Resistors, inductors, capacitors and op-amp |
| | C. | Only resistors and capacitors | C. | All of above |
| 59. | On the basis of frequency characteristics filter can be define as | | | |
| | A. | Low pass, high pass, band pass and band stop | B. | Active filter and passive filter |
| | C. | T filter and π filter | D. | None of these |
| 60. | An ideal filter should have | | | |
| | A. | Zero attenuation in the pass band. | B. | Zero attenuation in the attenuation band. |
| | C. | Infinite attenuation in the pass band. | D. | None of these |
| 61. | For an m-derived high pass filter, the cut off frequency is 4KHz and the filter has an infinite attenuation at 3.6 KHz, the value of m is | | | |
| | A. | 0.436 | B. | 4.36 |
| | C. | 0.34 | D. | 0.6 |
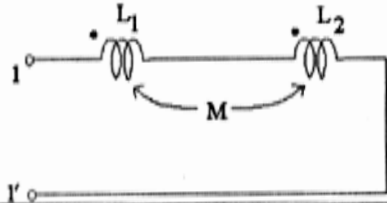
| | | | | |
|-----|--|---|----|--|
| 62. | The frequency of infinite attenuation $f(\infty)$ of a low pass m-derived section is | | | |
| | A. | Equal to cut off frequency $f(c)$ of the filter. | B. | $f(\infty) = \infty$. |
| | C. | Close to but greater than the $f(c)$ of the filter. | D. | Close to but less than the $f(c)$ of the filter. |
| 63. | A constant k low pass T-section filter has $Z_0 = 600\Omega$ at zero frequency. At $f = f_c$ the characteristic impedance is | | | |
| | A. | 600Ω | B. | 0 |
| | C. | ∞ | C. | More than 600Ω |
| 64. | In the m-derived HPF, the resonant frequency is to be chosen so that it is | | | |
| | A. | Above the cut-off frequency. | B. | Below the cut-off frequency. |
| | C. | Equal to the cut-off frequency. | D. | None of these. |
| 65. | In constant k type filter value of k is | | | |
| | A. | $\sqrt{L/R}$ | B. | $\sqrt{L/C}$ |
| | C. | $(\omega L/C)$ | C. | None of these |
| 66. | A $3-4j$ is the source impedance. For maximum power to be transfer the load impedance must be equal to | | | |
| | A. | $3-4j\Omega$ | B. | $3-5j\Omega$ |
| | C. | $3+4j\Omega$ | C. | None of these |
| 67. | All pass filter | | | |
| | A. | Passes whole of the audio band. | B. | Passes whole of the radio band. |
| | C. | Passes all frequencies with very low attenuation. | D. | Passes all frequencies without attenuation but phase is changed. |
| 68. | A delta connection contains three impedances of 60Ω each. The impedances of equivalent star connection will be | | | |
| | A. | 15Ω each. | B. | 20Ω each. |
| | C. | 30Ω each. | D. | 40Ω each. |
| 69. | The equivalent inductance of Fig at terminals 1 1' is equal to | | | |
| |  | | | |
| | A. | L_1+L_2+2M | B. | L_1+L_2-2M |
| | C. | L_1+L_2 | D. | L_1-L_2+2M |
| 70. | The following constitutes a bilateral element | | | |
| | A. | A resistor. | B. | FET. |
| | C. | Vacuum tube. | D. | Metal rectifier. |


ગુજરાતી

| | | | | |
|-----|---|-----------------|----|-------------------|
| નં. | પ્રશ્ન તેમજ વિકલ્પ | | | |
| ૧. | બ્રાંચ ને એક્ટીવ કહેવાય જ્યારે તે ધરાવતી હોય | | | |
| | A. | એનર્જી સોર્સ | B. | રેજીસ્ટર |
| | C. | ઇન્ડક્ટર | D. | કેપેસિટર |
| ૨. | કોઇ સર્કીટ ને લીનીઅર કહેવાય જ્યારે તેના વોલ્ટેજ કરંન્ટ રીલેસનસીપ ને રજૂઆત કરવા માટે વાપરવા માં આવે લીનીઅર | | | |
| | A. | એલજેબ્રીક સૂત્ર | B. | ડિફ્રન્સીઅલ સૂત્ર |

| | | | | |
|----|--|---|----|--|
| | C. | ઇન્ટીજરલ સૂત્ર | D. | અહીં આપેલા બધાજ |
| | નીચે ની કઇ લાક્ષણિકતા ઇન્કીપેન્ડેન્ટ વોલ્ટેજ સોર્સ ની નથી. | | | |
| ૩. | A. | વોલ્ટેજ, કરંટ ના મેગનીટ્યૂડ થી ઇન્કીપેન્ડેન્ટ | B. | વોલ્ટેજ, કરંટ ના મેગનીટ્યૂડ થી ડીપેન્ડેન્ટ |
| | C. | વોલ્ટેજ, કરંટ ની દિશા થી ઇન્કીપેન્ડેન્ટ | D. | કોન્સ્ટન્ટ વોલ્ટેજ સાથે અને ઇન્ટરેપ્ટેડ એનર્જી આપી શકે અને લઇ શકે, |
| | એક પ્રેક્ટીકલ વોલ્ટેજ સોર્સ એટલે | | | |
| ૪. | A. | આઇડીઅલ વોલ્ટેજ સોર્સ અને સીરીઝ માં જોડેલો ઇન્ટરનલ રેજીસ્ટર | B. | આઇડીઅલ વોલ્ટેજ સોર્સ અને પેરેલેલ માં જોડેલો ઇન્ટરનલ રેજીસ્ટર |
| | C. | ઇન્ટરનલ રેજીસ્ટર નીગલેક્ટ કરી ને | D. | અહીં આપેલા એક પણ નહીં. |
| ૫. | બે રેજીસ્ટર 5Ω અને 20Ω પેરેલેલ માં જોડેલા છે. એ બંને સીરીઝ માં 1Ω ના રેજીસ્ટર સાથે અને 50 V સપ્લાઇ સાથે જોડેલા છે. તો 20Ω ના રેજીસ્ટર માંથી પસાર થતો કરંટ | | | |
| | A. | 10 A | B. | 8 A |
| | C. | 2 A | D. | અહીં આપેલા એક પણ નહીં. |
| ૬. | સ્ટાર અને ડેલ્ટા ટ્રાન્સફોરમેસન અને તેનું ઉલટ્ટ એ સર્કીટ માં કરવામા આવે જેમાં સર્કીટ એલીમેન્ટ કનેક્ટેડ હોઇ | | | |
| | A. | સીરીઝ- પેરેલેલ માં | B. | સીરીઝ માં |
| | C. | પેરેલેલ માં | D. | અહીં આપેલા એક પણ નહીં. |
| ૭. | નીચે આપેલ કયો સર્કીટ એલીમેન્ટ બાઇલેટરલ નથી? | | | |
| | A. | ટ્રાન્ઝીસ્ટર | B. | રેજીસ્ટર |
| | C. | ઇન્ડક્ટર | D. | કેપેસિટર |
| ૮. | ટ્રાન્સ-પોર્ટ નેટવર્ક ના એનાલીસીસ માટે કયું કોમ્પીનેસન જરૂરી છે? | | | |
| | A. | ચાર ઇન્કીપેન્ડેન્ટ વેરીએબલ અને ચાર પેરામીટર | B. | ચાર ઇન્કીપેન્ડેન્ટ વેરીએબલ અને બે પેરામીટર |
| | C. | બે ઇન્કીપેન્ડેન્ટ વેરીએબલ અને ચાર પેરામીટર | D. | અહીં આપેલા એક પણ નહીં. |
| ૯. | આપણે "વોલ્ટેજ એકોસ" કે પછી "વોલ્ટેજ વીથ રીસપેક્ટ ટુ" કેમ કહીએ છીએ? ખાલી વોલ્ટેજ કેમ ના કહેવાય? | | | |
| | A. | વોલ્ટેજ એ બે ઇલેક્ટ્રીક પોઇન્ટ વચ્ચે નૂ પોટેન્સીઅલ ડિફરન્સ છે | B. | એ એક ઇલેક્ટ્રીક 'ક્લોય' છે. |
| | C. | બીજો પોઇન્ટ નેગેટીવ કે | D. | અહીં આપેલા એક પણ નહીં. |

| | | | | |
|-----|----|---|----|--|
| | | પોઝીટીવ હોઇ શકે. | | |
| ૧૦. | | દૂ-પોર્ટ નેટવર્ક માં, બદલતા વોલ્ટેજ અને બદલતા કરંટ ના ભાગાકારને કહેવાય... | | |
| | A. | ફોરવર્ડ કરંટ ગેઇન | B. | ઇનપૂટ ઇમ્પીડન્સ |
| | C. | આઉટપૂટ ઇમ્પીડન્સ | D. | સોર્ટ સર્કીટ કરંટ ગેઇન |
| ૧૧. | | $5k\Omega$ નો રેજીસ્ટર 50 V સપ્લાઇ સાથે જોડેલો છે. રેજીસ્ટર દ્વારા વપરાતો પાવર..... | | |
| | A. | 1000mW | B. | 500mW |
| | C. | 250mW | D. | 10mW |
| ૧૨. | | A 16 W ના રેજીસ્ટર નો કરંટ રેટીંગ 400 mA છે. જો પાવર રેટીંગ 1 W હોય તો કરંટ રેટીંગ કેટલો મળે? | | |
| | A. | 400 mA | B. | 300 mA |
| | C. | 200 mA | D. | 100mA |
| ૧૩. | | π નેટવર્ક નો કેરેક્ટરીસ્ટીક ઇમ્પીડન્સ | | |
| | A. | $= T$ નેટવર્ક નો કેરેક્ટરીસ્ટીક ઇમ્પીડન્સ | B. | $\neq T$ નેટવર્ક નો કેરેક્ટરીસ્ટીક ઇમ્પીડન્સ |
| | C. | $= Z1 * Z2 / T$ નેટવર્ક નો કેરેક્ટરીસ્ટીક ઇમ્પીડન્સ | D. | અહીં આપેલા એક પણ નહીં. |
| ૧૪. | | બે નીચમ જે સર્કીટ એનલીસીસ માટે બનાવાયેલ છે..... | | |
| | A. | બોહર નો | B. | ઓહમ નો |
| | C. | કિર્ચોફ નો | D. | કેરાડે નો |
| ૧૫. | | નોડ સાથે કેટલી બ્રાંચ જોડાયેલ હોય છે? | | |
| | A. | 1 | B. | 2 |
| | C. | 3 | D. | કેટલી પણ |
| ૧૬. | | નોડલ સૂત્ર બનાવવા માટે જરૂર પડે છે... | | |
| | A. | KVL | B. | KCL |
| | C. | ઓહમ નો નીયમ | D. | અહીં આપેલા બધાજ |
| ૧૭. | | નોડલ એનલીસીસ ટેકનીક નો ત્યારે ઉપયોગ થાય જ્યારે સર્કીટ માં | | |
| | A. | કરંટ સોર્સ હોય | B. | કરંટ સોર્સ અને વોલ્ટેજ સોર્સ હોય |
| | C. | ડિપેન્ડેન્ટ સોર્સ હોય | D. | અહીં આપેલા બધાજ |
| ૧૮. | | મેસ એનલીસીસ માં ઇન્ડિપેન્ડેન્ટ વેરીએબલ હોય છે..... | | |
| | A. | નોડ કરંટ | B. | મેસ કરંટ |
| | C. | બ્રાંચ કરંટ | D. | નોડ વોલ્ટેજ |
| ૧૯. | | જો મેસ માંથી બ્રાંચ કાઢી નાખવામાં આવે તો | | |
| | A. | કરંટ પર અસર થાય છે | B. | ઓપન સર્કીટ થાય છે. |
| | C. | સોર્ટ સર્કીટ થાય છે. | D. | અહીં આપેલા એક પણ નહીં. |

| | | | | |
|-----|--|---|----|--------------------------------------|
| ૨૦. | જ્યારે બે ટૅમીનલ વચ્ચે થેવેનીન થીયરી વાપરવા માં આવે ત્યારે થેવેનીન વોલ્ટેજ = | | | |
| | A. | સોર્ટ સર્કીટ ટૅમીનલ વોલ્ટેજ | B. | ઓપન સર્કીટ ટૅમીનલ વોલ્ટેજ |
| | C. | નજીક ની બેટરી ના વોલ્ટેજ | D. | સર્કીટ માં મળતા નેટ વોલ્ટેજ |
| ૨૧. | થેવેનીન થીયરી વાપરવા માં આવે જ્યારે | | | |
| | A. | ફક્ત ડી.સી. સર્કીટ માટે | B. | ફક્ત એ.સી. સર્કીટ માટે |
| | C. | ડી.સી. અને એ.સી બંને સર્કીટ માટે | D. | અહીં આપેલા એક પણ નહીં. |
| ૨૨. | સોર્ટ સર્કીટ કરંટ જે લોડ માંથી પસાર થાય છે તે | | | |
| | A. | ઇનફાઇનાઇટ ઇમ્પીડન્સ | B. | ઝીરો ઇમ્પીડન્સ |
| | C. | કેપેસિટીવ ઇમ્પીડન્સ | D. | ઇન્ડક્ટીવ ઇમ્પીડન્સ |
| ૨૩. | ઓપન સર્કીટ વોલ્ટેજ એ બે પોઇન્ટ વચ્ચેનો પાવર ડિફરન્સ છે જેનો ઇમ્પીડન્સ | | | |
| | A. | ઝીરો હોય છે | B. | ફાઇનાઇટ હોય છે |
| | C. | ઇનફાઇનાઇટ હોય છે | D. | રીએક્ટીવ હોય છે |
| ૨૪. | થેવેનીન ઇક્વીવેલેન્ટ સર્કીટ માં હોય છે..... | | | |
| | A. | એક કરંટ સોર્સ અને એક વોલ્ટેજ સોર્સ | B. | વોલ્ટેજ સોર્સ સાથે સીરીઝ રેજીસ્ટર |
| | C. | કરંટ સોર્સ સાથે પેરેલલ રેજીસ્ટર | D. | વોલ્ટેજ સોર્સ સાથે પેરેલલ રેજીસ્ટર |
| ૨૫. | નોર્ટન ઇક્વીવેલેન્ટ સર્કીટ માં હોય છે..... | | | |
| | A. | વોલ્ટેજ સોર્સ સાથે પેરેલલ રેજીસ્ટર | B. | કરંટ સોર્સ સાથે પેરેલલ રેજીસ્ટર |
| | C. | વોલ્ટેજ સોર્સ સાથે સીરીઝ રેજીસ્ટર | D. | કરંટ સોર્સ સાથે સીરીઝ રેજીસ્ટર |
| ૨૬. | સૂપરપોઝીશન થીયર નીચેના કયા નેટવર્ક માટે એપ્લીકેબલ નથી? | | | |
| | A. | લીનીઅર એલીમેન્ટ | B. | નોનલીનીઅર એલીમેન્ટ |
| | C. | ડીપેન્ડેન્ટ કરંટ સોર્સ | D. | ટ્રાન્સફોર્મર |
| ૨૭. | નેટવર્ક લીનીઅર કહેવાય જો | | | |
| | A. | ઇનપૂટ ને પ્રોપોસનલ રીસપોન્સ હોય | B. | સૂપરપોઝીશન ના પ્રીન્સીપલ પ્રમાણે હોય |
| | C. | હોમોજીનીટીના પ્રીન્સીપલ પ્રમાણે હોય | D. | B અને C બંને |
| ૨૮. | નીચે નૂ કયૂ વાક્ય ખોટું છે? | | | |
| | A. | નોડલ અને મેસ એનાલીસીસ ફક્ત લીનીઅર નેટવર્ક માટે વપરાય છે | B. | કેમર ફૂલ નોડલ એનાલીસીસ માટે વપરાય છે |

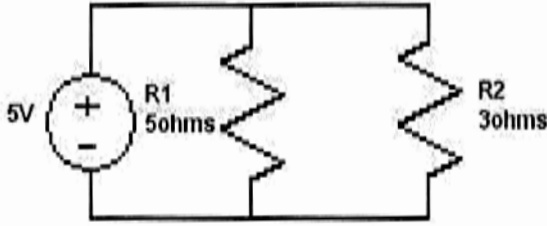
| | | | | |
|-----|--|---|----|---|
| | C. | ગોસીયન મેથડ નોડલ એનાલીસીસ માટે વપરાય છે | D. | મેસ એનાલીસીસ માટે નોડલ એનાલીસીસ વપરાય છે |
| ૨૯. | સર્કીટ સોલ્વ કરતી વખતે નેગેટીવ (-) સાઇન નો મથલબ શું થાય? | | | |
| | A. | કંઈ નહીં. | B. | એનો મથલબ કે કશૂક ખોટી ગણતરી થઇ રહી છે. |
| | C. | ખરેખર કરંન્ટ અને વોલ્ટેજ ધારેલ કરતા ઓપોઝીટ દિશા માં છે | D. | કદાચ નાનો સ્કેલીંગ ફેક્ટર વાપરેલો હોય. |
| ૩૦. | પેરેલલ RLC નેટવર્ક નો રેઝોનન્સ ફ્રિક્વન્સી એ ડાયનામિક ઇમ્પીડન્સ | | | |
| | A. | C/LR | B. | LC/R |
| | C. | L/CR | D. | R/LC |
| ૩૧. | બે રેજીસ્ટર ને સીરીઝ માં 10V ની બેટરી એકોશ જોડેલ છે. એક રેજીસ્ટર ની કિંમત બીજા કરતા બમણી છે તો કયા રેજીસ્ટર એકોશ વધારે વોલ્ટેજ મળશે? | | | |
| | A. | V(નાનો રેજીસ્ટર)=5V અને V(મોટો રેજીસ્ટર)=5V. | B. | V(નાનો રેજીસ્ટર)=6.67V and V(મોટો રેજીસ્ટર)=3.33V. |
| | C. | V(નાનો રેજીસ્ટર)=3.33V V(મોટો રેજીસ્ટર)=6.67. | D. | અહીં આપેલા એક પણ નહીં. |
| ૩૨. | 1 ohm, 2 ohm, અને 3 ohm એક બીજા સાથે પેરેલલ માં છે.તો ટોટલ રેજીસ્ટન્સ = | | | |
| | A. | 6/3 Ω | B. | 3/6 Ω |
| | C. | 11/6 Ω | D. | 6/11 Ω |
| ૩૩. |  | | | |
| | R1 અને R2 રેજીસ્ટર માંથી પસાર થતો કરંન્ટ = | | | |
| | A. | I1=1A અને I2=25A | B. | I1=0.1A અને I2=0.1667A |
| ૩૪. | બે રેજીસ્ટર પેરેલલ માં વોલ્ટેજ સોર્સ સાથે જોડાયેલ છે. તો તેમની એકોસ ના વોલ્ટેજ | | | |
| | A. | બંને રેજીસ્ટર એકોસ ના વોલ્ટેજ સોર્સ જેટલા હોય | B. | બંને રેજીસ્ટર એકોસ ના વોલ્ટેજ સોર્સ થી અડધા જેટલા હોય |
| | C. | એક રેજીસ્ટર એકોસ ના વોલ્ટેજ કુલ સોર્સ જેટલા હોય અને બીજા રેજીસ્ટર એકોસ ના | D. | અહીં આપેલા એક પણ નહીં. |

| | | | | |
|-----|--|---|----|---------------------------|
| | | ઝીરો હોય | | |
| | | મેક્સીમમ પાવર ટ્રાન્સફર જ્યારે થાય ત્યારે લોડ ઇમ્પીડન્સ | | |
| ૩૫. | A. | સોર્સ ઇમ્પીડન્સ ના કોમ્પ્લેક્સ કોન્જ્યુગેટ જેટલો હોય | B. | સોર્સ ઇમ્પીડન્સ જેટલો હોય |
| | C. | A અને B બંને | D. | અહીં આપેલા એક પણ નહીં. |
| | | સીરીઝ RLC સર્કીટ નો ટોટલ રીએક્ટન્સ રેઝોનન્સ કેટલો હોય છે? | | |
| ૩૬. | A. | XL બરાબર | B. | XC બરાબર |
| | C. | R બરાબર | D. | ઝીરો |
| | | સીરીઝ RLC સર્કીટ નો ફેઝ એન્ગલ રેઝોનન્સ કેટલો હોય છે? | | |
| ૩૭. | A. | ઝીરો | B. | 90 ° |
| | C. | 45 ° | D. | 30 ° |
| | | સીરીઝ RLC સર્કીટ માં L=15mH, C=0.015μF અને R=80Ω છે. ઇમ્પીડન્સ રેઝોનન્સ કેટલો હોય છે? | | |
| ૩૮. | A. | 15mH * ω | B. | 0.015F*ω |
| | C. | 80Ω | D. | 1/(ω*0.015) |
| | | સીરીઝ RLC સર્કીટ જે રેઝોનન્સ ફ્રિક્વન્સી કરતા ઓછી ફ્રિક્વન્સી પર કામ કરતી હોય તેનો કરંટ... | | |
| ૩૯. | A. | I leads Vs | B. | I lags behind Vs |
| | C. | I અને Vs બંને ફેઝ માં હોય | D. | અહીં આપેલા એક પણ નહીં. |
| | | સીરીઝ RLC સર્કીટ C ની વેલ્યુ વધે તો રેઝોનન્સ ફ્રિક્વન્સી કેટલી હોય ? | | |
| ૪૦. | A. | તે વધે | B. | તે ઘટે |
| | C. | તે હોય તેટલી જ રહે | D. | તે ઝીરો થઇ જાય |
| | | સીરીઝ RLC સર્કીટ માં VC=150V, VL=150V અને VR=50V. તો સોર્સ વોલ્ટેજ ની વેલ્યુ કેટલી હોય? | | |
| ૪૧. | A. | ઝીરો | B. | 50V |
| | C. | 150V | D. | 200V |
| | | સીરીઝ RLC સર્કીટ ની બેન્ડવિડ્થ 1000Hz છે. જો કોઇલ ને ઓછી Q વાળી કોઇલ થી બદલવા મા આવે તો તેની બેન્ડવિડ્થ ? | | |
| ૪૨. | A. | વધે | B. | ઘટે |
| | C. | ઝીરો થઇ જાય | D. | અહીં આપેલા એક પણ નહીં. |
| | | પેરેલલ રેઝોનન્સ સર્કીટ માં ઓછી રેઝોનન્સ ફ્રિક્વન્સી એ કેમ કરંટ સોર્સ વોલ્ટેજથી પાછળ રહી જાય છે? | | |
| ૪૩. | A. | સર્કીટ રેજુસ્ટીવ થાય છે | B. | સર્કીટ ઇન્ડક્ટીવ થાય છે |
| | C. | સર્કીટ કેપેસીટીવ થાય છે | D. | અહીં આપેલા એક પણ નહીં. |
| ૪૪. | કોઇલ દ્વારા ઉત્પન્ન થતું બધું જ ફલક્સ બીજી કોઇલ સાથે જોડાય જ્યારે કપલીંગ કો- | | | |

| | | | | |
|-----|--|---|----|---|
| | A. | R_0 | B. | $\frac{2N}{N^2-1} R_0$ |
| | C. | $(N-1)R_0$ | D. | $\frac{N}{N^2-1} R_0$ |
| ૫૩. | સિમેટ્રીકલ π એટેન્યુએટર જેનું એટેન્યુએસન N છે અને કેરેક્ટરીસ્ટિક ઇમ્પીડન્સ R_0 છે. તો તેની સન્ટ બ્રાંચ નો રેજીસ્ટન્સ બરાબર | | | |
| | A. | R_0 | B. | $(N-1)R_0$ |
| | C. | $\frac{N-1}{N+1} R_0$ | D. | $\frac{N+1}{N-1} R_0$ |
| ૫૪. | એક નેપર બરાબર | | | |
| | A. | 0.8686 dB | B. | 8.686 dB |
| | C. | 0.1152 dB | D. | 86.86 dB |
| ૫૫. | સિમેટ્રીકલ એટેન્યુએટર માં 'N' = $V_1/V_2 = I_1/I_2$ છે તો N = | | | |
| | A. | Antilog(dB/20) | B. | 20log(dB/20) |
| | C. | Antilog(20/dB) | D. | અહીં આપેલા એક પણ નહીં.. |
| ૫૬. | જો f_1 અને f_2 હાફ પાવર ફ્રિક્વન્સી હોય અને f_0 રેઝોનન્સ ફ્રિક્વન્સી હોય તો RLC સર્કિટ ની સિલેક્ટવીટી | | | |
| | A. | $f_2 - f_1 / f_0$ | B. | $f_2 - f_1 / 2f_0$ |
| | C. | $f_2 - f_1 / f_1 - f_0$ | D. | $f_2 - f_0 / f_1 - f_0$ |
| ૫૭. | એડમીટન્સ નો યુનિટ | | | |
| | A. | ઓહમ | B. | હેનરી |
| | C. | એમ્પીયર | D. | મહો |
| ૫૮. | એક્ટીવ ફિલ્ટર સર્કિટમાં | | | |
| | A. | રેજીસ્ટર, કેપેસિટર અને ઇન્ડક્ટર હોય છે | B. | રેજીસ્ટર, કેપેસિટર, ઇન્ડક્ટર અને ઓપેમ હોય છે |
| | C. | ફક્ત રેજીસ્ટર અને કેપેસિટર હોય છે. | D. | અહીં આપેલા બધાજ |
| ૫૯. | ફ્રિક્વન્સી પર થી ફિલ્ટર નું વર્ગીકરણ | | | |
| | A. | લો પાસ , હાઈ પાસ, બેન્ડ પાસ, અને બેન્ડ સ્ટોપ માં થાય છે | B. | એક્ટીવ અને પેસીવ ફિલ્ટર માં થાય છે. |
| | C. | T અને π ફિલ્ટર માં થાય છે | D. | અહીં આપેલા એક પણ નહીં. |
| ૬૦. | એક આઇડિઅલ ફિલ્ટર ના | | | |
| | A. | પાસ બેન્ડ માં ઝીરો અટેન્યુએસન હોવું જોઈએ | B. | અટેન્યુએસન બેન્ડ માં ઝીરો અટેન્યુએસન હોવું જોઈએ |
| | C. | પાસ બેન્ડ માં ઇનફાઈનાઈટ | D. | અહીં આપેલા એક પણ નહીં. |

| | | | | |
|-----|--|--|----|---|
| | | અટેન્યુએશન હોવું જોઈએ | | |
| ૬૧. | m- ડ્રાઈવ હાઈ પાસ ફિલ્ટર માં કટઓફ ફ્રિક્વન્સી 4KHz અને ઇનફાઈનાઈટ એટેન્યુએશન 3.6KHz મળે છે. તો m ની કિંમત | | | |
| | A. | 0.436 | B. | 4.36 |
| | C. | 0.34 | D. | 0.6 |
| ૬૨. | લો પાસ m-ડ્રાઈવ માટે ફ્રિક્વન્સી ઓફ ઇનફાઈનાઈટ એટેન્યુએશન $f(\infty) = \dots\dots\dots$ | | | |
| | A. | કટ ઓફ ફ્રિક્વન્સી $f(c)$ | B. | $f(\infty) = \infty$ |
| | C. | $f(c)$ ની નજીક પણ તેના થી વધારે | D. | $f(c)$ ની નજીક પણ તેના થી ઓછી |
| ૬૩. | ઝીરો ફ્રિક્વન્સીએ કોન્સ્ટન્ટ K લો પાસ T-ફિલ્ટર નો કેરેક્ટરીસ્ટીક ઇમ્પીડન્સ $Z_0 = 600\Omega$ છે.. તો $f=f_c$ એ તેનો કેરેક્ટરીસ્ટીક ઇમ્પીડન્સ | | | |
| | A. | 600Ω | B. | 0 |
| | C. | ∞ | D. | 600Ω થી વધારે |
| ૬૪. | m-ડ્રાઈવ હાઈ પાસ ફિલ્ટર ની રેઝોનન્સ ફ્રિક્વન્સી એવી રીતે નક્કી કરવા માં આવી છે કે | | | |
| | A. | તે કટ ઓફ ફ્રિક્વન્સી થી વધારે હોઈ | B. | તે કટ ઓફ ફ્રિક્વન્સી થી ઓછી હોઈ |
| | C. | તી કટ ઓફ ફ્રિક્વન્સી જેટલી હોઈ | D. | અહીં આપેલા એક પણ નહીં. |
| ૬૫. | કોન્સ્ટન્ટ K ટાઇપ ફિલ્ટર માં k ની વેલ્યુ | | | |
| | A. | $\sqrt{L/R}$ | B. | $\sqrt{L/C}$ |
| | C. | $(\omega L/C)$ | D. | અહીં આપેલા એક પણ નહીં. |
| ૬૬. | જો 3-4j સોર્સ ઇમ્પીડન્સ હોય તો મેક્સીમમ પાવર ટ્રાન્સફર માટે લોડ ઇમ્પીડન્સ ની વેલ્યુ | | | |
| | A. | $3-4j\Omega$ | B. | $3-5j\Omega$ |
| | C. | $3+4j\Omega$ | D. | અહીં આપેલા એક પણ નહીં. |
| ૬૭. | ઓલ પાસ ફિલ્ટર | | | |
| | A. | અખા ઓડીઓ બેન્ડ ને પાસ થવા દે છે | B. | અખા રેડીઓ બેન્ડ ને પાસ થવા દે છે |
| | C. | ઓછા અટેન્યુએશન સાથે બધી ફ્રિક્વન્સી ને પાસ થવા દે છે | D. | અટેન્યુએશન વગર બધી ફ્રિક્વન્સી ને પાસ થવા દે છે |
| ૬૮. | ડેલ્ટા કનેક્શન માં બધા રેજિસ્ટર ની વેલ્યુ 60Ω છે તો તેના સ્ટાર કન્વર્ઝન માં રેજિસ્ટર ની વેલ્યુ કેટલી હોઈ? | | | |
| | A. | 15Ω each. | B. | 20Ω each. |
| | C. | 30Ω each. | D. | 40Ω each. |

| | | | |
|---|---|----|--|
| એફીસીન્ટ | | | |
| A. | $K=0$ | B. | $K=1$ |
| C. | $0 < K < 1$ | D. | અહીં આપેલા બધા. |
| આઇડીઅલ પેરેલલ રેઝોનન્સ સર્કિટ નો ઇમ્પીડન્સ કેટલો હોય છે? | | | |
| ૪૫. A. | ઝીરો | B. | ઇન્ફકટીવ |
| C. | કેપેસિટીવ | D. | ઇન્ડક્ટીવ |
| જો લોવર કટઓફ ફ્રિક્વન્સી 2400Hz અને હાયર કટઓફ ફ્રિક્વન્સી 2800Hz હોય તો બેન્ડવિડ્થ? | | | |
| ૪૬. A. | 400 Hz | B. | 2800Hz |
| C. | 2400 Hz | D. | 5200Hz |
| સીરીઝ RLC સર્કિટ અને પેરેલલ RLC સર્કિટ ની રેઝોનન્સ ફ્રિક્વન્સી સરખી હોય જ્યારે | | | |
| ૪૭. A. | $Q \gg 10$ | B. | $Q \ll 10$ |
| C. | $Q=1$ | D. | અહીં આપેલા એક પણ નહીં. |
| ટ્રાન્સફોર્મર પાસે | | | |
| A. | પ્રાઇમરી અને સેકન્ડરી વાઇન્ડીંગ હોય છે જે ઇનપુટ તરીકે લેવા માં આવે છે | B. | પ્રાઇમરી અને સેકન્ડરી વાઇન્ડીંગ હોય છે જે આઉટપુટ તરીકે લેવા માં આવે છે |
| ૪૮. C. | પ્રાઇમરી વાઇન્ડીંગ હોય છે જે આઉટપુટ તરીકે લેવા માં આવે છે અને સેકન્ડરી વાઇન્ડીંગ હોય છે જે ઇનપુટ તરીકે લેવા માં આવે છે | D. | પ્રાઇમરી વાઇન્ડીંગ હોય છે જે ઇનપુટ તરીકે લેવા માં આવે છે અને સેકન્ડરી વાઇન્ડીંગ હોય છે જે આઉટપુટ તરીકે લેવા માં આવે છે |
| જો α એટેન્યુએસન નેપર માં હોય તો | | | |
| ૪૯. A. | એટેન્યુએસન dB માં = $\alpha / 0.8686$ | B. | એટેન્યુએસન dB માં = $\alpha * 0.8686$ |
| C. | એટેન્યુએસન dB માં = 0.1α | D. | એટેન્યુએસન dB માં = 0.01α |
| એટેન્યુએટર એ | | | |
| ૫૦. A. | R નેટવર્ક | B. | RL નેટવર્ક |
| C. | RC નેટવર્ક | D. | LC નેટવર્ક |
| એટેન્યુએટર નું કામ | | | |
| ૫૧. A. | સિગ્નલ ની સ્ટ્રેન્થ વધારવાનું છે | B. | ઇમ્પીડન્સ મેચ કરવાનું છે |
| C. | રેફ્લેક્સન ઘટાડવાનું છે. | D. | સિગ્નલ ની સ્ટ્રેન્થ ઘટાડવાનું છે |
| ૫૨. | સિમેટ્રીકલ T એટેન્યુએટર જેનું એટેન્યુએસન N છે અને કેરેક્ટરીસ્ટિક ઇમ્પીડન્સ RO છે. તો તેની સન્ટ બ્રાંચ નો રેજીસ્ટન્સ બરાબર | | |
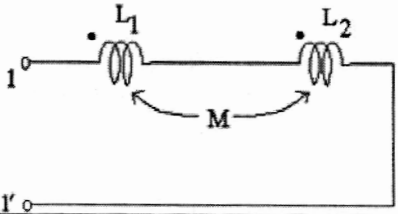
| | | | | |
|-----|--|---------------|----|-----------------|
| ૬૯. | <p>ટેર્મીનલ 1 - 1' પર ઇન્ડક્ટન્સ ની વેલ્યુ</p>  | | | |
| | A. | $L1+L2+2M$ | B. | $L1+L2-2M$ |
| | C. | $L1+L2$ | D. | $L1-L2+2M$ |
| ૭૦. | <p>નીચેનો કયો એલિમેન્ટ બાઈલેટરલ છે ?</p> | | | |
| | A. | રેજિસ્ટર | B. | FET |
| | C. | વેક્યુમ ટ્યુબ | D. | મેટલ રેક્ટીફાયર |
