Seat No.: _____ Enrolment No.____

GUJARAT TECHNOLOGICAL UNIVERSITY

MCA - SEMESTER-I • EXAMINATION - SUMMER 2013

•			e: 2610004 Date: 13-06-2013	
•			e: Fundamentals of Computer Organization	
			m to 13:00pm Total Marks: 70	
Instru			was all avecations	
	1. 2.		npt all questions. e suitable assumptions wherever necessary.	
	3.		res to the right indicate full marks.	
		0		
Q.1	(a)	i)	Define the following terms: register, multiplexer, latch	03
		ii)	Convert $(0.6875)_{10}$ to binary.	02
		iii)	Convert (1010.011) ₂ to decimal.	02
	(b)	i)	What is a BCD code? What are its advantages and disadvantages?	03
		ii)	Where does complements are used? Compare 1's complement with 2's	04
			complement.	
Q.2	(a)	i)	State the De Morgan's theorems. Explain any one.	03
	(a)	ii)	Simplify the following Boolean function:	03
		11)	i) xy+x'z+yz	04
			ii) x'y'z+x'yz+xy'	
	(b)		Draw and explain the block diagram of a digital computer.	07
	` /		OR	
	(b)		Briefly explain the working of any three peripheral devices.	07
Q.3	(a)	i)	Draw the truth table and graphical symbol, and write the algebraic	03
			function for following gates: AND, XOR	
		ii)	Simplify the Boolean function: F= A'B'C'+B'CD'+A'BCD'+AB'C'	04
	(b)		What is Flip-flop? Draw and explain the logic diagram and	07
			characteristics table of RS flip flop.	
Q.3	(a)	:/	OR Implement the Realess function E = vv+v'v'+v'z using logic getes	03
	(a)	i) ii)	Implement the Boolean function $F = xy+x'y'+y'z$ using logic gates. Simplify the following Boolean function: $F(w,x,y,z) = xy+y'z$	03
		11)	$\sum (0,1,2,4,5,6,8,9,12,13,14)$	04
	(b)		What is counter? Design and explain 3-bit binary counter.	07
	(6)		what is counter. Besign and explain 5 on omary counter.	07
Q.4	(a)	i)	Implement full adder in sum of products.	03
	, ,	ii)	Define following terms: instruction word, instruction cycle, instruction	04
			counter, op-code register	
	(b)		What do you mean by Addressing Techniques? Explain the direct,	07
			relative and indexed addressing techniques with an example.	
0 1		٠,	OR	0.7
Q.4	(a)	i)	Define access time; seek time and latency for disk memories.	03
	(I-)	ii)	Differentiate Static and dynamic RAM	04
	(b)		Explain the organization of control registers of control unit.	07
Q.5	(a)		Explain the interface of different buses with processor, memory and	07
_	` /			

		I/O devices.	
	(b)	Draw and explain the block diagram of 8086 and explain it.	07
		OR	
Q.5	(a)	Briefly explain the instruction format of 8086 and explain the working of following instructions: Working of MOV, ADD, MUL, CMP, DEC, XOR	07
	(b)	Draw the structure of 8086 execution unit and explain it.	07