

Seat No.: _____

Enrolment No. _____

GUJARAT TECHNOLOGICAL UNIVERSITY

MCA – SEMESTER - I • EXAMINATION – WINTER 2012

Subject code: 610004

Date: 07/01/2013

Subject Name: Fundamentals of Computer Organization (FCO)

Time: 02:30 pm – 05:00 pm

Total Marks: 70

Instructions:

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.

- Q. 1**
- (a) 1. Prepare a truth table for the boolean expression: $ABC + AB'C' + A'B'C'$ **01**
2. Prove the two basic De Morgan theorems, using the proof by perfect induction. **02**
3. Draw K-map for: **04**
 a. $m_0 + m_1 + m_4 + m_5$ (K-map in A,B,C)
 b. $m_2 + m_6 + m_8 + m_{10} + m_{14}$ (K-map in W,X,Y,Z)
- (b) Perform the following operations: **01**
 1. $0011 - 1000$ (Using 2's complement system). **01**
 2. Convert the hexadecimal number E2C.8 to Binary. **02**
 3. Prove by perfect induction $X + X'Y = X + Y$ **03**
 4. Derive a Boolean expression (in SOP form) for a logic circuit that will have a 1 output when $X=0, Y=0, Z=1$ and $X=1, Y=1, Z=0$ and a 0 output for all other input states. Draw a block diagram for this logic circuit.
- Q. 2**
- (a) Write short note on universal gates with circuit and truth table. **07**
(b) Write a note on display units. **OR** **07**
(b) Write a short note on Printer and its types. **07**
- Q. 3**
- (a) Discuss the concept of Master Slave Flip-Flop with Diagram. **07**
(b) Explain RS Flip Flop by giving its characteristic table and the circuit diagram. **03**
(c) Explain Cache Memory and Virtual Memory. **04**
- OR**
- (a) Explain Up-Down counters with example. **07**
(b) Explain 4-bit shift register with example. **07**
- Q. 4**
- (a) Explain BCD adder with example. **07**
(b) Briefly explain the working of Half-Adder and Full-Adder along with the circuit diagrams. **07**
- OR**
- (a) Explain how to multiply 7×9 in the registers. (all are 5 bit registers) **07**
(b) Reduce following expression using K-map and write SOP and POS form of Reduced expression. Draw circuit using Universal Gate. **07**
 $f = \sum m(0, 2, 8, 9, 10, 11) + d(1, 3)$
- Q.5.**
- (a) 1. Write short note on instruction formats. **04**
 2. Write short note on modes of Transfer. **03**
(b) 1. Explain various components of ALU in brief. **03**
 2. Explain 3-to-8 decoder. **04**
- OR**
- (a) What is a Multiplexer? Explain 4-to-1 line multiplexer. **07**
(b) What is Decoder ? Explain Binary to Octal Converter. **04**
(c) Explain JK flip-flops. **03**
