

**GUJARAT TECHNOLOGICAL UNIVERSITY****M. E. Sem – IV Examination May 2011****Subject code: 740301****Subject Name: Advance VLSI Design****Date: 16/05/2011****Time: 10.30 am – 01.00 pm****Total Marks: 70****Instructions:**

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.

- Q.1** (a) Explain Flatten Logic Structures for timing in Architecting Speed. **07**  
 (b) Discuss impact of reset on area in general, and Resources without reset in particular. **07**
- Q.2** (a) Explain the issues related to gated clock in Architecting Power. **07**  
 (b) Briefly explain software/hardware co-design. **07**
- OR**
- (b) Define Metastability and describe Metastability caused by timing violation. **07**
- Q.3** (a) Discuss resource sharing in FPGA **07**  
 (b) List various power management techniques and discuss input control in detail. **07**
- OR**
- Q.3** (a) Briefly explain Graphical State machines. **07**  
 (b) Explain any two solution of metastability problem. **07**
- Q.4** (a) Discuss Asynchronous Assertion, Synchronous Deassertion for reset circuit. **07**  
 (b) In decision tree, draw and discuss following: **07**  
 (1) Simple priority with serialized Mux structure (2) Priority-encoded logic
- OR**
- Q.4** (a) Explain potential hazard on reset pin, and draw waveform with reset hazard in internally generated reset. **07**  
 (b) Discuss Combinatorial Loops in detail. **07**
- Q.5** (a) Explain Partitioning in general; and Data Path Versus Controlling in particular. **07**  
 (b) Define or briefly discuss following: **07**
1. Floor planning
  2. Rise and fall time of signal
  3. ASIC
  4. Fully asynchronous reset
  5. Latency
  6. Throughput
  7. Dynamic power consumption in CMOS
- OR**
- Q.5** (a) Discuss speed versus area in synthesis optimization. **07**  
 (b) Explain the effect of reset on register balancing **07**