Seat No.:	Enrolment No.
-----------	---------------

GUJARAT TECHNOLOGICAL UNIVERSITY

ME Semester –II Examination Dec. - 2011

•	Subject code: 1720302 Date: 12/12/2 Subject Name: Advance Instrumentation			
-				
Instructions:				
	2.	Attempt all questions. Make suitable assumptions wherever necessary. Figures to the right indicate full marks.		
Q.1	(a)		07	
	(b)	frequency Fc= 1000 Hz Derive an equation for output impendence of non-inverting operational amplifier.	07	
Q.2	(a)	· · · · · · · · · · · · · · · · · · ·	07	
	(b)	affected by offset.	07	
	(b)	OR List and explain Operational Amplifier noise	07	
	(0)	List and explain Operational Amphiner hoise	U /	
Q.3	(a) (b)		07 07	
0.3	()	OR	0.5	
Q.3	(a)	amplifier.	07	
	(b)	Design Low pass filter using sallen configuration. Stop band attenuation is 54 dB. Pass band attenuation is 3 dB. Passband frequency where attenuation gain is maximum is 10 KHz. Stop band frequency is 20 KHz. Gain is unity.	07	
Q.4	(a)	•	07	
	(b)	capacitors and resistors in circuit are equal. Derive an equation of CMRR amplifier. OR	07	
Q.4	(a)	Draw and explain circuit diagram of differentiator with effect of	07	
	(b)	capacitance on gain and frequency on operational amplifier. Draw and explain high pass KRC filter with it equation with Q factor.	07	
Q.5	(a) (b)		07 07	
Q.5	(a) (b)	How performance of integrator can be improved?	07 07	
