# **GUJARAT TECHNOLOGICAL UNIVERSITY ME – SEMESTER II (OLD) EXAMINATION – SUMMER 2017**


# **Subject Code : 1720302 Subject Name: Advance Instrumentation** Time:10:30 A.M. to 01:00 P.M.

Date:10/05/2017

**Total Marks: 70** 

**Instructions:** 

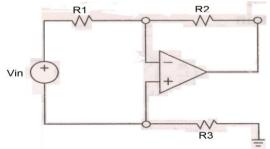- 1. Attempt all questions.
- Make suitable assumptions wherever necessary and mention it clearly in your 2. solution.
- 3. Figures to the right indicate full marks.
- 4. Draw all necessary circuit diagrams in your solution.
- 5. All symbols carry their usual meanings.
- 6. Show all node voltages and currents used in circuit diagram of your solution.
- 0.1 For the circuit shown in following figure derive the equation of feedback factor 14 β.




Consider R1=30k $\Omega$ , R2=20k $\Omega$ , R3=10k $\Omega$ , r<sub>d</sub>=150k $\Omega$ , and r<sub>o</sub>=75 $\Omega$ , evaluate the feedback factor  $\beta$ .

- **O.2** What do you mean by loading effect? With the help of circuit diagram and 07 (a) equations explain the loading effect in voltage amplifier. Explain your point considering suitable values of resistors and parameters.
  - (b) Design a variable source having the range  $-10V \le Vs \le 10V$  using a 741 op-07 amp and a 100 k $\Omega$  potentiometer. What is the need of op-amp in this design? If Vs is set to 5V how much does it change when we connect a 1 k $\Omega$  load to the source?

OR

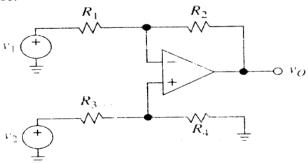(b) Derive the equations of  $A_{dm}$ ,  $A_{cm}$ , and  $CMRR_{dB}$  for difference amplifier shown 07 in following figure.




Q.3 Strain gauge bridge is cascaded by instrumentation amplifier of gain A. Strain 14 gauges are mounted in all four arms of the bridge. It has calibration facility against reference voltage ( $V_{REF}$ ) and strain gauge tolerances. Draw the circuit diagram showing all components and derive the equation of output voltage  $v_0$  from instrumentation amplifier. What is the advantage of using strain gauges in all four arms?

Let the strain gauge in your design be  $100 \pm 1\%$  types. Limit maximum current through strain gauges to 15 mA to avoid excessive self heating. Assume  $V_{REF} = 10V \pm 5\%$ . Specify suitable values for resistors connected for calibration purposes. Outline the calibration procedure.

## OR

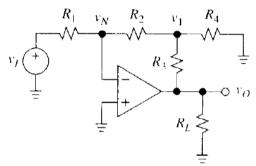**Q.3** Derive the equations for ideal gain and actual gain of the circuit shown in following figure. Consider  $R_1 = 1 \text{ M}\Omega$ ,  $R_2 = 1 \text{ M}\Omega$ ,  $R_3 = 100 \text{ k}\Omega$ ,  $R_4 = 1 \text{ k}\Omega$ , and  $R_L = 2\text{k}\Omega$ , evaluate ideal and actual gain considering  $r_d = 1 \text{ M}\Omega$ ,  $a = 10^5 \text{ V/V}$ , and  $r_0 = 75 \Omega$ .



- Q.4 (a) With the help of circuit diagram and frequency response discuss the limitation 07 of differentiator circuit and provide solution for the same.
  - (b) List important features of switched capacitor filters. Discuss its practical 07 limitations in detail.


### OR

- Q.4 (a) Define input bias and input offset currents. What are their typical valued for 741 07 op-amp? Derive the equation of error voltage generated due to input bias and input offset currents. Give your suggestion to reduce the error voltage.
  - (b) Explain the effect of finite gain bandwidth product on integrator circuits with 07 the help of diagrams and equations.
- **Q.5** (a) Draw the circuit diagram of second order band-pass KRC filter and derive of equations for dc gain, and  $\omega 0$ . Design a filter with  $f_0 = 1000$  Hz and bandwidth of 200 Hz. What is its resonance gain?
  - (b) With the help of circuit diagrams, equations and Bode plot describe any two 07 first-order active filters.

### OR

Q.5 (a) Explain noise power density, spectral noise density, and white noise in detail. 07

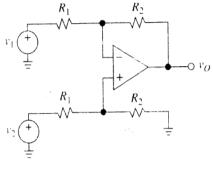(b) The difference amplifier of following figure uses a 741 opamp having CMRR of 90 dB and perfectly matched resistances  $R1=15k\Omega$  and  $R2=150k\Omega$ . If the inputs are tied together and driven with a common signal v<sub>I</sub> (i.e v<sub>1</sub> = v<sub>2</sub> = v<sub>1</sub>) then estimate the typical change in v<sub>0</sub> if (i) v<sub>1</sub> is slowly changed from 0 to 10V and (ii) v<sub>1</sub> is a 10 kHz, 10 V peak to peak sine wave. Consider CMRR at 10 kHz of 57 dB.



\*\*\*\*\*