Seat No.:	Enrolment No.

GUJARAT TECHNOLOGICAL UNIVERSITY ME – SEMESTER II (OLD) EXAMINATION – SUMMER 2017

Subject Code: 1720709 Subject Name: Advanced Power Converters Time: 10:30 A.M. to 01:00 P.M. Instructions: Total Marks			Date:12/05/2017	
			al Marks: '	70
		Attempt all questions. Make suitable assumptions wherever necessary. Figures to the right indicate full marks.		
Q.1	(a)	What is multi pulse converter? What are its disadvantages? With a	ppropriate	07
	(b)	block diagram explain how a 12 pulse converter can be obtained. With relevant waveforms and circuit diagram explain operation loaded resonant half bridge dc to dc converter operating in discontinue.		07
Q.2	(a)	Explain in brief how switching stress can be reduced on electron using ZCS and ZVS topologies.	ics switch	07
	(b)	Discuss different transformer connections for multi pulse converter. OR		07
	(b)	Explain the operation of series loaded resonant (SLR) half-bridg converter operating in discontinuous mode.	ge DC-DC	07
Q.3	(a) (b)	Write a brief note on 5 level NPC multi level inverter. Discuss 4 step commutation technique for matrix converter. OR		07 07
Q.3	(a)	Write a brief note on electronics switches used in matrix converter. rules to be observed for operating the switches of a matrix converter.	State basic	07
((b)	Mention the advantages and disadvantages of matrix converter with other means by which output voltage magnitude and frequence controlled.	-	07
Q.4	(a)	Write a brief note on cascaded H-bridge multi level inverter ope carrier based PWM control strategy.	rated with	07
	(b)	Write a brief note on the control strategy used for transmitting through HVDC terminals.	the power	07
		OR		
Q.4	(a)	Explain the switching sequence to get minimal neutral point voltage d for NPC multilevel inverter.	eviation	07
	(b)	Write a brief note on STATCOM and explain how it differs from SVO	J.	07
Q.5	(a)	What is MPPT when referred to solar photo voltaic system? How is a with DC-DC converter feeding a DC load?	t achieved	07
	(b)	With suitable block diagram discuss the control scheme for De Induction Generator based wind energy generation system.	oubly Fed	07
Q.5	(a)	OR Explain with block diagram scheme for instantaneous VAR compensations this method differ from that of fixed capacitor thyristor reactors?		07

(b) Draw the space vector diagram for diode-clamped 3-level inverter. Hence,

derive the dwell time equations for the space vectors for any one region.

07