Seat No.:	Enrolment No.
Deat 1 10	Emoment 1 10:

GUJARAT TECHNOLOGICAL UNIVERSITY ME – SEMESTER II (OLD) EXAMINATION – SUMMER 2017

Subject Code: 1724502 Date:10/05/2017

Subject Name: Power Electronics II

Time: 10:30 A.M. to 01:00 P.M. Total Marks: 70

Instructions:

1. Attempt all questions.

- 2. Make suitable assumptions wherever necessary.
- 3. Figures to the right indicate full marks.

77	Q.1	(a)	Explain operation of 3-Ø to 3-Ø Matrix Converter. Also draw Switching Matrix Symbol in support.	07
		(b)	List various Power Factor Improvement Techniques. Explain Extinction Angle Control with necessary diagram and waveforms.	07
	Q.2	(a)	List various drawbacks of Basic Series Resonant Converter. Draw necessary supportive circuit to overcome mentioned drawbacks.	07
		(b)	type Converter.	07
		(b)	OR Draw necessary circuit and switching sequence for 3-Level Neutral Point Clamped Inverter.	07
	Q.3	(a)	Explain operation of Six Pulse Bridge Converter with neglecting Source Inductance, L _s . Draw necessary waveforms in support.	07
		(b)	Explain Thermal consideration with respect to design and selection of Magnetic Component. Write necessary equations in support.	07
	Q.3	(a)	Justify need of Twelve Pulse Converter. Draw necessary circuit and waveforms in support.	07
		(b)	With respect to Magnetic Circuit Design explain importance of Eddy Current Loss in Laminated Cores.	07
	Q.4	(a)	Explain Half Bridge Series Loaded Resonant DC-DC Converter in Discontinuous mode of Operation. Draw necessary diagrams in support.	07
		(b)	circuit.	07
	Q.4	(a)	Explain Half Bridge Parallel Loaded Resonant DC-DC Converter in Discontinuous mode of Operation. Draw necessary diagrams in support.	07
		(b)	Explain Zero Voltage Switching (ZVS) Resonant Converter with necessary circuit.	07

Q.5	(a)	List various applications of Unity Power Factor Rectifiers. Explain any one in detail.	07
	(b)	Explain Resonant DC Link Inverter with Zero Voltage Switching. Draw necessary circuit and waveforms in support. OR	07
Q.5	(a)	Explain Boost type Power Factor Correction (PFC) Circuit with adequate supportive diagrams.	07
	(b)	Explain High Frequency Link Integral Half Cycle Converter with necessary diagrams.	07
