Seat No.:	Enrolment No.

GUJARAT TECHNOLOGICAL UNIVERSITY

ME SEMESTER - I EXAMINATION - SUMMER 2017

Subject Code: 2714502 Subject Name: Solid State DC Drives			Date:10/05/2017	
Tiı	me:0 tructio 1. 2.	2:30 p.m. to 05:00 p.m. Total Marks:	70	
Q.1	(a) (b)	Explain four quadrant operation of motor which driving a hoist load. What are the main factors which decide the choice of DC drive for a given application?	07 07	
Q.2	(a)	For type-A dc chopper with RLE load and continuous load current condition shows that per unit ripple current is maximum when duty cycle is 0.5. Also draw the necessary waveforms and circuit diagram.	07	
	(b)	Explain class D type chopper control DC motor drive. OR	07	
	(b)	Explain the armature control and flux control of dc motors and also explain constant torque and constant power operation.	07	
Q.3	(a)	Discuss the dynamic braking of separately excited DC motor? During braking, separately excited motor can be converted as self excited generator, why?	07	
	(b)	Draw circuit diagram, waveform and write the equations for 1-phase full controlled converter, separately excited dc motor drive where current of the armature is assumed to be discontinuous mode.	07	
Q.3	(a)	OR Draw equivalent circuit and output voltage waveform of an ideal dual converter. Derive necessary condition of firing angles.	07	
	(b)	Explain multi phase chopper drive.	07	
Q.4	(a)	Explain the principle of phase control. Obtain the equation of output voltage of phase controlled DC motor drive.	07	
	(b)	Describe the working of a three phase full converter fed DC separately excited motor with relevant waveforms and expressions. OR	07	
Q.4	(a)	Explain different types of control strategies for chopper drive.	07	
	(b)	Develop a transfer function of separately excited DC motor with speed control loop. Give the limitation of only speed control loop.	07	
Q.5	(a)	What are the reasons for using load equalization in an electrical drive? Why current sensing is required in electrical drives? What are the common methods of current sensing?	07	
	(b)	Explain close loop control of DC motor with block diagram. OR	07	
Q.5	(a)	How does a phase locked loop speed control scheme operate? Where do you use it?	07	
	(b)	With neat schematic Block diagram describe the Micro-computer control of 4 quadrant DC drives with flow chart.	07	
