

**GUJARAT TECHNOLOGICAL UNIVERSITY**  
**ME SEMESTER II EXAMINATION – SUMMER 2017**

**Subject Code: 2720312**

**Date: 25/05/2017**

**Subject Name: Intelligent Sensor and Instrumentation**


**Time: 02:30 PM to 05:00 PM**

**Total Marks: 70**

**Instructions:**

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.

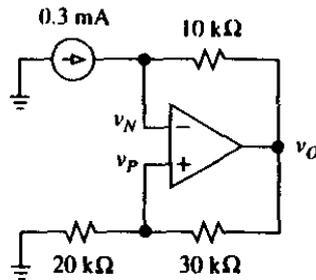
**Q.1 (a) Find  $V_N$ ,  $V_P$  and  $V_O$  in the circuit of Fig1. 07**



Repeat with a 40Kohm resistance in parallel with the 0.3mA source.

**(b) Explain switched capacitor integrator in detail. 07**

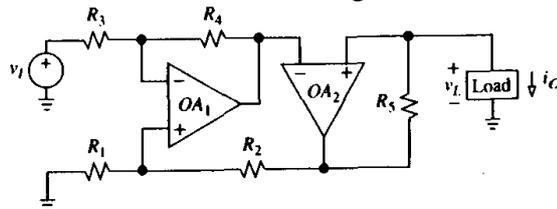**Q.2 (a) Given that the circuit of fig.2 yields  $i_o = A v_i - (1/R_o)v_L$ , find expressions for A and  $R_o$ , as well as the condition among its resistances that yields  $R_o = \infty$ . Also discuss the effect of using 1% resistances. 07**



**(b) Explain IEEE 1451.1 standard in detail. 07**

**OR**

**(b) Explain wireless sensor network in detail. 07**

**Q.3 (a) Explain Chebyshev approximation in detail. 04**

**(b) Explain the error caused by Input bias and offset currents in detail 10**

**OR**

**Q.3 (a) Briefly explain the term sensitivity related to active filter design. 04**

**(b) Explain in detail compensation of input offset error in OP-Amp. 10**

**Q.4 (a) How performance of integrator may improved by selecting the high quality of capacitor? 07**

**(b) Find n for a low pass butterworth response with  $f_c=1\text{kHz}$ ,  $f_s=2\text{kHz}$ ,  $A_{max}=1\text{dB}$  and  $A_{min}= 40 \text{ dB}$ . 07**

**OR**

**Q.4 (a) Draw and explain band pass multiple feedback filter with its equation with Q factor. Also design the multiple feedback band pass filter with  $f_o=1\text{kHz}$ ,  $Q=10$  and  $H_o=20\text{dB}$ . 14**

**Q.5 (a) Design a 6<sup>th</sup> order causer low pass filter with  $f_c=1\text{kHz}$  and  $H_o=0\text{dB}$ . 14**  
 $f_{01}=648.8\text{Hz}$ ,  $f_{02}=916.5\text{Hz}$ ,  $f_{03}=1041.3\text{Hz}$ ,  $f_{z1}=4130.2\text{Hz}$ ,  $f_{z2}=1664.3\text{Hz}$ ,  $f_{z3}=1329.0\text{Hz}$   $Q_1=0.625$ ,  $Q_2=1.789$   $Q_3=7.880$

**OR**

- Q.5 (a)** Design a 5<sup>th</sup> order elliptic high pass filter(direct design) with  $f_c=300\text{Hz}$ ,  $f_s=150\text{Hz}$ ,  $A_{\text{max}}=0.1\text{dB}$  and  $A_{\text{min}}= 40 \text{ dB}$ .  $L_1=1.02789\text{H}$ ,  $L_2=0.15134\text{H}$ ,  $L_3=1.63179\text{H}$ ,  $L_4=0.44083\text{H}$  and  $L_5=0.81549\text{H}$ , and  $C_1=1.215134\text{F}$  and  $C_2=0.93525\text{F}$  **14**

\*\*\*\*\*