## GUJARAT TECHNOLOGICAL UNIVERSITY

M. E. - SEMESTER- II • EXAMINATION – SUMMER 2017

Subject Code: 2722914  Subject Name: Industrial Electronics & Control  Time: 02:30 PM – 05:00 PM  Instructions:  Total Mar				
Q.1	(a)	Draw only the basic structure of a Power MOSFET and briefly exp principle of operation with neat diagram.	lain its 07	
	<b>(b)</b>	A UPS is driving a 1kW load which has a lagging power factor of The efficiency of the inverter is 84%. The battery voltage is 24V there is a separate charger for battery, determine: (i) kVA rating inverter, (ii) Wattage of rectifier and (iii) AH rating of battery for a latine of 15 minute.	DC. If of the	
Q.2	(a)	What is an electric drive? What is the basic difference between DC and AC drive? Explain any one method of breaking of a DC moto neat diagram.		
	<b>(b)</b>	Why electrical power is transmitted at high voltage level? advantages and disadvantages of HVDC transmission over transmission.  OR		
	<b>(b)</b>	(i) What are the applications of high frequency induction heating only the expression of heat generated in the work-piece usin frequency induction heating.		
		<ul> <li>(ii) Induction heating is used for hardening of an aluminum Required depth of penetration is 1.3mm. Relative permeabilist specific resistance of aluminum is 1.0 &amp; 5×10<sup>-7</sup>Ωm respectively.</li> </ul>	ty and	
Q.3	(a)	Compare Online UPS and Offline UPS. Explain Offline UPS with block diagram.	h neat 07	
	<b>(b)</b>	Explain the principle of operation of SCR using two-transistor equipmodel.  OR	ivalent <b>07</b>	
Q.3	(a)	Why battery charging is required? What are the different charging representation of the property of the proper	nodes? <b>07</b>	
	<b>(b)</b>	Explain feed-forward SMPS with neat circuit diagrams and waveform	ms. <b>07</b>	
Q.4	(a) (b)	Explain battery operated vehicle with basic block diagram.  Explain the principle of operation of dielectric heating with neat dia  What are the applications of dielectric heating?  OR	97 grams. 97	
Q.4	(a) (b)	Explain energy storage welding system with neat diagram. Enlist various speed control methods of DC series and shunt r Explain any one method.	07 notors. 07	

Q.5	(a) (b)	Explain the concept of V/f control of induction motor. Explain push-pull SMPS with neat circuit diagrams and waveforms.			
		OR			
Q.5	(a)	Draw only the basic structure of an IGBT and briefly explain its principle of operation with neat diagram.			
	<b>(b)</b>	Classify various welding methods. Explain spot welding with neat diagram.	07		

\*\*\*\*\*\*