Seat No.:	Enrolment No.

## GUJARAT TECHNOLOGICAL UNIVERSITY

ME - SEMESTER- III (NEW) EXAMINATION - SUMMER 2017

	•	Code: 2734501 Date:02/05/20 Name: Application of Power Electronics to Power System	17
Tir	ne:02	2:30 pm to 05:00 pm Total Marks:	70
	2.	Make suitable assumptions wherever necessary. Figures to the right indicate full marks.	
Q.1	(a) (b)	Explain operation of Thyristor Control Rectifier (TCR). Explain the operation of Static Synchronous Series Capacitor (SSSC).	07 07
Q.2	(a) (b)	Give classification of FACTS devices and their advantages.  With phasor diagram explain load compensation and system compensation.  OR	07 07
	<b>(b)</b>	Explain the FC-TCR configuration. Explain operating characteristic without step down transformer and losses in FC-TCR.	07
Q.3	(a)	Derive an expression for mid-point voltage of a symmetrical lossless transmission line as a function of power flow on it.	07
	<b>(b)</b>	Explain the construction and working of IPFC.  OR	07
Q.3	(a)	Discuss the influence of SVC on the system voltage to which it is connected through coupling transformer.  Discuss the role of SVC as a voltage controller.	07 07
0.4	(b)	· ·	07
Q.4	(a) (b)	Briefly describe the working of a Thyristor Controlled Transformer (TCT).  Draw and explain the V-I characteristics of STATCOM and give a brief comparison with the V-I characteristics of TSC-TCR.	07
Q.4	(a)	OR Explain the construction and working of a UPFC.	07
r.y	(b)	Explain the construction and working of a CTTC.  Explain the application of STATCOM for improving transient stability of a power system. Discuss the control strategy used.	07
Q.5	(a)	Explain the principle of operation of basic Thyristor-Controlled Series Capacitor (TCSC) scheme.	07
	<b>(b)</b>	Discuss the importance of having slope in the dynamic characteristic of SVC. <b>OR</b>	07
Q.5	(a) (b)	Explain synchronous reference frame theory.  Draw and explain compensating voltage verses line current characteristics of TCSC in voltage control mode and reactance control mode.	07 07

\*\*\*\*\*