GUJARAT TECHNOLOGICAL UNIVERSITY ME – SEMESTER IV(NEW) - EXAMINATION- SUMMER- 2017

Subject Code: 2744502Date:03/05/2017Subject Name: Electromagnetic Compatibility in Power ElectronicsTime: 02:30 pm to 05:00 pmInstructions:1. Attempt all questions.2. Make suitable assumptions wherever necessary.3. Figures to the right indicate full marks.			
Q.1	(a) (b)	Derive the equations of insertion loss of two port network in terms of Z parameters and ABCD parameters. Explain EMI from rectifier circuits.	07 07
Q.2	(a) (b)	Describe parallel injection method of worst-case insertion loss test method. Write a short on measuring HF characteristics of EMI filter elements. OR	07 07
	(b)	Explain impulse voltage withstand test with necessary diagram.	07
Q.3	(a) (b)	Describe in detail the noise suppression in relay system. Draw and explain equivalent circuits of common mode choke coils. OR	07 07
Q.3	(a) (b)	Explain the application of RC snubbers to power semiconductors. Discuss inductive noise coupling mode of electromagnetic coupling.	07 07
Q.4	(a) (b)	Explain any one electromagnetic disturbance in details with suitable example. Write a short note on measuring the interference voltage. OR	07 07
Q.4	(a) (b)	Why EMC test is required? Discuss the EMC tests as per IEC specifications. Explain wiring layout method to reduce EMI coupling.	07 07
Q.5	(a) (b)	Explain in detail about spectrum analyzers. What are the effects of extreme condition of mismatched impedance on EMI filter?	07 07
OR			
Q.5	(a) (b)	Briefly explain the surge protection devices. Explain Laplace transform root calculation method.	07 07
