Seat No.:	Enrolment No
-----------	--------------

Subject Code: 710702N

GUJARAT TECHNOLOGICAL UNIVERSITY ME SEMESTER – I (OLD) EXAMINATION – SUMMER 2017

Subject Name: Advanced Power Electronics Time:02:30 P.M. to 05:00 P.M. **Total Marks: 70 Instructions:** 1. Attempt all questions. 2. Make suitable assumptions wherever necessary. 3. Figures to the right indicate full marks. (a) Describe the necessity of Isolation of gate and Base drives and explain how they are 0.1 07 implemented using the pulse transformer and Opto Isolator with necessary circuit diagrams. Develop the steady-state and switching characteristics of (i) Power BJT and (ii) SCR. 07 **(b) Q.2** Explain the working of dc-dc converter. Explain the working of Buck regulators with the **07** help of circuit diagram and various waveforms. A 230 V, 1 kW resistive load is connected to a half bridge rectifier. Input voltage of 07 the rectifier is 230 V ac. Find the values of (a) output dc power (b) Output ac power (c) Output Gross power. OR **(b)** Write short note on SMPS design criterion. 07 Q.3 Discuss circulating current operation of 3-phase cyclo-converter. 07 (a) Explain difference in inverter and cyclo-converter circuit. **(b)** 07 OR Define step-up and step-down cycloconverter. Discuss 3-phase to 3- phase bridge type **Q.3** (a) **07** cycloconverter with necessary diagram. **(b)** Explain operation of current source inverter with neat diagram. Differentiate it from **07** voltage source inverter. A single phase AC voltage regulator is supplied by single phase ac 230 Volts, 50 Hz 0.4 07 supply. A resistive load of 10 ohms is connected at the output of ac voltage regulator. Find rms value of output voltage and current and input power factor if firing angle α is (b) Discuss 3-phase bidirectional delta-connected AC controller with necessary circuit and 07 waveforms for the delay angle of 120° . OR What is the difference in design of power transformer and high frequency transformer? 07 0.4 (a) Discuss steps illustrating design of inductor. **(b) 07** Discuss various harmonics reduction techniques in the Inverter output with necessary **07** Q.5 sketches. **(b)** Explain single quadrant, two quadrant and bidirectional operation of switches. 07 **Q.5** Explain the various protection circuits against dv/dt, di/dt and overvoltage in the driver **07** (a) circuit of power devices. Distinguish between SCR, GTO, Power MOSFET and IGBT. 07 **(b)**

Date:09/05/2017