Seat No.:	Enrolment No.

GUJARAT TECHNOLOGICAL UNIVERSITY ME SEMESTER – I (OLD) EXAMINATION – SUMMER 2017

Subject Code: 714501N Subject Name: Power Electronics – I Time: 02:30 P.M. to 05:00 P.M. Instructions:			Date: 08/05/2017	
		rks: 70		
11150	1. 2.	Attempt all the questions. Make suitable assumptions wherever necessary. Notations and symbols used have usual technical meaning.		
Q.1	(a) (b)	Explain principle of operation of IGBT. Explain Class-D commutation of SCR.	07 07	
Q.2	(a) (b)	Explain the operation of 3-phase bridge inverter with Y-connected resistive load in 180° conduction mode with neat circuit diagram and waveforms. Explain any one harmonic elimination technique with respect to 1-phase	07 07	
	(b)	OR Draw only the basic structure of a TRIAC. Enlist all the possible triggering modes of TRIAC. Explain any one triggering mode.	07	
Q.3	(a)	Explain unipolar switching scheme of a 1-phase sinusoidal PWM inverter with neat circuit diagram and waveforms.	07	
	(b)	Explain center-tapped 1-phase to 1-phase cycloconverter with neat circuit diagram and waveforms.	07	
Q.3	(a) (b)	OR Explain UJT as a triggering circuit for SCR with necessary waveforms. Explain the need of Heat-sink. Explain its selection process.	07 07	
Q.4	(a)	Explain the "latching" phenomenon of SCR using its two-transistor equivalent model. Also derive the equation for the anode current.	07	
ΩA	(b)	Explain dual converter with circulating current control mode. OR Explain the operation of a 12-pulse converter with neat circuit diagram and	07 07	
V. -1	(b)	waveforms. Explain the operation of a 12 pulse converter with neat circuit diagram and necessary waveforms.	07	
Q.5	(a)	Draw only the basic structure, symbol and V-I characteristic of a GTO. Explain Turn ON and Turn OFF mechanism of GTO with neat diagrams.	07	
	(b)	Explain the operation of forward converter with neat circuit diagram and necessary waveforms.	07	
Q.5	(a)	OR Explain the principle of operation of integral cycle control type 1-phase AC voltage controller with neat diagram and waveforms. Also derive the expression for the RMS output voltage in terms of duty cycle.	07	
	(b)	Explain the operation of boost converter with necessary waveforms.	07	
