## **GUJARAT TECHNOLOGICAL UNIVERSITY** M. E. - SEMESTER - I • EXAMINATION - SUMMER • 2013

Subject code: 710305NDate: 06-06-2013Subject Name: Programmable Logic Controller			
Time: 10.30 am – 01.00 pm Total Marks: 70			
Instructions:			
	-	Attempt all questions.	
	2. 3.	Make suitable assumptions wherever necessary. Figures to the right indicate full marks.	
Q.1	(a) (b)	Explain the technique by which PLC scan and execute any ladder program. Explain the difference between data processing computer and process control computers with help of functional block diagram.	07 07
Q.2	(a)	Enumerate types of PLC modules and explain discrete DC output module	07
	(b)	showing its internal functional block diagram. Discuss merits and demerits of PLC.	07
		OR	~-
	(b)	What is the difference between discrete I/O and digital I/O? Explain with the help of suitable examples.	07
Q.3	(a)	Realize 8X1 multiplexer circuit using PLC ladder diagram.	07
	(b)	Explain in details counters in PLC. OR	07
Q.3	<b>(a)</b>	Develop PLC ladder to realize following Boolean equation: (1) $N = A \cdot P(A + C + C + C + C + C + C + C + C + C + $	07
	(b)	(1) $X = A+B(A + CB\phi + DA\phi C) + ABCD$ (2) $Y = (A+BA\phi) + (C+D + EC\phi)\phi$ Explain in details timers in PLC.	07
Q.4	(a)	List out PLC comparison functions. Explain Greater than or equal to (GEQ)	07
	(b)	and less than or equal to (LEQ) functions with suitable examples. Develop Ladder Logic Diagram to generate square wave.	07
<b>0</b> 4		OR	~-
Q.4	<b>(a)</b>	<ul><li>Explain following PLC functions with suitable examples:</li><li>1) SKIP 2) Jump with return 3) Block Move</li></ul>	07
	(b)	Make a program to increase the counter by one with each pulse from the pulse generator PG and decrease another counter by the same pulse.	07
Q.5	(a) (b)	Explain PLC shift register functions with suitable example. Construct ladder diagram for the following process: Two motors are to be controlled as follows:	07 07
		<ul> <li>When the switch is operated both motor must run</li> </ul>	
		<ul> <li>After 3 min motor one must stop</li> </ul>	
		<ul><li>Motor two continue running for another 3 min</li><li>At this point lamp must go ON</li></ul>	
		<ul> <li>After further 2 min, lamp goes OFF and cycle repeats</li> </ul>	
		<ul> <li>If stop switch is operated at any time, the system will continue till end of the cycle and then stop.</li> </ul>	
OR			
Q.5	(a) (b)	List all PLC Matrix Functions. Explain any one in details. Write a short note on PLC networking.	07 07

\*\*\*\*\*