Seat No.:	Enrolment No.

GUJARAT TECHNOLOGICAL UNIVERSITY

M. E. - SEMESTER – I • EXAMINATION – SUMMER • 2013

	•	code: 710412N Date: 18-06-2013	
Tir	ne: 1	Name: Digital VLSI Design 0.30 am – 01.00 pm Total Marks: 70 tions:	
	1. 2.	Attempt all questions. Make suitable assumptions wherever necessary. Figures to the right indicate full marks.	
Q.1	(a) (b)	Explain the concept of Regularity, Modularity and Locality in detail Explain the need for LOCOS process, principal of LOCOS and LOCOS process with all necessary diagrams.	07 07
Q.2	(a) (b)	Discuss procedure to measure data for experimental determination of the parameters k_n , V_{TO} and substrate bias coefficient. Define threshold voltage for MOS transistor. Describe the four component of threshold voltage.	07 07
	(b)	Describe Accumulation, Depletion and Inversion process for the MOS system under external bias. Also derive the equation for maximum depletion region depth at the onset of surface inversion.	07
Q.3	(a) (b)	What do you mean by MOSFET Scaling? Explain Constant-field Scaling and Constant-voltage Scaling in detail Draw and explain voltage transfer characteristic of CMOS inverter and discuss noise margin.	07 07
Q.3	(a) (b)	OR Draw two-input CMOS NAND gate and obtain expression for switching threshold voltage (v_{th}) . Assume that both NMOS transistors are identical. Similarly, PMOS transistors are also identical. Write a short note on oxide related MOSFET capacitance.	07 07
Q.4	(a) (b)	Define PHL and PLH for CMOS inverter. Derive PHL for CMOS Inverter What is CPL. Draw the circuit diagram of CPL NAND2 and CPL NOR2 gate and explain working.	07 07
Q.4	(a) (b)	Write short note on domino logic circuit Explain RC Delay model and Elmore delay model.	07 07
Q.5	(a) (b)	Draw the circuit diagram and stick diagram of 2-input CMOS NOR gate. Explain CMOS transmission gate in detail. OR	07 07
Q.5	(a) (b)	Explain basic principles of pass transistor, using logic õlö transfer event. How it is important in dynamic logic circuits. Draw and explain CMOS clocked JK latch circuit with waveform.	07 07
