GUJARAT TECHNOLOGICAL UNIVERSITY M. E. - SEMESTER – I • EXAMINATION – SUMMER • 2013

Subject code: 712902N

Subject Name: Power Processing Circuits

Time: 10.30 am – 01.00 pm

Instructions:

Date: 04-06-2013

Total Marks: 70

- 1. Attempt all questions.
- 2. Make suitable assumptions wherever necessary.
- 3. Figures to the right indicate full marks.
- Q.1 (a) Explain construction and working of IGBT. Also compare with 07 MOSFET in all respect.
 - (b) Discuss about driving circuit and protection for MOSFET power 07 switch.
- Q.2 (a) Explain working of m phase controlled converter circuit. And find the 07 expression of an output voltage.
 - (b) The single phase half bridge inverter supplies a resistive load of 10 07 ohms. The supply voltage input to the inverter is 200 Vdc. Determine,
 - (1) RMS output voltage at the fundamental frequency
 - (2) Output power
 - (3) Average, RMS and peak currents of power switch.

OR

- (b) A single phase full wave controlled rectifier is operated through single 07 phase AC source 200V, 50Hz. The load on the converter consists of R=10 ohms, emf E=100 V dc. The SCR is triggered with continuous DC signal. Calculate (1) Average and Peak current of the switch (2) average value of load current.
- Q.3 (a) Explain three phase full bridge converter circuit with R-L load. Draw 07 appropriate load.
 - (b) Write a brief note on effect of source inductance on controlled 07 converter.

OR

- Q.3 (a) Explain operation of single phase integral cycle control for AC voltage 07 controller.
 - (b) Discuss the boost type DC-DC converter circuit. Derive an expression 07 for output voltage of the boost converter.
- Q.4 (a) Discuss Buck-boost type DC-DC converter circuit along with relevant 07 waveforms.
 - (b) Describe how single phase variable ac voltage with variable frequency 07 can be obtained from three phase ac supply.

OR

- Q.4 (a) Explain operation of three phase inverter circuit with 120 degree 07 conduction for delta type load.
 - (b) Explain full bridge type topology of DC-DC converter circuit. 07
- Q.5 (a) Write a brief note on space vector PWM technique for inverter. 07
 - (b) Explain dual converter with non-circulating current mode. 07

OR

Q.5 (a) Explain single pulse width modulation for single phase inverter circuit. 07

Also discuss how selected harmonic can be eliminated?

(b) Discuss Class D type commutation circuit for SCR. Draw appropriate 07 waveforms of SCR current and voltage.
