GUJARAT TECHNOLOGICAL UNIVERSITY M. E. - SEMESTER – I • EXAMINATION – SUMMER • 2013

Subject code: 712907NDate: 06-06-2013Subject Name: Power Devices and ApplicationsTotal Marks: 70Time: 10.30 am - 01.00 pmTotal Marks: 70Instructions:Total Marks: 70			
	1. 2.	Attempt all questions. Make suitable assumptions wherever necessary. Figures to the right indicate full marks.	
Q.1	(a)	each component in details.	07
Q.2	(b) (a)		07 07
	(b)	 Why schotky diodes switch off much faster than p-n junction diode? A diode has a reverse recovery time of 2.5 μs if di/dt is 17.5 A/μs, find a stored charge and peak reverse current. 	07
	(b)	-	07
Q.3	(a)	Draw and explain Power circuit, symbol and waveforms of PUT. What are the advantages of PUT over UJT?	07
	(b)	Compare various types of firing circuits in tabular forms. OR	07
Q.3	(a) (b)	Compare SUS and SBS in tabular forms. Draw the Power circuit, V-I characteristic and waveforms for UJT as a relaxation oscillator. Also derive the equation for frequency of UJT relaxation oscillator.	07 07
Q.4	(a) (b)	Define Commutation. Enlist and explain TURN-ON methods of SCR. Draw and explain two transistor model of SCR. Also explain regenerative action of thyristor by taking $1+2 \times 1$ as a reference. OR	07 07
Q.4	(a)	-	07
	(b)		07
Q.5	(a)	Draw and explain block diagram of UPS systems. Also list out the applications of UPS systems.	07
	(b)	Enlist applications of thyristor. Explain light-dimmer control. OR	07
Q.5	(a) (b)	Why battery charging is needed? Draw and explain battery charging circuit. Explain Power circuit of ideal zero voltage switch with neat sketch.	07 07
