<b>GUJARAT TECHNOLOGICAL UNIVERSITY</b> M. E SEMESTER – II • EXAMINATION – SUMMER • 2013			
Subject code: 725203Date: 03-06-2013Subject Name: Analog and Mixed Signal IC Design Time: 10.30 am – 01.00 pmTotal Marks: 70Instructions:1. Attempt all questions.1. Attempt all questions.2. Make suitable assumptions wherever necessary.3. Figures to the right indicate full marks.			
Q.1	(a) (b)	List MOSFET second order effects and discuss any one in detail. Draw the CS (Common Source) stage with diode connected load and small signal equivalent circuit of it. Derive voltage gain for the same.	07 07
Q.2	<b>(a)</b>	Draw the Common Drain stage and small signal equivalent circuit of it. Derive voltage gain for the same.	07
	(b)	List different specifications of data converter and explain any three in brief. OR	07
	(b)	Discuss performance parameters of Operational amplifier.	07
Q.3	(a) (b)	Draw and explain Gilbert cell. Draw the circuit diagram of a single stage operational amplifier and explain the operation.	07 07
Q.3	(a) (b)	OR Explain Thermal Noise and Flicker noise. Discuss simple current mirror circuit and find current gain and output impedance.	07 07
Q.4	(a) (b)	Discuss characteristics of PLL and charge pump PLL. Draw and explain current steering DAC. <b>OR</b>	07 07
Q.4	<b>(a)</b>	Discuss different building blocks that are required for constructing switch capacitor circuits.	07
	(b)	Discuss temperature independent references in brief.	07
Q.5	(a) (b)	Discuss stability and also explain one-pole, two poles and Three poles system. Explain Op-amp gain boosting. <b>OR</b>	07 07
Q.5	<b>(a)</b>	Draw high frequency equivalent circuit of Source Follower and derive input and output impedance.	07
	(b)	List all the feedback topologies and discuss any two in detail	07

\*\*\*\*\*