Sea	t No.:		
		GUJARAT TECHNOLOGICAL UNIVERSITY	
C 1	• •	M. E SEMESTER – II • EXAMINATION – SUMMER • 2014	
	U	code: 1710411 Date: 24-06-2014	
Tiı	me: 0	Name: RF and Microwave Engineering 2:30 pm - 05:00 pm Total Marks: 70	
Ins		Attempt all questions	
	2.	Attempt all questions. Make suitable assumptions wherever necessary. Figures to the right indicate full marks.	
Q.1	(a)	With neat sketch explain õAperture Couplingö with equivalent electric and magnetic polarization for various Transmission Line and Waveguide	0
	(b)	Configurations. How Signal Flow Graph can be reduced to a single branch between two nodes to obtain any desired wave amplitude ratio using õDecomposition Rulesö.	0
Q.2	(a)	Define the Terms: Reflection Coefficient, Return Loss, VSWR and Characteristic Impedance.	0
	(b)	Prove that TE mode of Rectangular Waveguide, Cut-off Frequency is $f_{c_{m,n}} = \frac{K_C}{2\pi\sqrt{\mu\varepsilon}}$.	0
		OR	
	(b)	Discuss: TE mode of Circular Waveguide.	0
Q.3	(a) (b)	Compare: Series Resonator and Parallel Resonator What are the problems with Lossless T-Junction Power Divider? Explain WILKINSON Power Divider with necessary equations. OR	0
Q.3	(a)	Define: õResonance Isolatorö. Explain Resonance Isolator with E-Plane and S-Plane Slab.	0
	(b)	Write Short Note on: 180° HYBRID	0
Q.4	(a) (b)	With neat Sketch explain õBalanced Amplifierö using 90° Hybrid Coupler. Discuss: Time Varying Maxwelløs Equations. OR	0
Q.4	(a)	What do you understand by õConversion Loss of Mixerö? Explain õSingle Ended Mixer Circuit	0
	(b)	What is õMicrowave Integrated Circuit? Explain Monolithic Microwave Integrated Circuit in brief with advantage and disadvantage.	0
Q.5	(a)	A lossless T-Junction power divider has a source impedance of 100 . Find the output characteristics impedance so that the input power is divided in a 2:1 ratio. Compute the reflection coefficients seen looking into the output ports	0
	(b)	Explain Gain and Stability of two port amplifier circuit in terms of S parameter of Transistor.	0
Q.5	(a)	OR Draw õLumped-element equivalent circuitö of two wire Transmission Line.	0
	(b)	Prove that Characteristic Impedance: $Zo = \sqrt{L/C}$ with necessary equations. Write Short Note on: Smith Chart	0
