Sea	t No.: ₋	Enrolment No GUJARAT TECHNOLOGICAL UNIVERSITY M. E SEMESTER – II • EXAMINATION – SUMMER • 2014	
Sul Tin	oject l ne: 02 tructio	code: 1720305 Date: 20-06-2014 Name: Applied Transducers 2:30 pm - 05:00 pm Total Marks: 70 ons:	
	2.	Attempt all questions. Make suitable assumptions wherever necessary. Figures to the right indicate full mark.	
Q.1	(a) (b)	Explain the principle of linear and rotary incremental position encoder. Explain the chopper amplifiers.	07 07
Q.2	(a) (b)	Write a short note on turbine flow meter in detail. Draw and explain the current telemetering using four wires, three wires and two wires.	07 07
	(b)	OR Explain different grounding methods and equivalent circuit to analyze them.	07
Q.3	(a) (b)	Explain the vortex shedding flow meters in detail. Draw and explain the basic circuit for digital to resolver converter. OR	07 07
Q.3	(a) (b)	Explain the offset and drifts in op-amp. Draw and explain the basic circuit for resolver to digital converter.	07 07
Q.4	(a)	How the vibrating wire strain gauge used for multiple applications? Explain in	07
	(b)	detail. Find the input zero error (IZE) and output zero error (OZE) of amplifier for voltage divider and also state the heat generated and dissipated components of amplifiers.	07
		OR	
Q.4	(a) (b)	Explain the drifts in variable resistance (potentiometer). Explain the composite amplifiers with suitable diagrams.	07 07
Q.5	(a) (b)	Explain the applications of Thermistors in detail. Explain the principle of absolute position encoder. OR	07 07
Q.5	(a) (b)	Draw and explain the noise in transimpedance amplifier. Explain the application of LVDTs.	07 07
