Seat No.: Enrolment No			
•		GUJARAT TECHNOLOGICAL UNIVERSITY M. E SEMESTER – II • EXAMINATION – SUMMER • 2014 code: 1722901 Date: 16-06-2014 Name: Advanced Power Converters and Control	
· ·			
		tions:	
	2.	Attempt all questions. Make suitable assumptions wherever necessary. Figures to the right indicate full marks.	
Q.1	(a)	Explain control characteristics of converters used in HVDC transmission system.	07
	(b)		07
Q.2	(a)	 45 H, C = 7 F, and R = 4á. The frequency of output voltage is 4.5 kHz and DC input is 200 Volt. SCR turn off time is 15 Sec. Calculate: (a) Circuit turn off time, (b) Maximum possible output frequency and 	07
	(b)	 (c) Capacitor voltage. Describe M type ZCS resonant converter with neat diagram and appropriate waveforms. 	07
		OR	
	(b)	With neat circuit diagram and waveform discuss class E resonant inverter.	07
Q.3	(a)	converter. Explain 5 th and 7 th harmonics elimination in 12-pulse converter.	07 07
	(b)	appropriate example.	U/
		OR	
Q.3	(a) (b)	_	07 07
Q.4	(a) (b)	•	07 07

Q.4 Discuss venturini control method for matrix converter in brief. (a) **07** What is need of small signal model? Explain small signal model of 07 **(b)** converter circuit. Explain voltage control mode of DC-DC converters. **Q.5 07** (a) Explain high frequency link integral half cycle converter with neat diagram. **07 (b)** Discuss the basic concept of multi pulse converter. Explain how the **Q.5** (a) 07 number of pulses can be increased from available three phase supply. What are the advantages of multi-level inverter w.r.t. two-level inverter? **(b)** 07
