Seat No.:		Enrolment No	
		GUJARAT TECHNOLOGICAL UNIVERSITY	
		M. E SEMESTER - II • EXAMINATION - SUMMER • 2014	
Subject (		t code: 1723106 Date: 23-06-2014	
Sul	bject	Name: Electromagnetic Compatibility	
		2:30 pm - 05:00 pm Total Marks: 70	
Inst	tructio		
		Attempt all questions.  Make suitable assumptions wherever necessary.	
		Figures to the right indicate full marks.	
Q.1	(a)	Derive the equation of magnetic coupling for shielded receiver conductor	07
	(b)	when shield is grounded at both ends.  Derive the capacitive coupling equation when center conductor is extended	07
	(6)	beyond the shield on receiver side and shield is not grounded.	U I
Q.2	(a)	What is the difference between magnetic coupling and capacitive coupling?	07
Q. <u>-</u>	(4)	How they are actually represented through electric circuits?	07
	<b>(b)</b>	What are the three necessary elements to produce an interface problem?	07
		Explain types of noise sources with examples. Explain concept of typical	
		noise path.  OR	
	(b)	Explain types of capacitor with construction and material used.	07
Q.3	(a)	Define hybrid ground. Draw their circuits and Give reason for their behavior.	07
<b>Q.</b> 5	(b)	Define CMRR. Derive the equation of CMRR for Unbalance source	07
	( )	resistance. Give any example of such situation.	
0.1	( )	OR	0.7
Q.3	(a) (b)	What is a parasitic effect? Explain concept of parasitic effect with any circuit.  Derive the equation of CMRR for Unbalance load resistance. Give any	07 07
	(6)	example of such situation.	U I
Q.4	(a)	Explain various noises in circuits operating at high frequency with necessary	07
r.y	(a)	circuits.	07
	<b>(b)</b>	How to ground the shield when an ungrounded amplifier is connected to the	07
		grounded source. Which one is best connection and why?	
Q.4	(a)	OR  Explain networks that used across the load to minimize the inductive kick	07
Q.1	(4)	produced by an Inductor.	07
	<b>(b)</b>	How internal noise source cause disturbances to Digital circuit? Explain it	07
		with any circuit.	
Q.5	(a)	Write a short note on Near field measurements.	07
	<b>(b)</b>	Explain Intrinsic noise sources. How it can be calculated?	07
Q.5	(a)	OR Explain methods of Noise Factor measurements.	07
<b>Q.</b> 3	(a) (b)	Write a short note on ferrites	07

\*\*\*\*\*