Sea	ıt No.:	Enrolment No	-
GUJARAT TECHNOLOGICAL UNIVERSITY M. E SEMESTER – II • EXAMINATION – SUMMER • 2014 Subject code: 1724502 Date: 18-06-2014 Subject Name: Power Electronics-II			
	•		
Time: 02:30 pm - 05:00 pm Total Marks: 70 Instructions:			
		. Attempt all questions.	
		. Make suitable assumptions wherever necessary.	
	3.	Figures to the right indicate full marks.	
Q.1	(a)	Explain concept and importance of High Frequency Transformer. Also write steps for the designing of the same.	07
	(b)	For the Basic Series Resonant Inverter having L ₁ = L ₂ = L = 50 μH, C = 6 μF, R = 2Ω, the DC input voltage is 220 V and frequency of output voltage is 7 KHz. The turn off time of the switch is 10 μS. Determine: (i) The available turn off time (ii) The maximum permissible frequency (iii) The peak-to-peak capacitor voltage Support answer with necessary circuit and waveforms.	07
Q.2	(a)	List disadvantages of Single-Phase Line-Commutated Rectifiers. Suggest necessary circuit, waveforms and control system diagram of Single Phase Boost	07
	(b)	Rectifier. Explain the working of the PFC circuit shown in fig.1. Also draw the waveforms for switch 'S, Input Current $i_1(t)$ and Input V-I Characteristics. OR	07
	(b)	Explain the working of the PFC circuit shown in fig.2. Also draw the waveforms for switch 'S, Input Current $i_1(t)$ and Input V-I Characteristics.	07
Q.3	(a)	With necessary circuit and waveforms explain operation of High Frequency Link Integral Half Cycle Converter.	07
	(b)	Explain Two Quadrant ZVS Resonant Converter. Support the answer with necessary circuits and waveforms.	07
		OR	
Q.3	(a)	Explain 3-Ø Resonant DC link Inverter. Also explain Active Clamp Circuit for the same.	07
	(b)	Explain L-type ZCS Resonant Converter. Support the answer with necessary circuits and waveforms.	07
Q.4	(a)	Compare various Multilevel carrier-based PWM techniques for Multilevel inverter. Draw necessary diagram to support the answer.	07
	(b)	Explain Single Phase structure of a Multilevel Cascaded H-Bridge Inverter with five separate DC sources. Support the answer with necessary circuit and waveforms.	07
0.4	(-)	OR Explain concent of Multilevel Convertor Compare the same with respect to	07
Q.4	(a)	Explain concept of Multilevel Converter. Compare the same with respect to	07

(b) Compare Five Level Diode Clamped and Capacitor Clamped Inverter in all

(a) Explain significance of Multi-Pulse Converters. Also explain Twelve Pulse

Conventional Converter.

Converter with Application.

Q.5

respect. Draw necessary circuits in support.


07

07

(b) Explain Power Factor in Electrical Power Systems with Linear and Non-Linear Loads. Derive necessary equations to support the answer.

OR

- Q.5 (a) Explain working Principle of Matrix Converter. Also discuss Practical issues 07 related to same.
 - (b) Explain importance of EMI filters. Also write steps involves in designing of the same. 07

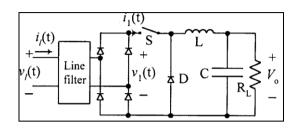

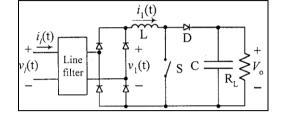


Fig.1 Q.2 (b)

Fig.2 Q.2 (b) (OR)
