Enrolment No.

# **GUJARAT TECHNOLOGICAL UNIVERSITY**

## M. E. - SEMESTER – II • EXAMINATION – SUMMER • 2014

Subject code: 2725204

Date: 12-06-2014

Subject Name: Designing with Modeling and FPGA's

Time: 02:30 pm - 05:00 pm

## **Total Marks: 70**

#### Instructions:

- 1. Attempt all questions.
- 2. Make suitable assumptions wherever necessary.
- 3. Figures to the right indicate full marks.
- Q.1 (a) Draw the structure of MOSFET and explain its behavior when its terminal 07 voltages  $V_{GS}$  and  $V_{DS}$  vary. Obtain the relationship between the drain current of a MOSFET and its terminal voltages (Neglecting Second order effects).
  - (b) Draw the Common Source stage with resistive load, diode connected load, 07 current source load and triode load. Discuss Proøs and Conøs of each configuration.
- Q.2 (a) Describe the operation of Basic current mirror with a circuit diagram. 07 Derive an equation for current gain. Specify your assumptions.
  - (b) Discuss various feedback topologies and their effect on input and output 07 impedances.

OR

(b) Briefly explain MOSFET second-order effects. Discuss channel length 07 modulation in detail.

# Q.3(a)Discuss Performance parameters of an OPAMP.07(b)Design a fully differential telescopic op amp with the following07

specifications:  $V_{DD} = 3V$ , Power dissipation = 10mW, voltage gain = 1400. Assume  $_{n}C_{ox} = 60 \quad A/V^{2}$ ,  $_{p}C_{ox} = 30 \quad A/V^{2}$ ,  $\lambda_{n} = 0.1 V^{-1}$ ,  $\lambda_{p} = 0.2 V^{-1}$  (for an effective channel length of 0.5 m)  $V_{THN} = |V_{THP}| = 0.7v$ .

#### OR

~ ~	<i>(</i> )		~-
Q.3	(a)	Explain the condition for oscillation and condition for stability in a negative	07
		feedback system. Discuss in detail two frequency compensation techniques.	
	<b>(b)</b>	Which properties of noise can be predicted? Explain any two in detail.	07
Q.4	<b>(a)</b>	Draw and explain the circuit implementation of generating supply independent current and generation of temperature independent voltage.	07
	<b>(b)</b>	Discuss speed and noise issues in bandgap reference circuits with the help of an example.	07
		OR	
Q.4	(a)	Discuss the behavior of MOSFET as a sampling switch.	07
	(b)	Explain the following in detail	07
		(i) Ring oscillator (ii) Voltage controlled oscillator	
Q.5	<b>(a)</b>	Discuss the necessity, operation and implementation of simple Charge pump	07
		PLL with appropriate diagrams.	
	(b)	List ADC specifications. Discuss briefly any two ADC architectures.	07
		OR	
Q.5	(a)	Explain the terms below.	07
	. /	(i) Bus functional modeling (ii) Timed and untimed functions (iii) TLM	

(b) Draw the high frequency model of a common-source stage. Explain what 07 Millers theorem is and how it is useful in analyses of frequency response of the amplifier.

\*\*\*\*\*