GUJARAT TECHNOLOGICAL UNIVERSITY M. E. - SEMESTER – I • EXAMINATION – SUMMER • 2014

Subject code: 710702N Date: 17-06-2014 **Subject Name: Advanced Power Electronics** Time: 02:30 pm - 05:00 pm **Total Marks: 70 Instructions:** 1. Attempt all questions. 2. Make suitable assumptions wherever necessary. 3. Figures to the right indicate full marks. (a) Explain single quadrant, two quadrant and bidirectional operation of 07 Q.1 switches. Suggest power semiconductor devices capable to realize it. **(b)** Discuss steps illustrating design of inductor. **07** Q.2(a) Discuss static and dynamic characteristics of power MOSFET and IGBT. 07 (b) Distinguish isolated and non isolated converters. Discuss PUSH-PULL **07** converter. OR **(b)** Write short note on SMPS design criterion. 07 (a) Explain full bridge dc-dc converter. 0.3 **(b)** Discuss selected harmonic elimination technique to eliminate 5th and 7th harmonics from output voltage of the inverter. OR (a) Compare operation of 3-phase bridge inverter with 150° , 120° and 180° 07 Q.3conduction mode. **(b)** Discuss space vector pulse width modulation (SVPWM) technique in brief. 07 **Q.4** Discuss importance of isolation in driver circuit. Discuss various 07 electrically isolated driver circuits. **(b)** Discuss circulating current operation of 3-phase cyclo-converter. 07 OR **Q.4** (a) Discuss cascade connected drive circuits. Explain driver circuit protection 07 in brief. **(b)** Explain difference in inverter and cyclo-converter circuit. 07 **Q.4** Q.5 (a) Explain operation of current source inverter with neat diagram. Differentiate it from voltage source inverter. (b) What is the difference in design of power transformer and high frequency 07 transformer? OR (a) Discuss Couk converter with suitable diagram and waveforms. 07 Q.5 **(b)** Explain operation 3-phase full wave controllers with resistive loads. 07
