Seat No.:	Enrolment No.
-----------	---------------

GUJARAT TECHNOLOGICAL UNIVERSITY M. E. - SEMESTER – I • EXAMINATION – SUMMER • 2014

Subject code: 713101N Date: 13-06-2014 **Subject Name: Medical System Design** Time: 02:30 pm - 05:00 pm **Total Marks: 70 Instructions:** 1. Attempt all questions. 2. Make suitable assumptions wherever necessary. 3. Figures to the right indicate full marks. Q.1 Design 50V/1A regulated power supply with series pass element and short 10 circuit protection circuit. Vin = 230± 20V, Ripple Voltage (v): 7% ripple of Vo & t = 3msec (b) Sketch Necessary Voltage Wave form at every stage of Above Power supply 04 design. **Q.2** (a) Prove that oWhen operated with negative feedback, an ideal op-amp force V_N **07** to track V_p but without drawing any current at either input terminal.ö (b) Explain Constant current limiting circuit with necessary safe operating area. **07** OR Explain fold back current limiting circuit with necessary safe operating area. **07** (b) Q.307 Explain Current óVoltage Converters. (a) Explain Instrumentation Amplifier with its advantages. 07 **(b)** OR Q.3 Explain Voltage-Current Converters. 07 (a) Derive Equation for V_{CM} and V_{DM} for Difference Amplifier. (b) **07** Explain Op-amp as a Voltage Comparator with any one application in detail. **Q.4** 07 (a) Explain Resistance transformer with its ideal equivalent circuit. 07 (b) OR 0.4 Derive the equation for V_T for Non Inverting Schmitt Trigger. **07** (a) Explain sample and Hold Circuit & determine acquisition time to 0.1% full **07 (b)** scale or a 10V step input with $C_H = 10$ nf and $R_{ON} = 300$ **Q.5** Explain PLL and explain its operation in Locked Condition. **07** (a) Explain 4-bit approximation A to D converter. 07 **(b)** OR **Q.5** Explain Logarithmic Characteristic and transdiode configuration of amplifier. 07 (a) (b) Write a short note on Pipe Line structured ADC. 07
