Enrolment No.

GUJARAT TECHNOLOGICAL UNIVERSITY M. E. - SEMESTER – III • EXAMINATION – SUMMER • 2014

Subject code: 734501Date: 03-06-2014Subject Name: Application of Power Electronics to Power SystemTime: 02:30 pm - 05:00 pmTotal Marks: 70

Instructions:

- 1. Attempt all questions.
- 2. Make suitable assumptions wherever necessary.
- 3. Figures to the right indicate full marks.
- Q.1 (a) State the names of various shunt, series and hybrid type FACTS devices and 07 write function of each in brief.
 - (b) Derive the ratio of reactive power compensation to be provided by a series of compensator and a midpoint shunt compensator, to achieve the same change in active power transfer through a given transmission line. Assume identical voltages at respective ends of the line in both the cases. Calculate this ratio for a line operating with a 15° phase angle difference between the two ends.
- Q.2 (a) A STATCOM made of 3-phase converter with constant dc link voltage, is capable of providing pure sinusoidal terminal voltage while operating in linear modulation range of 0.05 < m < 0.95, where *m* is amplitude modulation index. Find attainable lead and lag var compensation range of this STATCOM, when it is connected at mid-point of transmission line via a 0.2 per unit reactance. Assume the mid-point voltage being held constant at $1.0 \angle 0^\circ$ per unit. For synchronization of STATCOM with the line, the modulation index has to be kept at m=0.6.
 - (b) Explain the operation of Static Synchronous Series Capacitor (SSSC).

OR

- (b) Give comparison of conventional shunt/series compensation schemes and 07 FACTS schemes used in AC transmission systems.
- Q.3 (a) Explain how the series capacitive line compensation can cause subsynchronous 07 resonance (SSR). Show that a TCSC compensated line cannot cause SSR.
 - (b) Explain the principle of operation of basic Thyristor-Controlled Series 07 Capacitor (TCSC) scheme.

OR

- Q.3 (a) Explain steady-state operation of TCSC in capacitive region along with 07 relevant waveforms of Capacitor voltage and current; and TCR voltage and current.
 - (b) Draw and explain reactance (X_{TCSC}) vs thyristor firing delay angle (α) 07 characteristics of TCSC.
- Q.4 (a) Explain the "direct" output voltage control scheme based on internal voltage 07 (magnitude and angle) control at a sustained dc capacitor voltage for implementation of STATCOM. Draw relevant schematic block diagram and waveforms.
 - (b) Explain the application of STATCOM for improving transient stability of a 07 power system. Discuss the control strategy used.

OR

Q.4 (a) Explain the "indirect" output voltage control scheme based on variation of dc 07 capacitor voltage for implementation of STATCOM. Draw relevant schematic block diagram and waveforms.

1

07

	(b)	Explain principle of operation of UPFC with relevant phasor diagram and describe its implementation using back to back VSCs with schematic diagram.	07
Q.5	(a)	Explain operation of FC-TCR.	07
_	(b)	Explain the basic working principle of Thyristor Controlled Transformer.	07
		OR	
Q.5	(a)	Draw and explain V-I characteristics of Mechanically Switched Capacitor (MSC) ó Thyristor Controlled Reactor (TCR) with and without voltage control.	07
	(b)	Explain operation of TCR.	07
