GUJARAT TECHNOLOGICAL UNIVERSITY ME - SEMESTER- II (Old course)• REMEDIAL EXAMINATION – SUMMER 2015

Subject Code: 1720302 Date:13/05/2015


Subject Name: Advance Instrumentation

Time: 02:30 pm to 5:00 pm

Instructions:

Total Marks: 70

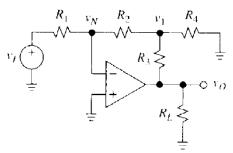
- 1. Attempt all questions.
- 2. Make suitable assumptions wherever necessary.
- 3. Figures to the right indicate full marks.
- 4. Make suitable assumptions wherever necessary and mention it clearly in your solution.
- 5. Consider design parameters of 741 op-amp when not mentioned explicitly in question.
- 6. Necessary circuit diagrams are must while deriving for equations.
- 7. Show all node voltages and branch currents used in your derivations.
- 8. Figures to the right indicate full marks.
- Q.1 Derive the equations for ideal gain and actual gain of the circuit shown in following figure. Consider $R_1 = 1 \text{ M} \acute{a}$, $R_2 = 1 \text{ M} \acute{a}$, $R_3 = 100 \text{ k} \acute{a}$, $R_4 = 1 \text{ k} \acute{a}$, and $R_L = 2 \text{ k} \acute{a}$, evaluate ideal and actual gain considering $r_d = 1 \text{ M} \acute{a}$, $a = 10^5 \text{ V/V}$, and $r_0 = 75 \text{ } \acute{a}$.



- Q.2 (a) What do you mean by loading effect? With the help of circuit diagram and 07 equations explain the loading effect in voltage amplifier. Explain your point considering suitable values of resistors and parameters.
 - (b) Derive the equation of closed loop actual gain of non-inverting amplifier. 07

OR

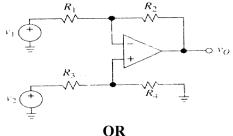- (b) Design a variable source having the range -10V Ö Vs Ö10V using a 741 opamp and a 100 ká potentiometer. What is the need of op-amp in this design? If Vs is set to 5V how much does it change when we connect a 1 ká load to the source?
- Q.3 (a) What is the need of bridge linearization circuits? Discuss them with the help of 07 circuit diagrams and necessary equations.
 - (b) Derive the equations of A_{dm} , A_{cm} , and $CMRR_{dB}$ for difference amplifier shown 07 in following figure.




Q.3 (a) Draw the circuit diagram of dual op-amp instrumentation amplifier with 07 variable gain and derive the equation of gain. Consider virtual short condition.


- (b) Draw the circuit diagrams of Howland and Improved Howland current pump and prove the advantage of Improved Howland circuit over Howland circuit by suitable example.
- Q.4 (a) Draw the circuit diagram of second order low pass KRC filter and derive the 07 equations for gain, 0 and Q-factor. Using the equal component design, specify elements for a second order low pass filter with $f_0 = 2$ kHz and Q = 5. What is the dc gain of this design?
 - (b) Define input bias and input offset currents. What are their typical valued for 741 op-amp? Derive the equation of error voltage generated due to input bias and input offset currents. Give your suggestion to reduce the error voltage.

OR

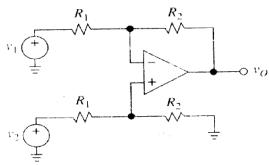- Q.4 (a) List important features of switched capacitor filters. Discuss its practical 07 limitations in detail.
 - (b) The difference amplifier shown in following figure uses 741 op-amp and a perfectly 07 matched resistance set with $R_1 = 10$ k and $R_2 = 1000$ k . Suppose the inputs are tied together and driven with a common signal v_{i} . Estimate the typical change in v_0 if (i) v_1 is slowly changed from 0 to 10V, and (ii) v_1 is a 100 kHz, 10V peak to peak sine wave. Consider CMRRdB (100 kHz) = 37dB.



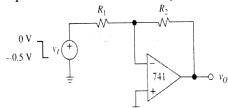Q.5 (a) Explain slew rate with the help of necessary waveforms and derivations. An opamp shown in following figure has an input bias current of 15 A and a compensation capacitance Cc of 20 pF, and slew rate of 0.5V/ s, find its response $v_o(t)$ to a step input of -0.5 V. Consider $R_1 = 2 k$ and $R_2 = 8 k$.



(b) With the help of circuit diagram and frequency response discuss the limitation 07 of differentiator circuit and provide solution for the same.

OR

- Q.5 (a) Discuss following terms (i) Spectral noise density (ii) Noise power density (iii) 06 White noise
 - (b) Describe the effect of finite GBP on integrator circuits.

08
