

GUJARAT TECHNOLOGICAL UNIVERSITY**ME - SEMESTER– II (Old course)• REMEDIAL EXAMINATION – SUMMER 2015****Subject Code: 1720705****Date:14/05/2015****Subject Name: Application of Power Electronics to Power System****Time: 02:30 pm to 5:00 pm****Total Marks: 70****Instructions:**

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.

- Q.1** (a) Explain Automatic Generation Control (AGC) and Excitation Control mechanism. **07**
- (b) Derive an expression for mid-point voltage of a symmetrical lossless transmission line as a function of power flow on it. Also, mention the typical values of line inductance and capacitance. **07**
- Q.2** (a) Explain (a) Load Compensation and (b) System Compensation and its effect on system. **07**
- (b) Explain Multilevel VSC-Based STATCOM and state its salient features. **07**
- OR**
- (b) Explain the working principle of UPFC and its various power flow control functions with the help of phasor diagrams. **07**
- Q.3** (a) For a given 765 kV, 50 Hz, 1000 km long, symmetrical transmission line with $l = 0.93 \text{ mH/km}$, $c = 12.1 \text{ nF/km}$ mid- point compensated line, compute uncompensated real power (P_s), compensated real power (P_{comp}) with unlimited capacity compensator at midpoint maintaining mid-point voltage to be 1.02 pu and injected reactive power (Q_v). The value of load angle δ is 30° . Also comment on results. **07**
- (b) Explain FC-TCR and its $V-I$ characteristics without coupling transformer. **07**
- OR**
- Q.3** (a) Explain with the help of suitable diagram working principle of STATCOM and its V-I characteristic. **07**
- (b) For a given 765 kV, 50 Hz, 1000 km long, symmetrical transmission line with $l = 0.93 \text{ mH/km}$, $c = 12.1 \text{ nF/km}$ mid- point compensated line, the operating load angle can be varied from 20° to 60° . Find the MVAR capacity range for var compensator. V_{mc} is to be held at 1.03 pu. Also, comment on results. **07**
- Q.4** (a) Define and explain following in brief. **07**
i) TCR ii) TSC iii) TSSR iv) FACTs
- (b) Draw simplified reactance capability curve of a multi-module TCSC and explain it. Also, draw $V-I$ capability characteristic for a multi-module (2 and 3 modules) TCSC. **07**
- OR**
- Q.4** (a) Explain TCSC constant-angle (CA) controller model in detail. Also, explain the role of regulator with the help of suitable diagram. **07**
- (b) Explain synchronous condenser and its application in power system. **07**
- Q.5** (a) Explain Harmonic performance of TCSC. **07**
- (b) Draw and explain voltage-current characteristic and current characteristics of TSC-TCR. **07**

OR

- Q.5 (a)** Explain how the collapsing of voltage in system can be prevented using TCSC. **07**
Also, draw typical voltage profile for critical bus employing TCSC.
- (b)** Draw and explain *IEEE* First Benchmark System and its components. List **07**
various methods used for analysis of SSR and explain any one in detail.
