GUJARAT TECHNOLOGICAL UNIVERSITY ME - SEMESTER- II (Old course) • REMEDIAL EXAMINATION - SUMMER 2015 **Subject Code: 1722901** Date: 12/05/2015 **Subject Name: Advanced Power Converters and Control** Time: 02:30 pm to 5:00 pm **Total Marks: 70 Instructions:** 1. Attempt all questions. 2. Make suitable assumptions wherever necessary. 3. Figures to the right indicate full marks. 4. Notations used have usual meaning. **Q.1** Explain in brief, How switching stress can be reduced on Power switch using 07 (a) ZCS and ZVS topologies? (b) Explain high frequency link integral half cycle converter with neat diagram. **07** 0.2 Explain cascaded multilevel inverter with neat diagram. 07 (a) **(b)** Discuss 18-pulse AC-DC converter topology with relevant transformer 07 connections. OR Explain 12-pulse AC-DC converter with neat diagram and compare its (b) 07 performance with 6 ópulse AC-DC converter in all respect. Q.3Explain Flying capacitor type multilevel inverter circuit with switching control 07 strategy. Write a short note on reactive power drawn by the converters in HVDC **07** (b) system. OR Discuss clamped voltage topology for DC-DC converter with illustration. 0.3 07 (a) (b) Explain how averaged model is generated for buck type dc-dc converter. 07 **Q.4** (a) Discuss bidirectional switch topologies for matrix converter. 07 Describe zero current switch topology for DC-DC buck converter with neat (b) **07** diagram. OR **Q.4** Write a short note on DC-link capacitor voltage balancing in multi-level **07** (a) inverter circuit. Discuss pulse width modulation technique for matrix converter. **07 (b) Q.5** Explain voltage control mode of DC-DC converters 07 (a) Discuss different converter configurations for HVDC transmission. **07 (b)** OR **Q.5** Write a brief note on protection issues for matrix converter. **07** (a)

\*\*\*\*\*

Explain basic concept of HVDC transmission.

(b)

Compare AC transmission system with DC transmission system in all respect.

07