		GUJARAT TECHNOLOGICAL UNIVERSITY SEMESTER– II (Old course)• REMEDIAL EXAMINATION – SUMMER 201 t Code: 1724101 Date:12/05/20	
Subject Name: RF and Microwave Circuits Time: 02:30 pm to 5:00 pm Total Marks: 7			
Instructions: 1. Attempt all questions. 2. Make suitable assumptions wherever necessary. 3. Figures to the right indicate full marks. 4. Use smith chart if required			
Q.1	(a)	For a rectangular waveguide derive the expression of Field components for TE	07
	(b)	mode. Use the Smith chart to find the following quantities for the transmission line circuit having $Z_L = 60 + j50$ ô and $Z_0=50$ á . The length of transmission line is 0.4 . (a) The SWR on the line. (b) The reflection coefficient at the load.	07
		(c) The load admittance.(d) The input impedance of the line.(e) The distance from the load to the first voltage minimum.f) The distance from the load to the first voltage maximum.	
Q.2	(a)	Write short note on quarter wave transformer with reference to microwave	07
	(b)	engineering. State the limitations of transmission line theory OR	07
	(b)	For a load impedance $Z_1 = 60$ -j80 á, design single stub (short circuit) shunt tuning network to match this load to 50á line. Assume that load is matched at 2GHz, and load consists of resistor and capacitor in series. Use smith chart to solve this problem.	07
Q.3	(a)	Describe microstrip line. What are its applications? Explain any three types of microstrip lines in brief.	07
	(b)	Describe scattering matrix for Magic tee and explain its applications.	07
Q.3	(a)	List out characteristics requirement from conducting and substrate material used to design MMIC and discuss advantages of MMIC based circuits over discrete circuits.	07
	(b)	What are dominant modes in circular waveguide? How Besseløs Function plays an important role in deciding dominant mode in circular waveguide? Justify this with suitable expression for TE and TM modes of circular waveguide.	07
Q.4	(a)	What are microwave filters? Explain image parameters method and Insertion loss method of filter design.	07
	(b)	Write short note on partially loaded waveguide.	07
Q.4	(a)	OR Describe low pass constant-k filter sections in T and forms. What are its advantages? Which modifications are done using m-derived low pass and high pass filter T-section?	07
		-	

pass filter T-section? (b) Derive the telegrapher equations for two wire transmission line. What are the $\frac{\lambda}{4}$ importances of $\frac{1}{4}$ transmission line? 07

Q.5 (a) List out various types of mixer circuits and explain one of them in detail

(b) What do you mean by microwave oscillator? Explain working of microwave 07 oscillator.

OR

- Q.5 (a) State the applications of signal flow graph and derive expressions for _{in} and 07 _{out} of two port network with general source and load impedance using signal flow graph theory.
 - (b) Explain properties of Ferrite materials. Also explain any one Ferrite device with 07 its construction.

07