Enrolment No._____

GUJARAT TECHNOLOGICAL UNIVERSITY ME - SEMESTER- I (New course)• REMEDIAL EXAMINATION – SUMMER 2015

Subject Code: 2710709Date:16/0Subject Name: Electrical DrivesTime: 10:30 am to 1:00 pmTotal MarInstructions:Total Mar			/05/2015	
			ks: 70	
Inst	1. 2. 3.	Attempt all questions. Make suitable assumptions wherever necessary.		
Q.1	(a)	Draw and explain block diagram of an electric drive and significance of each block.	07	
	(b)	Explain with neat diagram the four quadrant operation of hoist/wrench.	07	
Q.2	(a)	What is Dual converter? Draw and explain how the circulating current is controlled in dual converter with simultaneous control.	07	
	(b)	What is the significance of controlled fly-wheeling? Explain the continuous current mode of operation for motoring and regenerative braking for separately excited DC motor fed from 1-phase fully controlled rectifier.	07	
	(b)	Derive the condition for steady state stable operation of an electric motor and explain its significance with suitable examples for AC and DC motors.	07	
Q.3	(a)	Explain semiconductor converter based controlled dynamic braking and composite braking of DC motor.	07	
	(b)	Explain working of DC-DC converter based multi quadrant drive. OR	07	
Q.3	(a)	For a doubly fed wound rotor induction motor, discuss the sub-synchronous motoring and sub-synchronous braking operation.	07	
	(b)	Explain AC-AC converter based three phase induction motor speed control.	07	
Q.4	(a) (b)	Explain working of six step inverter. With neat diagram explain any one closed-loop control scheme for controlling the speed of a VSI fed induction motor.	07 07	
0.4		OR		
Q.4	(a) (b)	Explain the CSI based induction motor drive system. Discuss the operation of a cylindrical rotor synchronous motor operating from a current source.	07 07	
Q.5	(a)	Derive the equation of torque for a wound field salient pole synchronous motor operating from a voltage source of constant frequency. Hence, draw the torque angle characteristics for the same.	07	
	(b)	Write a brief note on modified Kramer drive.	07	
a –		OR		
Q.5	(a) (b)	Write a brief note on static static scherbius drive. Write a brief note on braking methods for synchronous motor.	07 07	