GUJARAT TECHNOLOGICAL UNIVERSITY				
ME - SEMESTER- I (New course)• REMEDIAL EXAMINATION – SUMMER 2015 Subject Code: 2714502 Date:14 /05/2015				
Subject Code: 2714502 Date:14705/2015 Subject Name: Solid State DC Drives				
Time: 10:30 am to 1:00 pm Total Marks: 70			)	
	Instructions:			
	1.			
	2. 3.	Make suitable assumptions wherever necessary. Figures to the right indicate full marks.		
Q.1	<b>(a)</b>	Explain principle of speed control of DC motor with necessary operating modes? Specify their field of applications.	07	
	(b)	For type-A dc chopper with RLE load and continuous load current condition shows that per unit ripple current is maximum when duty cycle is 0.5. Also draw the necessary waveforms and circuit diagram.	07	
Q.2	<b>(a)</b>	What are the main factors which decide the choice of DC drive for a given application?	07	
	(b)	What is the effect of back-emf on the firing angle and avg. output voltage? Draw necessary waveforms.	07	
	<b>A</b> \	OR	~ <b>-</b>	
	(b)	Draw circuit diagram, waveform and write the equations for 3-phase semi- controlled rectifier control of separately excited DC motor.	07	
Q.3	<b>(a)</b>	Explain four quadrant operation of DC motor. Also mention constant power and constant power region operation in the characteristic.	07	
	(b)	Draw equivalent circuit and output voltage waveform of an ideal dual converter. Derive necessary condition of firing angles.	07	
0.2	(-)	OR Discuss the control design for a two quadrant channel singuit	07	
Q.3	(a) (b)	Discuss the control design for a two quadrant chopper circuit Develop a linearized transfer model of DC series motor.	07 07	
Q.4	(a) (b)	State and explain the important features of various braking methods of DC motors. Explain the principle of phase control. Obtain the equation of output voltage of phase controlled DC motor drive.	07 07	
0.4	(-)	OR	07	
Q.4	<b>(a)</b>	Field control is employed for getting speeds higher than rated and armature voltage control is employed for getting speeds less than rated. Why?	07	
	(b)	Explain the speed control of DC series motor using tap changing transformer and uncontrolled rectifier.	07	
Q.5	(a) (b)	Explain the armature control and flux control of DC motors. Draw circuit diagram, waveform and write the equations for 3-phase full controlled rectifier control of separately excited DC motor. <b>OR</b>	07 07	
Q.5	(a)	Explain synchronizing firing of circuit, pulse transformer and draw circuit for gate	07	
		protection.		
	(b)	With neat schematic block diagram describe the Micro-computer control of 4 quadrant DC drives with flow chart.	07	

\*\*\*\*