GUJARAT TECHNOLOGICAL UNIVERSITY ME - SEMESTER- I (New course)• REMEDIAL EXAMINATION – SUMMER 2015 Subject Code: 2714505 Date:16/05/2015			
Subject Name: Power Conditioning Time: 10:30 am to 1:00 pm Total Marks: ' Instructions:			
	1. 2.	Attempt all questions. Make suitable assumptions wherever necessary. Figures to the right indicate full marks.	
Q.1	(a)	Compare static condenser with synchronous condenser. Explain the static condenser in details with diagram.	07
	(b)	Discuss various power conditioners in details and state their limitations.	07
Q.2	(a)	Explain the operation of fly back converter with the required diagram and waveform.	07
	(b)	Compare voltage mode control and current mode control of SMPS.	07
OR			
	(b)	Compare series and shunt active filters.	07
Q.3	(a)	With block diagram and control algorithm, explain shunt active filters used for sinusoidal current control.	07
	(b)	Explain the PFC converters utilizing DCM operation.	07
		OR	
Q.3	(a)	Describe PWM converter topology for three phase four wire shunt active filter with necessary block diagram.	07
	(b)	Describe Selective Harmonics Elimination Modulation Technique.	07
Q.4	(a) (b)	Draw and Explain the block diagram of design of SMPS. Differentiate on-line and off-line Uninterrupted Power Supply (UPS).	07 07
		OR	
Q.4	(a)	State the advantages and disadvantages of coreless type induction heating. Also explain the working of coreless type induction heating.	07
	(b)	Write a short note on Harmonic Standards.	07
Q.5	(a) (b)	Discuss harmonic distortion limit as per IEEE-519:1992. Explain the operation of power supply for steel camera.	07 07
		OR	
Q.5	(a) (b)	Explain the basic operation of DSP control of active power filter. Write a short note on surge suppressors.	07 07
