
Seat No.:	Enrolment No
-----------	--------------

Subject Code: 2720312

## GUJARAT TECHNOLOGICAL UNIVERSITY ME- SEMESTER II— EXAMINATION – SUMMER 2015

Date: 26/05/2015

Ti	me: 2 truction 1.	Attempt all questions.	<b>'</b> 0
		Make suitable assumptions wherever necessary.  Figures to the right indicate full marks.	
Q.1	(a) (b)	Explain triple op-amp instrumentation amplifier and derive formula for gain. Which are different thermal sensors? Give different applications of thermal sensors.	07 07
Q.2	(a) (b)	Explain the error caused by Input bias and offset currents in detail Explain Power supply and filtering needs for Op-Amp.  OR	07 07
	<b>(b)</b>	Find $v_0/v_I$ for the circuit shown in figure 1.	07
Q.3		Draw the circuit diagram of second order high-pass KRC filter and derive equations for dc gain, $$ 0, and Q. Design a filter with f0 = 500 Hz and Q = 2 using unity gain circuit.	14
		OR	
Q.3		Explain and design a multiple feedback band-pass filter with $f_0=1 \mbox{KHz}, \mbox{ Q=10},$ and H0 = 20DB. Also draw the circuit.	14
Q.4	(a) (b)	Explain switched capacitor in detail Briefly explain Wireless Sensor Based on Microcontroller and Communicating Devices	07 07
Q.4	(a) (b)	OR How performance of integrator can be improved? Briefly explain types of standards used for smart sensors.	07 07
Q.5	(a)	Find n for a low-pass Butterworth response with fc =1kHz, fs=2kHz,	07
	(b)	$A_{max}$ =1dB, and $A_{min}$ =40dB. The difference amplifier of figure 2 uses a 741 op amp having CMRR of 90dB and perfectly matched resistances R1=10K and R2=100K. If the inputs are tied together and driven with a common signal vI (i.e v1 = v2 = vI) then estimate the typical change in vo if (i) vi is slowly changed from 0 to 10V and (ii) vi is a 10KHz, 10 V peak to peak sine wave. Consider CMRR at 10 KHz of 57 dB.	07
0.5		OR	-
Q.5	(a)	Find $v_N$ , $v_P$ and $v_O$ in the circuit shown in fig. 3. Repeat with 40 Ká resistance in parallel with .4mA source.	07
	(b)	Explain Transducer bridge and derive formula for v <sub>O</sub> .	07

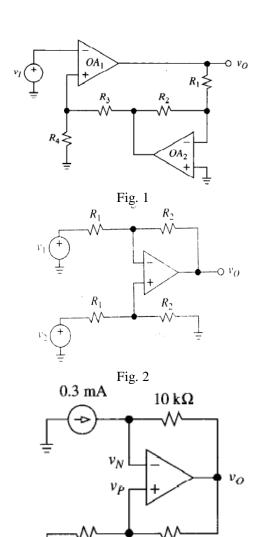

\*\*\*\*\*\*\*\*

Fig. 3

 $30~k\Omega$ 

 $20~k\Omega$