Seat No.:	Enrolment No.

GUJARAT TECHNOLOGICAL UNIVERSITY

ME- SEMESTER II - EXAMINATION - SUMMER 2015

-			/05/2015	
Гimе			Total Marks: 70	
	1. 2.	Attempt all questions. Make suitable assumptions wherever necessary. Figures to the right indicate full marks.		
Q.1	(a)	Mention the full names of series and shunt FACTS devices. Discuss the advantages of FACTS devices.	07	
	(b)	Briefly describe Sub-Synchronous Resonance. Mention the methods of mitigation of SSR.	07	
Q.2	(a)	Explain Static Voltage Compensator (SVC) in detail.	07	
	(b)	Write a short note on midpoint shunt compensation for a transmission line.	07	
	a >	OR	0.7	
	(b)	Discuss the application of SSSC as an active power controller. Draw and discuss the necessary control circuit.	07	
Q.3	(a)	Explain the construction and working of a Unified Power Flow Controller (UPFC).	07	
	(b)	Explain the schematic diagram and working principle of a STATCOM. OR	07	
Q.3	(a)	Draw the necessary block diagram and describe the application of a TCSC for SSR mitigation.	07	
	(b)	Write a short note on TSC-TCR.	07	
Q.4	(a)	Mention the modes of operation of a TCSC. Describe the Vernier Capacitive mode of operation in detail with steady state waveforms of voltages and currents.	07	
	(b)	Describe the Thyristor Controlled Reactor (TCR) with suitable diagram. Discuss its applications in the power system. OR	07	
Q.4	(a)	Mention the methods of passive reactive power compensation. Compare them with compensation using FACTS devices.	07	
	(b)	Mention the advantages of having slope in the dynamic characteristics of an SVC.	07	
Q.5	(a)	Discuss the role of TCSC as a power flow controller.	07	
	(b)	Explain the operating principle of FC-TCR in detail. OR	07	
Q.5	(a)	Explain the application of a suitable FACTS device to improve steady	07	
		state power transfer capability of transmission line.		
	(b)	Draw and discuss the firing delay angle versus the net fundamental reactance characteristic of a TCSC.	07	