Seat No.:	Enrolment No.
Jean 110	Emonient 110.

GUJARAT TECHNOLOGICAL UNIVERSITY ME- SEMESTER II— EXAMINATION – SUMMER 2015

Subject Code: 2720726 Date:03/06/ 2015 Subject Name: DIGITAL SIGNAL PROCESSING FOR POWER **ELECTRONICS** Time: 2:30 PM – 5:00 PM **Total Marks: 70** Instructions: 1. Attempt all questions. 2. Make suitable assumptions wherever necessary. 3. Figures to the right indicate full marks. 0.1 What are the desirable characteristics for power electronics device used for **07** (a) inverter application? **(b)** Why the Snubber circuit is used in power electronics application? Explain it 07 with circuit diagram. **Q.2** Explain working of Buck converter with wave-form. 07 (a) (b) Explain working of step-up DC-DC converter with waveform. 07 OR Explain how can you design inductor for step-up and step down DC-DC 07 converter. 0.3 What is the difference between half- bridge and full bridge topology used for 07 (a) single phase inverter? Explain 180 degree operation of inverter. (b) 07 **Q.3** Explain PWM switching technology used for inverter. Give its merits. (a) 07 Explain sine triangular method used for switching in inverter. 07 **Q.4** (a) Explain space vector PWM technique used for inverter. What is advantage of 07 it over other method? Explain hysteresis control strategy used for inverter. (b) 07 OR 0.4 Explain architecture for TI 2000 DSP. 07 (a) Explain different addressing mode for DSP. 07 (b) Q.5 Explain function of CAPTURE and ADC in DSP. 07 (a) Explain how DSP is used for switching for DC/DC converter for PV cell. 07 **(b)** OR 0.5 (a) Explain 120 degree operation for DC-AC converter. 07 How can you design snubber circuit for power electronics devices? 07 (b)