Seat No.:	Enrolment No
-----------	--------------

## GUJARAT TECHNOLOGICAL UNIVERSITY ME SEMESTED IL EVAMINATION SUMMED 2015

WIE-SEWIESTER II- EAAWIINATION - SUWIMER 2015						
Subject Name: POWER CONVERTER-II			2015			
			Total Marks: 70			
Instruction	ns:					
1. 2. 3. 4.	Ma Fig	rempt all questions.  Take suitable assumptions wherever necessary.  The suitable assumptions wherever necessary.				
Q.1	(a)	Describe M type ZCS resonant converter with neat diagram and	07			
	(b)	appropriate waveforms.  Discuss parallel resonant circuit for load resonant inverter.	07			
Q.2	(a)	The ZCS resonant converter has an input voltage of 18V. The output voltage is 12V ,resonant frequency 1MHz and $P_o=12$ W. Determine (i) The values of the resonant inductor and resonant capacitor (ii) the peak switch current and (iii) the peak voltage across the resonant capacitor.	07			
	(b)	Discuss Five-level multilevel inverter with diode-clamped topology with necessary diagrams and waveforms.  OR	07			
	(b)	Explain cascaded multi inverter with neat diagram.	07			
Q.3	(a)	Explain series loaded resonant DC-DC converter with unidirectional switches.	07			
	(b)	Discuss asynchronous modulation for multilevel converter.  OR	07			
Q.3	(a)	Discuss various transformer connections for multi-pulse converter.	07			
	(b)	Discuss venturini control method for matrix converter in brief.	07			
Q.4	(a)	Describe 12 pulse controlled converter with appropriate diagram	07			

**(b)** Discuss usage of Matrix converter in motor control application.

**07** 

Q.4	(a)	Discuss the basic concept of multi pulse converter. Explain how the number of pulses can be increased from available three phase supply.	07
	<b>(b)</b>	Discuss pulse width modulation technique for matrix converter.	07
- `	(a)	Explain how averaged model is generated for buck type dc-dc converter.	07
	<b>(b)</b>	Discuss voltage mode control of DC-DC converters in closed loop.	07
		OR	
Q.5	(a)	What is need of small signal model? Explain small signal model of a converter circuit.	07
	<b>(b)</b>	Write note on: - Adaptive control.	07

\*\*\*\*\*\*