Seat No.:	Enrolment No.

## **GUJARAT TECHNOLOGICAL UNIVERSITY**

ME - SEMESTER- I (OLD course)• EXAMINATION – SUMMER 2015

Subject Code: 710702 Subject Name: Advanced Power Electronics Time: 10:30 am to 1:00 pm Instructions:			Date:12/05/2015  Total Marks: 70	
		0:30 am to 1:00 pm Total Marks: 7		
11150	1. 2.	Attempt all questions.  Make suitable assumptions wherever necessary.  Figures to the right indicate full marks.		
Q.1	(a)	Draw and explain static <i>V-I</i> characteristics and transfer characteristics of Power MOSFET.	07	
	(b)	Draw the circuit of buck converter and explain its working in DCM when operating with constant input voltage $V_d$ . Also derive the expression,	07	
		$\frac{V_0}{V_d} = \frac{D^2}{D^2 + \frac{1}{4} \left(\frac{I_o}{I_{LB,max}}\right)}$		
Q.2	(a)	With neat diagram and necessary waveforms, explain the working of uk converter.	07	
	(b)	<ul> <li>Derive the expression for output voltage.</li> <li>(i) Compare SMPS with linear voltage regulator.</li> <li>(ii) Forward converter and DC-DC bridge converters (half-bridge or full bridge) are in-fact isolated buck converter. Which of these topologies is better? Justify your answer.</li> </ul>	07	
	(b)	OR With necessary discussions and derivation justify the following statement: õWhile operating with modulation index less than or equal to 1, output voltage of SVPWM is about 15% higher than that operating with SPWMö.	07	
Q.3	(a)	With neat waveforms explain the operation of 3-phase bridge inverter having 150° conduction mode control. Discuss how it incorporates the features of	07	
	(b)	both 180° and 120° conduction modes.  With relevant waveforms and circuit, explain the operation of 3-phase bidirectional (full wave) AC voltage controller operating with firing angle = 120° and feeding star connected resistive load.	07	
Q.3	(a) (b)	OR In a 1-phase ASCI, with load L, SCRs $T_3$ and $T_4$ are conducting a constant current $I = 10A$ . If $T_1$ and $T_2$ are turned on at $t = 0$ s to force commutate $T_3$ and $T_4$ ; find the time required for the load current to fall to zero. Load $L = 10~H$ and commutating capacitance $C = 6~F$ . Find also the total commutation interval and the circuit turn off time for each SCR.  Write a brief note on selective harmonic elimination technique.	07	
Q.4	(a)	A single-phase H-bridge inverter is triggered using a sine PWM control strategy. If amplitude modulation index is adjusted to unity and if frequency modulation index = 11 (eleven), show the harmonic spectrums for the output voltage for following cases: (i) Unipolar PWM and (ii) Bipolar PWM.	07	
	(b)	Write a brief note on the factors that decide the quality of output voltage in a Cyclo-converter.	07	

**Q.4** Draw the circuit for 3-phase to 1-phase cyclo-converter and discuss its **07** principle of operation in brief. **(b)** Draw and explain a gate driver circuit for firing a MOSFET operating at low **07** speed/low-switching frequency. Comment on how to achieve the four quadrant operation with conventional **Q.5** (a) **07** VSI. How is CSI superior to VSI in this aspect? What does one mean by Area Producto? List the steps involved in obtaining **07** (b) :Area-Productø for high frequency transformer used with forward converter. OR **Q.5** A single-phase AC voltage controller (having two anti-parallel connected 07 (a) SCRs) is feeding an R-L load having a load power factor angle . If the SCRs are triggered at a firing angle < , sketch the waveforms for output voltage and current for following cases: (i) if a single pulse with pulse width slightly more than thyristor turn off time) is used for firing (ii) if pulse train is used for triggering SCRs. State the important differences in the functioning and design of transformers **(b) 07** and inductors used for DC-DC converters. Also list the steps involved in the design of inductor of DC-DC converters.

\*\*\*\*\*