Seat No.:	Enrolment No
-----------	--------------

GUJARAT TECHNOLOGICAL UNIVERSITY

ME - SEMESTER- I (OLD course) • EXAMINATION - SUMMER 2015

Subject Code: 712902N Subject Name: Power Processing Circuits Time: 10:30 am to 1:00 pm Instructions:		Code: 712902N Date: 12/05/20	Date: 12/05/2015	
		0:30 am to 1:00 pm Total Marks: 70		
	1.	Attempt all questions. Make suitable assumptions wherever necessary. Figures to the right indicate full marks.		
Q.1	(a)	Explain construction and working of MOSFET. Also compare it with Power BJT in all respect.	07	
	(b)	Discuss about driving circuit for power Bipolar Junction Transistor switch.	07	
Q.2	(a) (b)	Explain working of Buck-boost DC-DC converter with neat diagram. A semi controlled bridge converter is supplied with single phase 240V, 50 Hz source, feeds a load with ripple free current. The load resistance is R_L =30 ohm. Find (1) Average load voltage (2) RMS input current for a firing angle =45. OR	07 07	
	(b)	A DC-DC buck converter is supplying energy to the load of R_L =20 ohms. The converter is operated with input voltage 200 Vdc. The switch is modulated with the frequency of 2 kHz. For duty cycle of 30%, calculate (i) t_{on} time (ii) Average output voltage (iii) output power of the converter.	07	
Q.3	(a)	Explain complementary voltage commutation of SCR with necessary waveforms.	07	
	(b)	Discuss the working operation of single phase integral cycle control for AC voltage controller.	07	
0.2		OR	0.5	
Q.3	(a) (b)	Explain three phase half wave converter circuit with necessary waveforms. Discuss the effect of source inductance on working of AC-DC converter.	07 07	
Q.4	(a)	Explain center-tapped 1-phase to 1-phase Cyclo-converter with neat circuit diagram and waveforms.	07	
	(b)	Discuss the working of DC-DC boost converter with appropriate waveforms. OR	07	
Q.4	(a)	Explain working operation of dual converter with circulating mode. Draw appropriate waveforms.	07	
	(b)	Describe working of phase controlled single phase AC-AC controller with R-L load with waveforms.	07	
Q.5	(a)	Explain working of three phase inverter circuit with 180 conduction mode. Draw line voltage and phase voltage waveforms.	07	
	(b)	Write a brief note on harmonics reduction in inverter output voltage. OR	07	
Q.5	(a) (b)	What is safe operating area? Discuss SOA for Bipolar Junction Transistor. Explain single pulse width modulation technique for single phase inverter circuit. Draw necessary waveforms.	07 07	