GUJARAT TECHNOLOGICAL UNIVERSITY

ME - SEMESTER-IV • EXAMINATION - SUMMER 2015

Subject Code: 742901 Date: 01/05/2015 **Subject Name: Harmonics and Filtration Methods** Time: 2:30 pm to 5:00 pm **Total Marks: 70 Instructions:** 1. Attempt all questions. 2. Make suitable assumptions wherever necessary. 3. Figures to the right indicate full marks. Explain about the generation of harmonics due to non-linearity of the load with **Q.1** 07 (a) suitable example. Define following terms and explain its significance. 07 **(b)** (1) Distortion factor (2) Total demand distortion **Q.2** Write a detailed note on monitoring of voltage events. 07 (a) A single phase fully controlled converter is supplying power to highly inductive 07 (b) load. If firing angle is , find the input current harmonics. A single phase AC-AC controller is feeding power to the resistive load. If firing **07** (b) angle is , find the load voltage harmonics. Q.3Explain singly tuned filter as a passive filter for harmonics filtration. Also 07 discuss general design aspects of passive filter. Write detailed note on harmonics propagation facts. 07 (b) Describe voltage event and write a brief note on its detection and evaluation. Q.307 (a) (b) Explain three phase four wire shunt active filter for power quality 07 improvement. **Q.4** Discuss the six pulse power converter as a source of harmonics generation. 07 also discuss about the characteristic harmonics generated due to power converter. Discuss how harmonics affect the performance of rotating machines. **07 (b)** OR **Q.4** Discuss the effect of harmonics on 07 (a) (1) Transformer (2) Capacitor bank Write a short note on series active power filter. Also compare its performance **07** with shunt active filter in all respect. 0.5 Explain Unified Power Flow Controller (UPFC) with neat diagram. 07 Describe hybrid active power filter for power quality enhancement with neat **07** (b) diagram. OR Describe voltage quality factor and power quality factor. Also discuss about its **Q.5** 07 (a) measurement and usage in brief. **(b)** Write a brief note on power quality measuring devices. 07
